

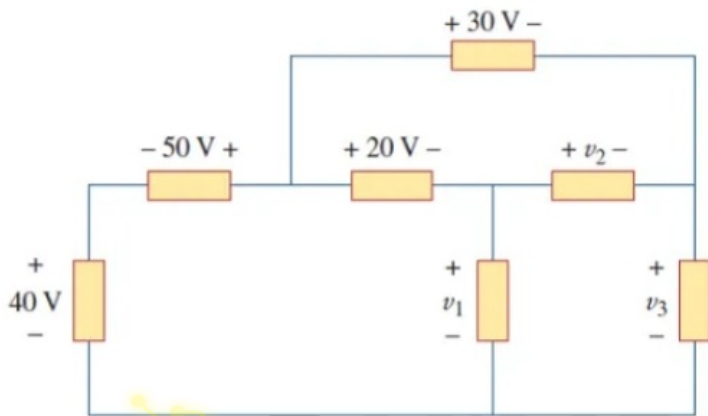



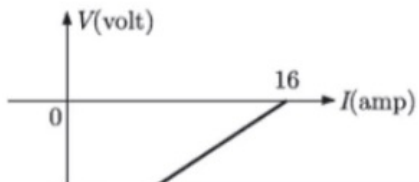
Find the value of v_3 in the circuit given below.




- 10 V
- 70 V
- 60 V
- 70 V
- 60 V

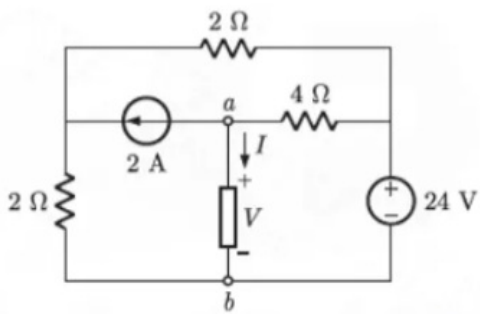The V-I curve of the element between the terminals a, b is given by




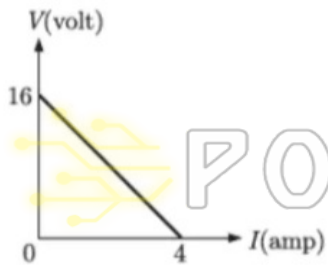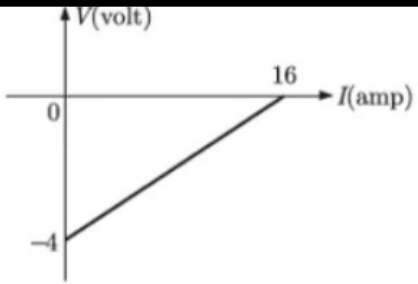

POWERUNIT

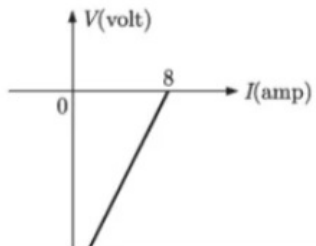


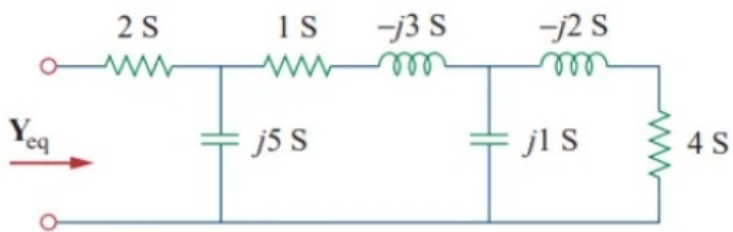For the circuit shown below, find the value of the equivalent admittance of the circuit Y_{eq}




- $Y_{eq} = 1.661 - j0.6647$
- $Y_{eq} = 0.6647 + j1.661$
- $Y_{eq} = 0.6647 - j1.661$
- $Y_{eq} = 0.6647 - j0.6647$
- $Y_{eq} = 1.661 + j0.6647$

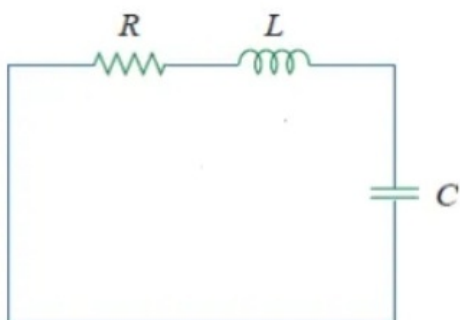What type of natural response will the circuit have when $R = 0$?




- An overdamped response
- An undamped response
- A critically damped response
- An underdamped response

Evaluate the phasor current I_2 .

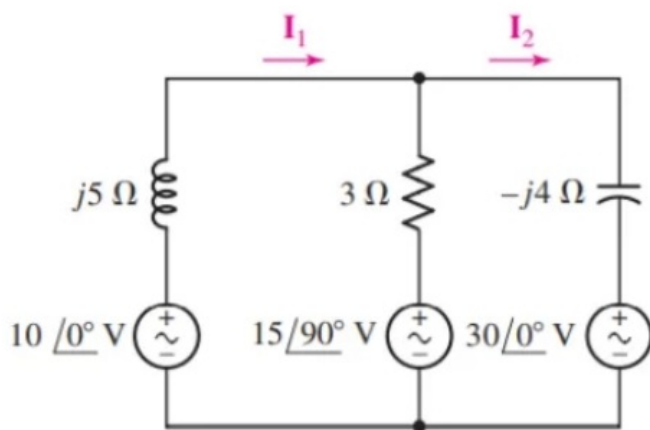


- POWERUNIT
- $6.255 \angle -170.094^\circ$
 - $6.255 \angle -140.518^\circ$
 - $9.979 \angle -170.094^\circ$
 - $7.17 \angle -144.9^\circ$
 - $9.979 \angle -140.518^\circ$

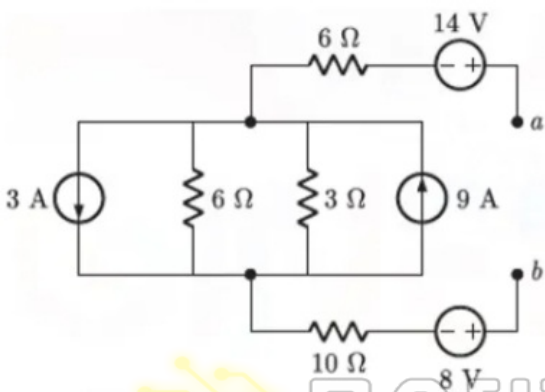One of the following circuits is equivalent to circuit shown below.




POWERUNIT

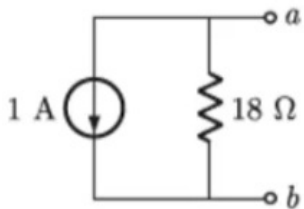


18 Ω

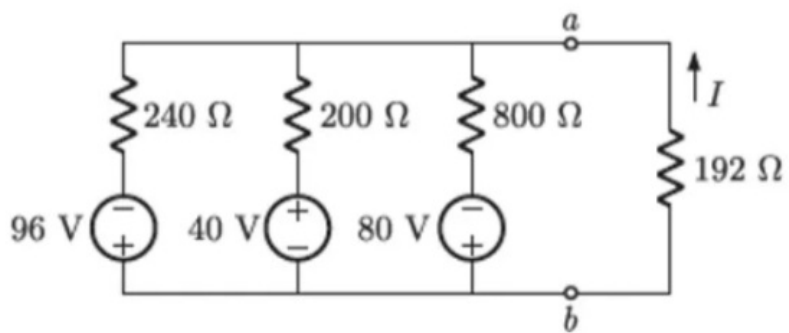Evaluate the current I in the circuit shown below.



- 10 mA
- 100 mA
- 233.33 mA
- 10 mA
- 100 mA
- 233.33 mA

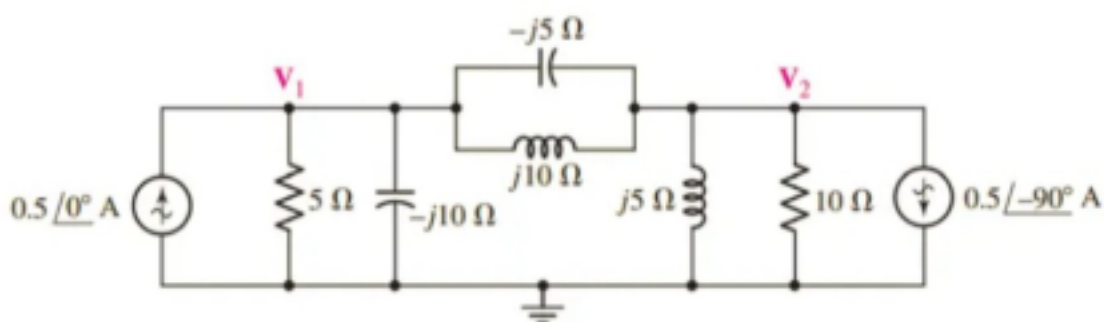Find the time-domain node voltage $v_1(t)$.



[Zoom image](#)

POWERUNIT

$v_1(t) = -\sin(\omega t)$


$v_1(t) = \sin(\omega t)$

$v_1(t) = 3.606\cos(\omega t + 123.69^\circ)$

$v_1(t) = 4.47\cos(\omega t + 116.6^\circ)$

$v_1(t) = 2.24\cos(\omega t - 63.4^\circ)$

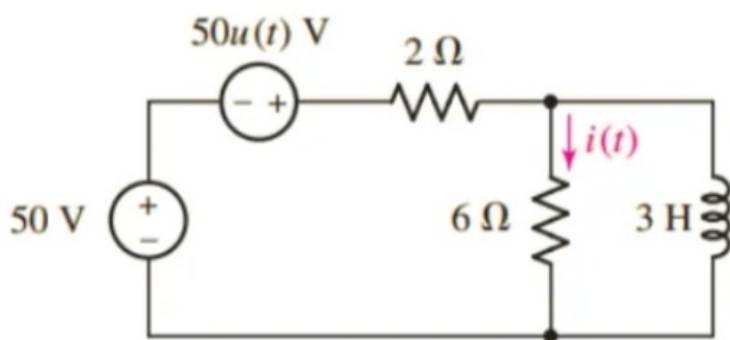
Find an expression for the current $i(t)$, for $t > 0$ in the circuit below.



POWERUNIT

- $i(t) = 50 - 25e^{-0.5t} \text{ A}$
- $i(t) = 50 - 37.5e^{-0.5t} \text{ A}$
- $i(t) = 37.5e^{-0.5t} \text{ A}$
- $i(t) = 6.25e^{-0.5t} \text{ A}$
- $i(t) = 50 - 18.75e^{-0.5t} \text{ A}$

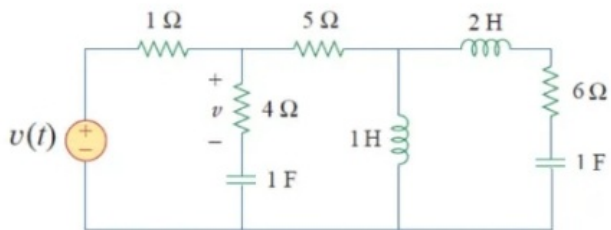
If $v(t) = 20 \cos(1000000t + 70^\circ)$. What is the maximum value of the voltage $v(t)$ (across the 4Ω resistor) in the figure?



🔍 Zoom image


- POWERUNIT
- 16 V
 - 0 V
 - 20 V
 - 8 V
 - 4 V

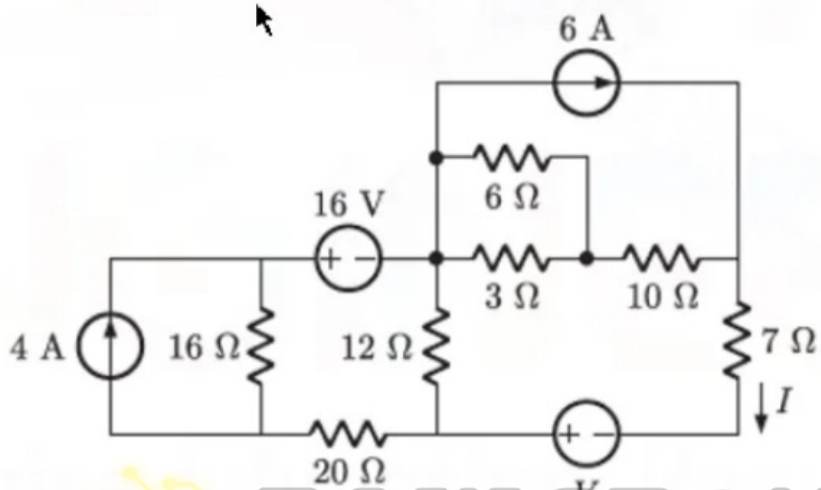If $I = 5\text{ A}$ in the circuit below, then the value of V_s is



- 56 V
- 224 V
- 228 V
- 200 V
- 28 V

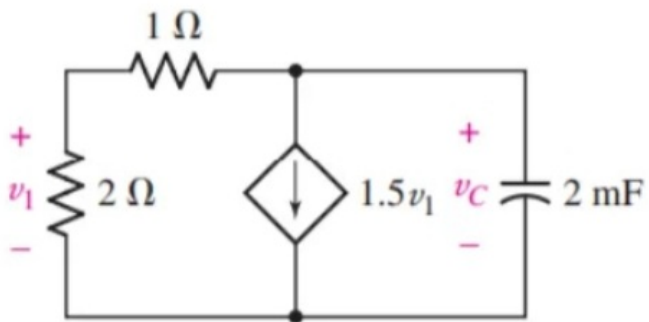Considering the circuit below, evaluate v_1 at $t=10^{-3}$ s when $v_c(0^-) = 11\text{V}$



7.5303 V

5.6476 V


11 V

3.7651 V

22 V

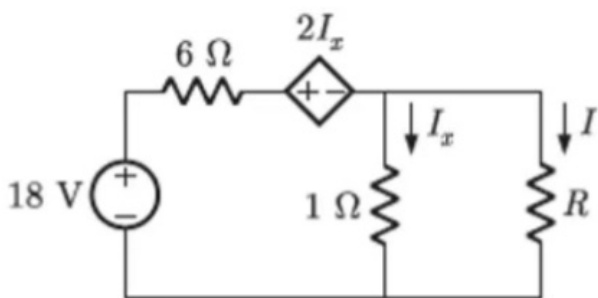11.295

For the circuit below, what value of R that will cause $I = 1 \text{ A}$?



POWERUNIT

- $R = 2/3 \Omega$
- $R = 4/3 \Omega$
- $R = 1/3 \Omega$
- It can not be determined
- $R = 0 \Omega$