

3

The breadboard is used to connect the elements with a need of Soldering of elements. \*  
(2 Points)



False

True

4

The cost of the resistor depends on \*  
(2 Points)

A. Ohmic value.

Both A and C


None of these.


C. Power ratings.

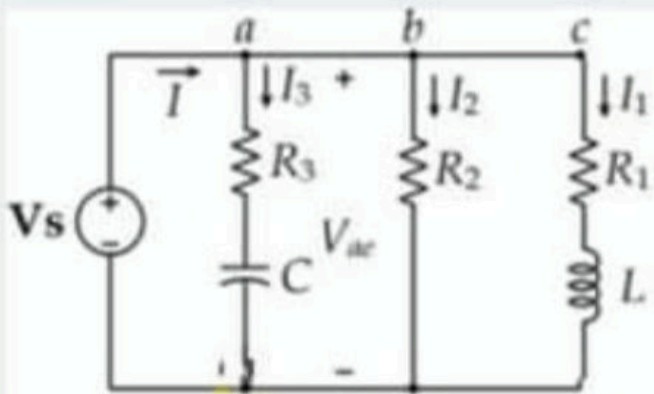B. Break down voltage.



5

According to the figure shown below, which statements is true: \*   
(2 Points)



Assume  $V_s$  is DC  
power supply


**$R_3 = 2R_1 = 4R_2$**

- D.  $I_1$  is one fourth of  $I_2$
- B. The current  $I_1$  is double of  $I_2$
- A. The current  $I_1$  is half  $I_2$
- Both B and C are correct
- Both A and C are correct
- C.  $I_3 = 0$

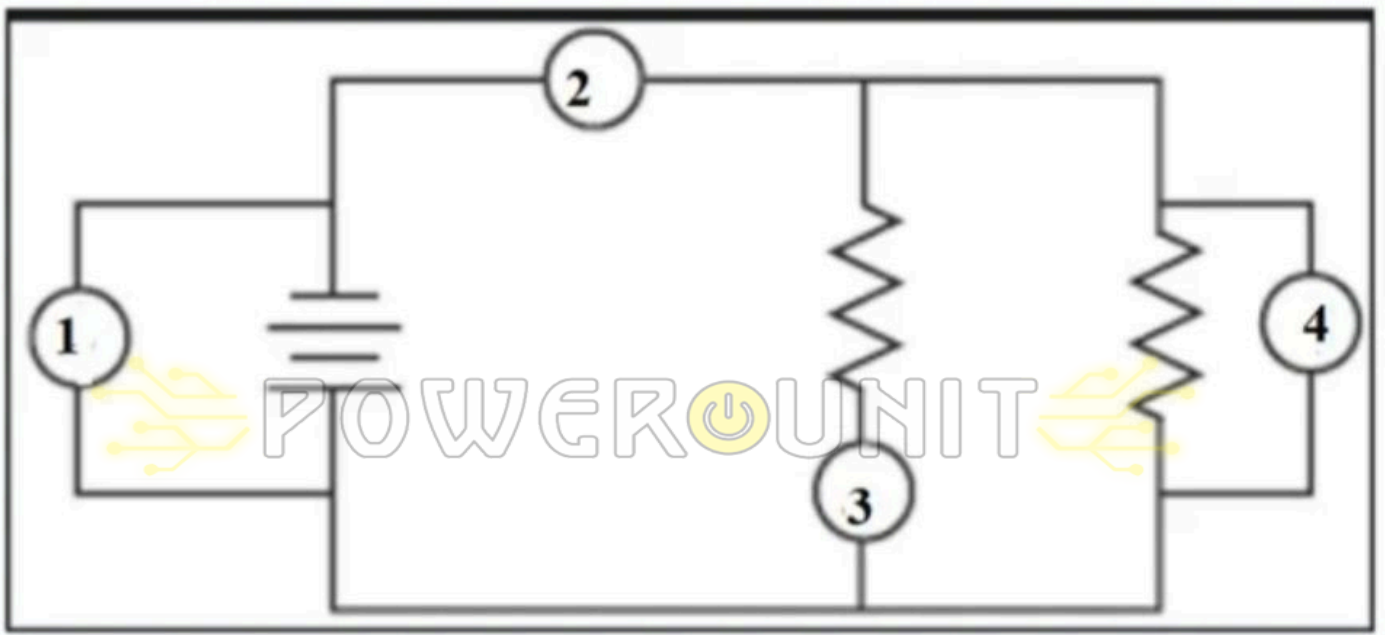
**C**

6

You are asked to connect the following circuit in the lab, to connect it correctly: \*  
(2 Points)



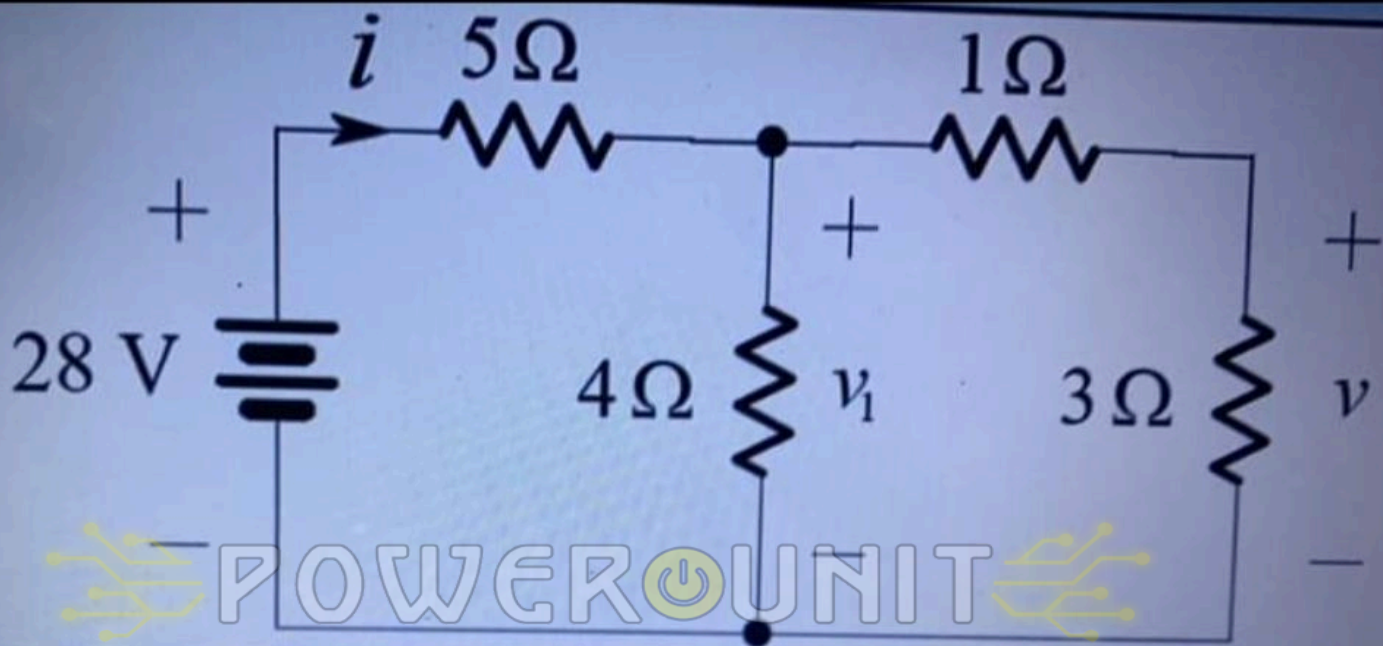- B. Device 2 and 4 are ammeters., 1 and 3 are voltmeters
- None of these.
- B. Device 2 and 3 are ammeters., 1 and 4 are voltmeters
- B. Device 1 and 4 are ammeters., 2 and 3 are voltmeters
- Both A and C are correct



- None of these
- A. The voltage across 4 ohm is higher than the voltage of 5 ohm across R1
- B. The current through 4 ohm is higher than the current through 3 ohm
- Both A and C
- C. The current through 4 ohm is equal to the current through 3 ohm

image, if you want to generate a square wave with 300 Hz, which bottoms you have to press \*  
(2 Points)



C with 4

B with 4

C, with 2


A, with 1

A with 4

For RLC parallel circuit with phasor diagram as shown in the figure, which of the following statements is correct?

\*

(2 Points)

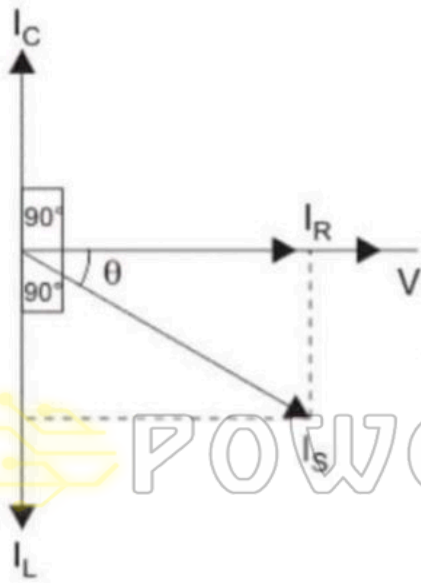

A.  $I_s = (I_c - I_L) + I_R$

B.  $I_s = (I_L - I_c) + I_R$

C.  $I_s = (I_R - I_L) + I_c$

D.  $I_s = (I_c - I_R) + I_L$

E. A and B are correct

B

A

E


C

D

(2 Points)

A series RLC circuit has  $R = 100 \Omega$ ,  $L = 1.25 \text{ H}$ ,  $C = 3.50 \mu\text{F}$ .  
It is connected to an AC source

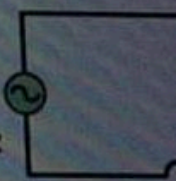$V_s = 150 \text{ V}$   
 $f = 60.0 \text{ Hz}$




- None of above
- 1529.92
- 303.92
- 1229
- 100


POWERUNIT 



11

For the series RLC circuit shown, what is the magnitude value of the current \*   
(2 Points)

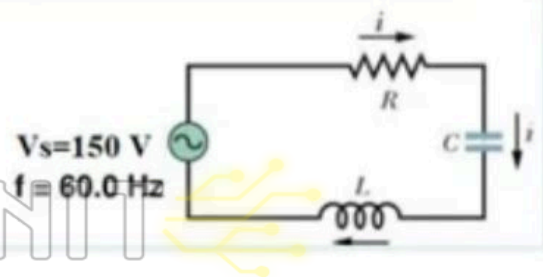A series RLC circuit has  $R = 100 \Omega$ ,  $L = 1.25 \text{ H}$ ,  $C = 3.50 \mu\text{F}$ .  
It is connected to an AC source




- None of above
- 0.49 A
- 4.9 A
- 0.15 A
- 1.5 A

12

For the series RLC circuit shown, what is the phase angle between the current and the voltage in (degree) \*  
(2 Points)

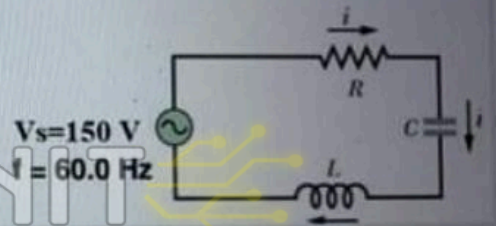A series RLC circuit has  $R = 100 \Omega$ ,  $L = 1.25 \text{ H}$ ,  $C = 3.50 \mu\text{F}$ .  
It is connected to an AC source



- 8.72
- 7.08
- 70.8
- 8.72
- None of above

For series R-L-C circuit at resonant frequency: \*  
(2 Points)

C and D are correct

A. The impedance  $Z$  is totally real


B.  $I$  is minimum and the voltage is maximum

C.  $Z$  is imaginary, the power factor is equal one

A and D are correct

D.  $I$  is maximum, and the Power is maximum


14

For parallel R-L circuit: \*   
(2 Points)

- As the frequency increases,  $X_L$  decreases
- $V$  lag  $I$
- As the frequency increases, the current decreases
- As the frequency increases,  $R$  decreases
- None of these

In the Figure shown, if  $i = \cos 100t$  and  $v = \sin 100t$ , the element is: \*

(2 Points)

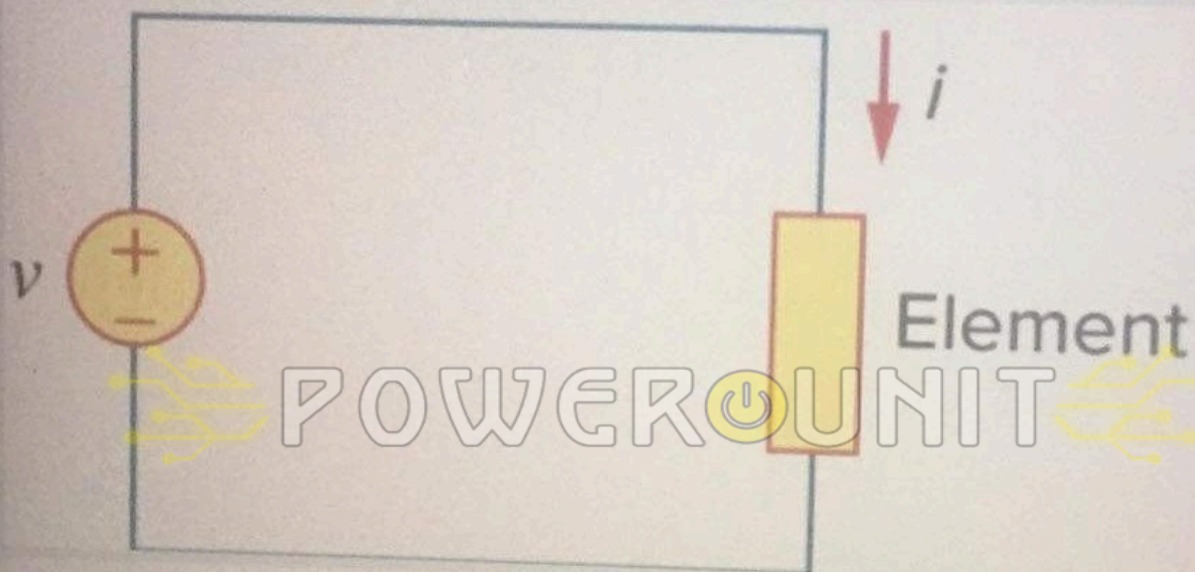

- a diode
- a capacitor
- an inductor
- a resistor
- None of these

16

A 10-H inductor changes its current by 3A in 0.2 s. The voltage produced at the terminals of the inductor is: \*

(2 Points)

- 3 V
- 1.2 V
- 150 V
- None of these
- 74 V
- 6.888 V

POWERUNIT

17

In the case of a parallel R-C circuit, the source current \_\_\_\_\_ the source voltage. \*

17

In the case of a parallel R-C circuit, the source current ..... the source voltage. \*  
(2 Points)

- None of these
- Lags
- Leads
- Remains in phase with

POWERUNIT

19

As frequency increases, what of the following statements is true? \*  
(2 Points)

- both series and parallel RC impedance decrease
- None of these
- series RC impedance decreases and parallel RC impedance increases
- series RC impedance increases and parallel RC impedance decreases
- both series and parallel RC impedance increase



20

The voltage  $v(t)$  expression is: \*

(2 Points)

- $2 \cos\left(\frac{\pi}{8}\right) V$
- $2 \sin\left(\frac{\pi}{2t}\right) V$
- $\cos(500\pi t) V$
- $\cos\left(\pi t - \frac{\pi}{4}\right) V$
- $2 \cos\left(500\pi t - \frac{\pi}{4}\right) V$

21

The impedance  $Z^*$   
(2 Points)

$0.04 - j0.72 \Omega$

$0.353 + j0.353 \Omega$

$0.255 - j0.54 \Omega$

$0.353 + j0.64 \Omega$

None of these

$41.45 \Omega$

$1.41 + j1.41 \Omega$

$1.41 - j1.41 \Omega$