

# GENERAL CIRCUITS

DR. SEREEN  
ALTHAHER

DONE BY  
DANA GHARABALLY

## Introduction:

\* Components of electric circuits:

① Source → voltage source like batteries.  
→ current source

② load → R (Resistor)  
→ L (Inductors)  
→ C (Capacitor)

③ Interconnection (wires) : to connect the source with the load.

\* The main unit to generate electricity is the Charge.

\* Electron is the smallest charge ( $1.602 \times 10^{-19} \text{ C}$ ).

\* Current: is the rate of change of charge. value  
direction.

$$i = \frac{dq}{dt}$$

$$\Rightarrow dq = i \cdot dt$$

$$\text{Coulomb} = \text{Ampere} \cdot \text{second}$$

$$[C = A \cdot s]$$

خلال كل ثانية يتحرك التيار في اتجاه

دوخذ القيمة والإشارة للتيار

كما



Note

\* Types of currents:

① Direct current (DC):



② Alternating current (AC): #periodic#

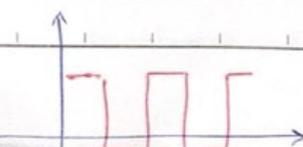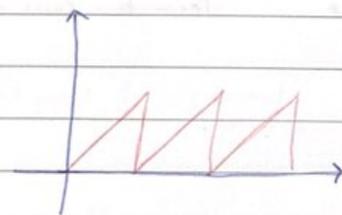

\* Voltage :   
 - value   
 - polarity (التيار موجب والسالب)



the energy required to move a unit charge through a circuit element.

\* The source   
 - (Current) source, it is current source   
 - (Voltage) source, it is voltage source

\* The voltage doesn't change with time / And must be between two points.


$$V = \frac{dW}{dq}$$

started with a positive  $\leftarrow$

$$V_{ab} = V_a - V_b$$



$$= (V_a - V_n) - (V_b - V_n)$$

Reference  $\leftarrow$   
= zero

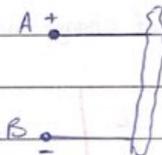

Note:  
 Be careful to the polarity.

Ex:

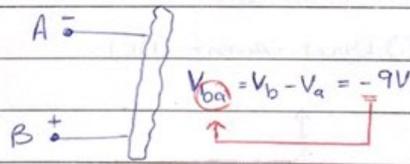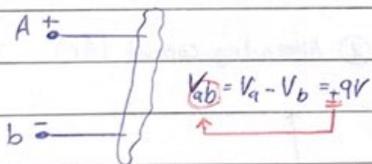

These two cases are equivalent ( $V_a > V_b$ )

\* شو با توجه به قطب الجهد   
 قطب (-) و (+) با هم   
 قطب polarity معاكس

\* Power:

$$P = \frac{dW}{dt} = \frac{dW}{dq} \times \frac{dq}{dt}$$

$\downarrow$  voltage       $\downarrow$  current

\* When there is more than one element,  $[\sum P = 0]$

(principle of conservation of the power).


$P = V \cdot i$

\* Elements in a circuit:

→ passive (load) / absorb or consume  $\Rightarrow$  it doesn't give power by itself.

→ active (source) / deliver or generate  $\Rightarrow$  it gives.

\* Passive sign convention:

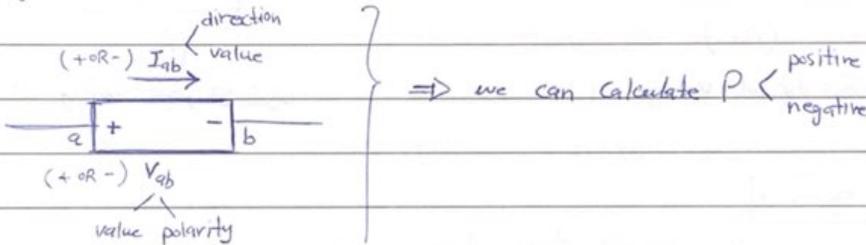


→ if (I) enters (+)

$$P = \pm V_{ab} \cdot I_{ab}$$

→ if (I) enters (-)

If  $P \geq 0 \Rightarrow$  absorb OR consume      #  $P_{absorbed} = P_{generated}$

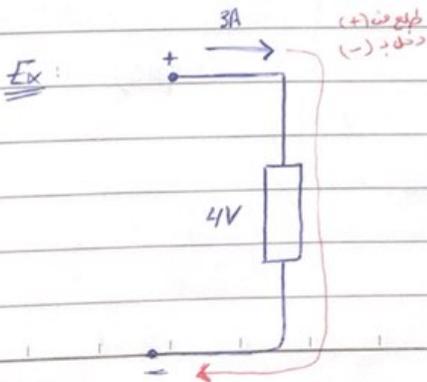$P < 0 \Rightarrow$  deliver OR generate.




$$P = \pm V_{ab} I_{ab}$$

$$= - (4)(3) = -12 \text{ watt (supply power)}$$


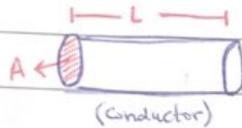
### \* Resistance:

A physical property or ability to resist current.



$$R \propto \frac{L}{A}$$

$$\Rightarrow R = \rho \frac{L}{A} \quad (\Omega)$$

↳ Constant = resistivity ( $\rho$ )

The symbol is:



### \* Ohm's law: ( $R/I/V$ )

$$I = \frac{V}{R}$$

↳ assume it is constant

so, the voltage across a resistor is directly proportional

to the current  $i$  flowing through the resistor. (linear)

↳ The slope =  $R$

The instantaneous power dissipated in a resistor:

$$P = Vi = \frac{V^2}{R} = Ri^2 \geq 0$$

$\Rightarrow$  always positive

always absorb power.

### \* Conductance:

is the ability of an element to conduct current.

$$G = \frac{1}{R}$$

$\Rightarrow$  measured in siemens ( $S$ ) or mho ( $\Omega^{-1}$ )

conductivity.  $\leftarrow$

### \* Short and Open circuit:

• short circuit:

$$R=0 \Rightarrow V=0$$

This doesn't mean that

there is NO current.


• Open circuit:

$$R=\infty \Rightarrow i=0 \text{ (no current)}$$

But there is voltage. ( $V$ ).


\* Series and parallel :

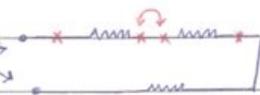• Series : carry the same current *not connected*



$$R_{eq} = R_1 + R_2 + R_3$$

• parallel : have the same voltage

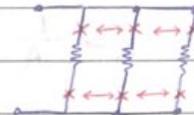


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

OR  
for 2 resistances

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

\* KCL :

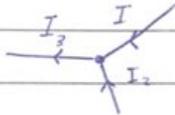

$$I_3 = I_1 + I_2$$

$$\boxed{\sum I_{in} = \sum I_{out}}$$

\* KVL : Sum of voltage drops = Sum of voltage rises.

$$\sum V = \text{Zero}$$


loop  $\Rightarrow$  direction (clockwise OR counter clockwise)

If it enters (+)  $\Rightarrow$  (+)

" " " (-)  $\Rightarrow$  (-)


$$-V_1 + V_2 + V_3 - V_4 = 0$$

$$-V_1 + R_1 I + R_2 I - V_4 = 0$$

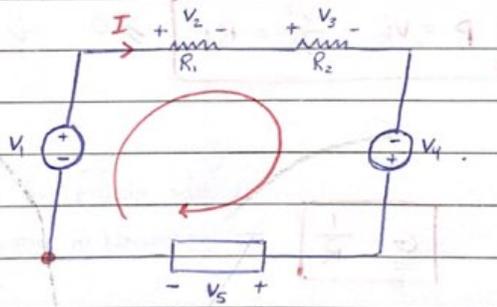

\* Connection of Resistance:

- Equivalent Resistance:

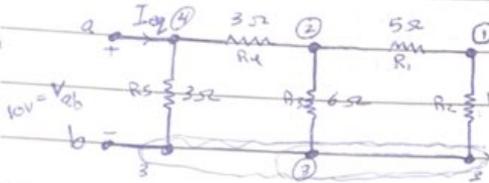

Ex:

Calculate Req between a and b:

$(R_1, R_2) \rightarrow$  series


$$R_1 + R_2 = 5 + 1 = 6 \Omega$$

$(R_2, R_3) \rightarrow$  parallel

$$\frac{(6)(6)}{6+6} = \frac{36}{12} = 3 \Omega$$

$$3 + 3 = 6 \Omega$$


(note: final result is 3Ω)

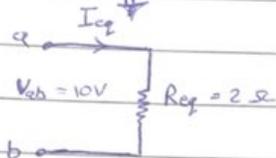


$$V_{ab} = +IR$$

$$10 = I(2)$$


$$I = 5A$$

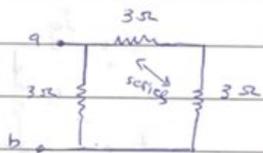
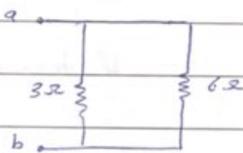
$$R_{eq} = \frac{(3)(6)}{3+6} = \frac{18}{9} = 2 \Omega$$




\* Past paper 2019: (First) 7KΩ

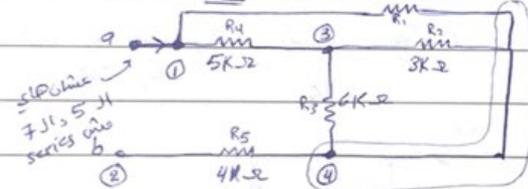

Calculate Req seen from a & b.

$(R_2, R_3) \rightarrow$  parallel


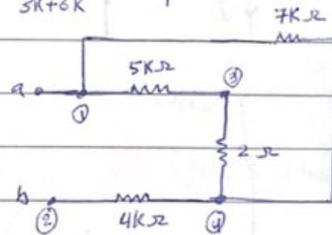
$$\frac{(3K)(6K)}{3K+6K} = \frac{18}{9} = 2 \Omega$$



$(5K, 2K) \rightarrow$  series.

$(7K, 7K) \rightarrow$  parallel

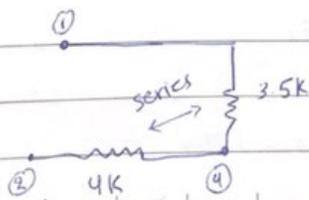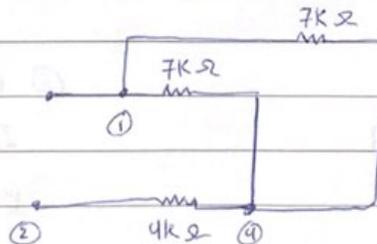
$$\frac{(7K)(7K)}{7+7} = \frac{49}{14} = 3.5$$



$$R_{eq} = 3.5K + 4K = 7.5 K \Omega$$


⊛ Voltage division and Current division:

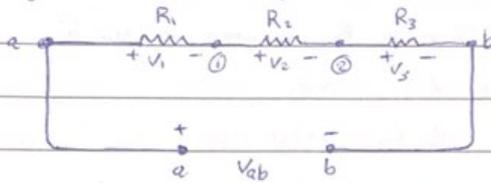- Voltage division  $\Rightarrow$  (Series)



$$V_1 = \left( \frac{V_{ab}}{R_1 + R_2 + R_3} \right) R_1$$

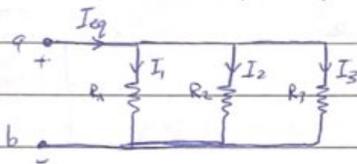
- Current division  $\Rightarrow$  (parallel)




$$I_1 = I_{eq} \left( \frac{R_{eq}}{R_1} \right)$$

If there is just 2 resistances:
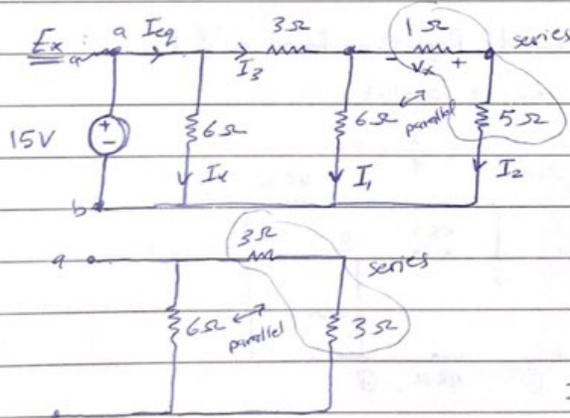
$$I_1 = I_{eq} \left( \frac{R_2}{R_1 + R_2} \right) \quad I_2 = I_{eq} \left( \frac{R_1}{R_1 + R_2} \right)$$



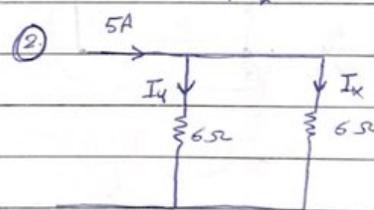Calculate: 1.  $I_{eq}$  2.  $I_1$  3. power absorbed by  $5\Omega$   
4.  $V_x$



$$I_x = \frac{(5)(6)}{12} = 2.5A$$


$$I_1 = \frac{2.5(6)}{12} = 1.25A$$

①  $R_{eq} = 3\Omega$   
 $V_{ab} = 15V$   
 $I_{eq} = \frac{15}{3} = 5A$   
 (circled)

③  $P = I_1^2 R =$   
 $I_2 = \frac{2.5(6)}{12} = 1.25A$   
 $P = (1.25)^2 (5)$


④  $V_x = + I_2 \cdot 1 = -1.25V$

past paper

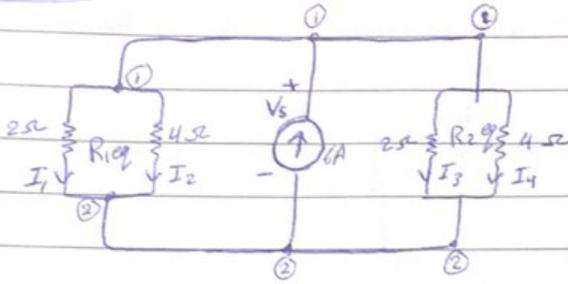

① Find  $I_1$

② Power generated by the current source

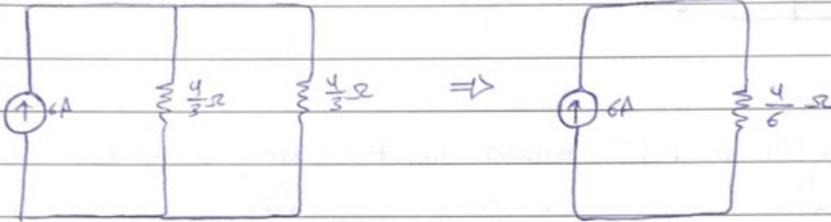

①  $I_1 = \frac{6(4/6)}{2} = 2A$

②  $P = -VI$   
 $= -V_s(6)$


$V_s = \frac{4}{6} \times 6 = 4 \text{ volts}$

$= -(4)(6) = -24 \text{ watts}$


$\bar{I} \rightarrow$  generate power.

\* Wye-Delta Transformations:

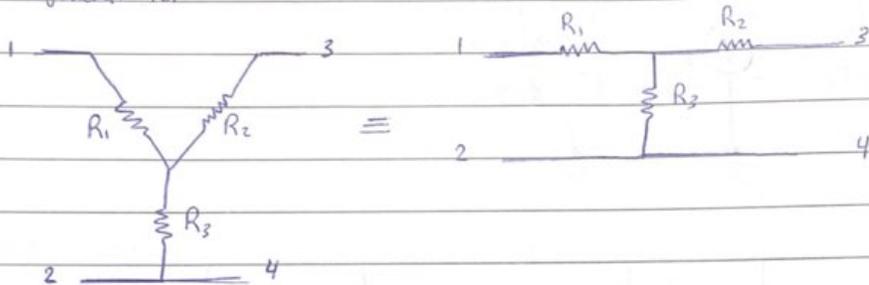- A wye (Y) or tee (T) network is a three-terminal with the following general form:



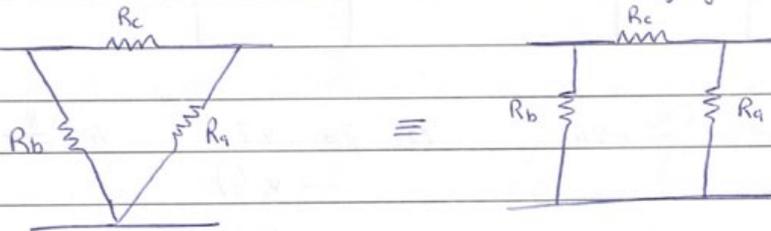- The delta ( $\Delta$ ) or pi ( $\Pi$ ) network has the following general form:




\* Delta-Wye Conversion:

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$
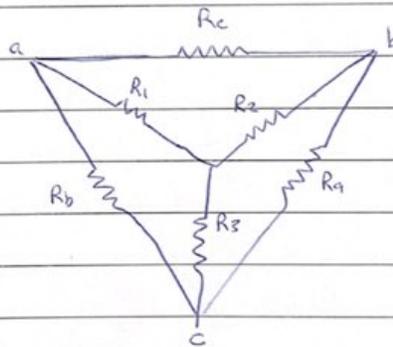
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



\* Wye-Delta Conversion:

$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

\* Y and  $\Delta$  are said to be balanced when:


$$R_1 = R_2 = R_3 = R_Y \text{ and } R_a = R_b = R_c = R_\Delta$$

$$R_Y = \frac{R_\Delta}{3} \text{ and } R_\Delta = 3R_Y$$

Always:  $R_a > R_Y$
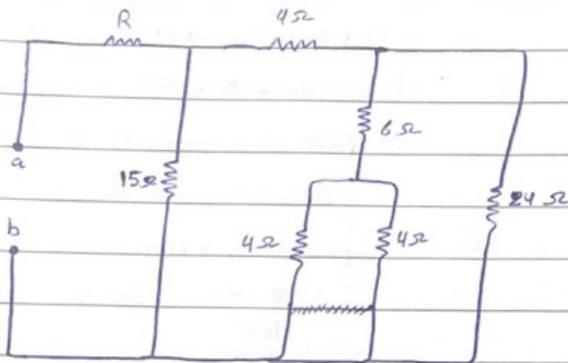
## Solving problems:

- ① In the circuit a figure below, if  $R = 1 \Omega$ , Find  $R_{eq}$  seen from ~~open~~ the source open circuit:



(4, 4) → ~~series~~ parallel

$$\frac{2(4)(4)}{8} = 2 \Omega$$

(6, 4) → series

$$6 + 4 = 10 \Omega$$

(8, 2) → series

$$6 + 2 = 8 \Omega$$

(10, 15) → parallel

$$\frac{(10)(15)}{25} = 6 \Omega$$

(8, 24) → parallel


$$\frac{(8)(24)}{32} = 6 \Omega$$

(6, 1) → series

$$R_{eq} = 7 \Omega$$

② (31/2)

Simplify the circuit:

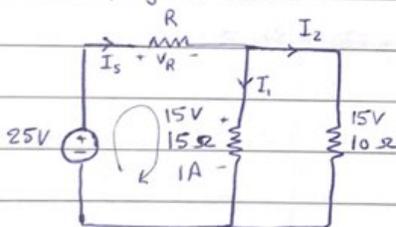

$$P_{15\Omega} = RI^2 \Rightarrow I_1 = \sqrt{\frac{P}{R}} = \sqrt{\frac{15}{15}} = 1A$$

$$V_{15\Omega} = RI_1 = (15)(1) = 15 \text{ Volts}$$

Because (10, 15) are parallel, they have the same voltage.

$$V_{10\Omega} = V_{15\Omega} = 15V$$

$$I_{10\Omega} = \frac{V}{R} = \frac{15}{10} = 1.5A$$

$$I_s = I_1 + I_2 = 1 + 1.5 = 2.5A$$

$$V_R = ? \Rightarrow \text{based on KVL}$$

$$-25 + V_R + 15 = 0 \Rightarrow V_R = 10 \text{ Volts}$$

$$R = \frac{V}{I} = \frac{10}{2.5} = 4 \Omega$$

③  $\frac{34}{\text{Ch. 2}}$

• Seen from ab if cd are open:

$(360, 540) \rightarrow \text{series}$

$$360 + 540 = 900 \Omega$$

$(180, 540) \rightarrow \text{series}$

$$180 + 540 = 720 \Omega$$

$(900, 720) \rightarrow \text{parallel}$

$$\frac{(900)(720)}{1620} = 400 \Omega$$

• Seen from cd if ab are open:

$(360, 180) \rightarrow \text{series}$

$$360 + 180 = 540 \Omega$$

$(540, 540) \rightarrow \text{series}$

$$540 + 540 = 1080 \Omega$$

$(540, 1080) \rightarrow \text{parallel}$

$$\frac{(540)(1080)}{1620} = 360 \Omega$$

• Seen from cd if ab short circuit:

$(360, 540) \rightarrow \text{parallel}$

$$\frac{(360)(540)}{900} = 216 \Omega$$

$(180, 540) \rightarrow \text{parallel}$

$$\frac{(180)(540)}{720} = 135 \Omega$$

$(216, 135) \rightarrow \text{series}$

$$216 + 135 = 351 \Omega$$

• Seen from ab if cd short circuit:

$(360, 180) \rightarrow \text{parallel}$

$$\frac{(360)(180)}{540} = 120 \Omega$$

$(540, 540) \rightarrow \text{parallel}$

$$\frac{(540)(540)}{1080} = 270 \Omega$$

$(120, 270) \rightarrow \text{series}$


$$120 + 270 = 390 \Omega$$

④ past paper: If  $I_s = 1 \text{ A}$ , then answer the following questions:

a. The value of  $i$

b. The value of  $V$

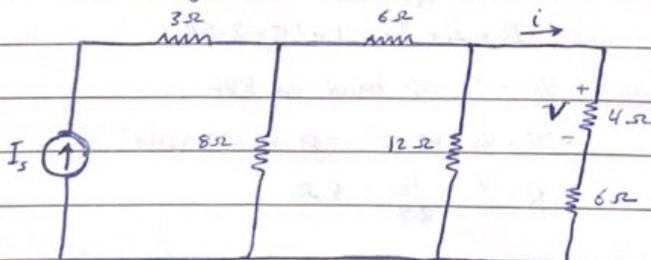c. The power delivered by the current source.



(4,6) → series


$$4+6 = 10 \Omega$$

(10, 12) → parallel

$$\frac{(10)(12)}{22} = 5.5 \Omega$$


(5.5, 6) → series

$$5.5+6 = 11.5 \Omega$$

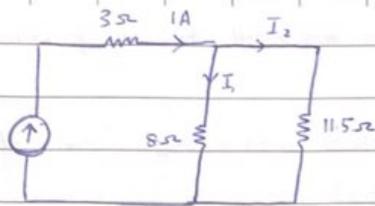

$I_2$  by current division:
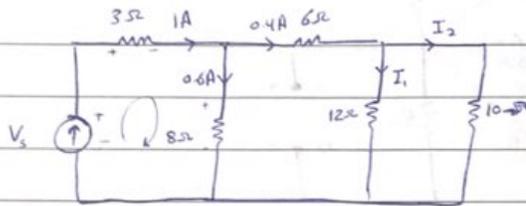
$$I_2 = 1 \left( \frac{8}{8+11.5} \right) = \frac{8}{19.5} = 0.4A$$



$I_2$  by current division:

$$I_2 = 0.4 \left( \frac{12}{12+10} \right) = 0.2A$$

Ⓐ  $V = +RI = +(4)(0.2) = +0.8 \text{ Volts}$

Ⓒ  $P = -VI$


$V_s$  by KVL  $\Rightarrow -V_s + 3 \times 1 + 8 \times 0.6 = 0$

$V_s = 7.8 \text{ volts}$

$P = -(7.8)(1) = -7.8 \text{ watt}$

⑤ If  $V_1 = 3V$ , then answer the following questions:

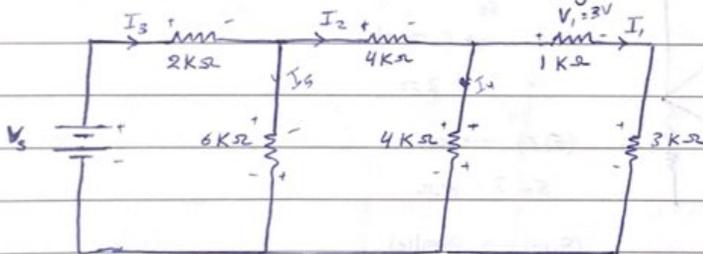$I_1, I_2, I_3, V_s$  and the power delivered by the source.



$R_1 = 1k\Omega$   
 $V_1 = 3V$   
 $\Rightarrow I_1 = \frac{V_1}{R_1} = \frac{3}{1k} = 3mA$

by KVL

$$-V_s + (2k)(12mA) + (6k)(6mA) = 0$$

$I_4 = I_1 = 3mA$

$V_s = 24 + 36 = 60 \text{ volts}$

$I_2 = I_1 + I_4 = 3mA + 3mA = 6mA$

$I_2 = I_5 = 6mA$

P delivered by the source:


$I_3 = I_2 + I_5 = 6mA + 6mA = 12mA$

$P = -VI = -(60)(12mA) = -720 \text{ mW}$

② If  $V_s = 3V$  and  $R = 2\Omega$ , then answer the following questions:

a. The value of  $i$

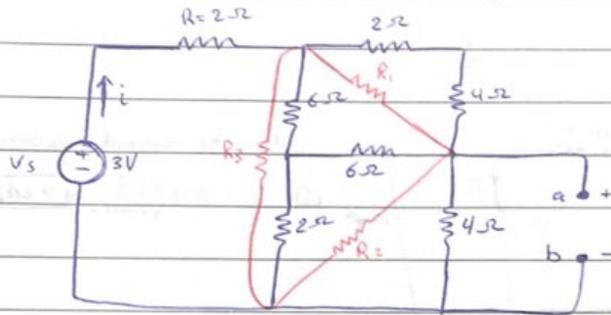
b. If the voltage source is replaced with a short circuit, then the equivalent resistance seen from a and b in (ohms) is:



$$R_1 = \frac{(6)(6) + (6)(2) + (2)(6)}{2} = \frac{60}{2} = 30\Omega$$

$$R_2 = \frac{(6)(6) + (6)(2) + (2)(6)}{6} = \frac{60}{6} = 10\Omega$$
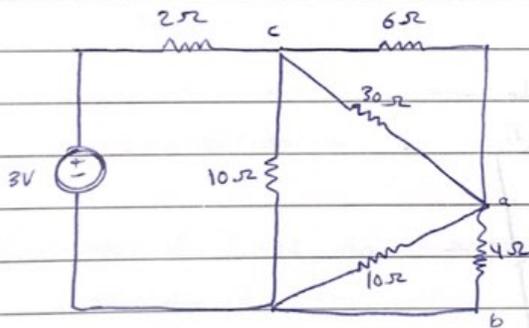
$$R_3 = \frac{(6)(6) + (6)(2) + (2)(6)}{6} = \frac{60}{6} = 10\Omega$$



$(6, 30) \rightarrow$  parallel

$$\frac{(6)(30)}{36} = 5\Omega$$

$(4, 10) \rightarrow$  parallel

$$\frac{(4)(10)}{14} = 3\Omega$$

$(5, 3) \rightarrow$  series

$$5 + 3 = 8\Omega$$

$(8, 10) \rightarrow$  parallel

$$\frac{(8)(10)}{18} = 4\Omega$$


$(4, 2) \rightarrow$  series

$$4 + 2 = 6\Omega \quad R_{eq}$$

$$i = \frac{V}{R} = \frac{3}{6} = 0.5A$$


⑦ If  $V_s = 40V$  find the voltage across  $R = 12K\Omega$

~~90??~~ 6.7 Volts

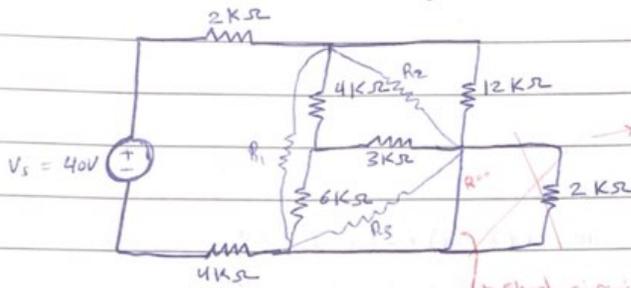


ignore all that part because the short circuit #
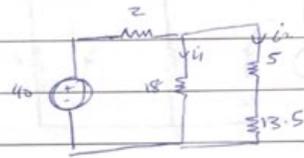
$$R_1 = \frac{(4)(3) + (4)(6) + (6)(3)}{3} = \frac{54}{3} = 18K\Omega$$


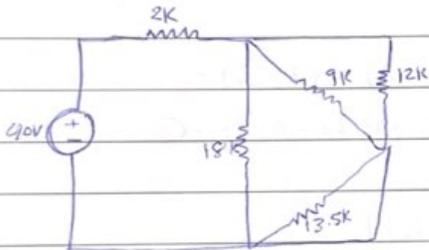
$$R_2 = \frac{54}{6} = 9K\Omega \quad R_3 = \frac{54}{4} = 13.5K\Omega$$



$$12 // 9 \Rightarrow \frac{(12)(9)}{21} = 5K\Omega$$

$$I_2 = \left( \frac{19}{36.5} \right) 3.6 = 1.78A$$

$$V = (5)(1.78) = 8.9V$$

$$5 + 13.5 = 18.5K\Omega$$


$$18.5 // 18 \Rightarrow \frac{(18.5)(18)}{36.5} = 9K\Omega$$

$$9 + 2 = 11K\Omega$$

$$I_{in} = \frac{V}{R} = \frac{40}{11} = 3.6A$$

⑧ Find  $R_{in} = ?$

~~6.7??~~ 7.5

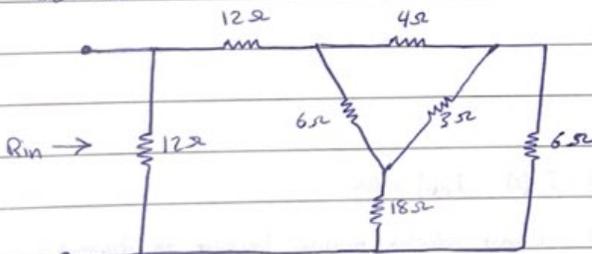


# Chapter 3:

## \* Mesh analysis:

- Mesh loop

- Mesh current  $\Rightarrow$  clockwise

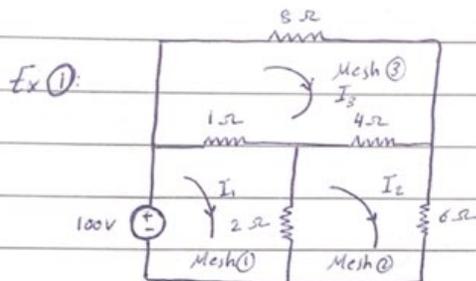

Mesh 1:

$$-100 + 1(I_1 - I_3) + 2(I_1 - I_2) = 0$$

$$100 = 3I_1 - 2I_2 - I_3 \quad \dots \textcircled{1}$$

Mesh 2:

$$4(I_2 - I_3) + 6I_2 + 2(I_2 - I_1) = 0$$

$$-2I_1 + 12I_2 - 4I_3 = 0 \quad \dots \textcircled{2}$$

Mesh 3:

$$8I_3 + 4(I_3 - I_2) + 1(I_3 - I_1) = 0$$

$$-I_1 - 4I_2 + 13I_3 = 0 \quad \dots \textcircled{3}$$

Mesh 1:

$$+ I_1(3) - I_2(2) - I_3(1) = 100$$

OR

Mesh 3:

$$8I_3 + 4(I_3 - I_2) + 1(I_3 - I_1) = 0$$

$$-I_1 - 4I_2 + 13I_3 = 0 \quad \dots \textcircled{3}$$

Mesh 2:

$$+ I_2(6) - I_1(2) - I_3(4) = 0$$

$$\ast V_x = -I_x(6)$$


Mesh 3:

$$+ I_3(13) - I_1(1) - I_2(4) = 0$$

$$= -I_1(6)$$

$$\ast P_{2\Omega} = I^2(2) = (I_1 - I_2)^2(2)$$

## \* If there is current source:

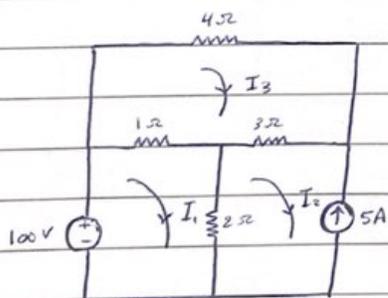

Mesh 1:

$$+ I_1(3) - I_2(2) - I_3(1) = 100$$


Mesh 2: Cannot calculate mesh 2 because the current source

$$I_2 = -5A \Rightarrow (\text{c.s. source})$$

Mesh 3:

$$+ I_3(8) - I_2(3) - I_1(1) = 0$$

Ex ②:

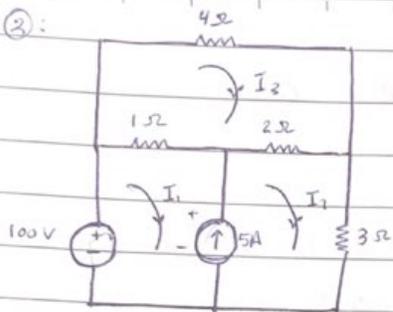

Cannot calculate from Mesh ① and Mesh ②

because the current source

$$5 = I_2 - I_1$$

Mesh ③:

$$+ I_2(7) - I_1(1) = 0$$

OR (outer loop)


$$-100 + (I_1 - I_2) + 2(I_2 - I_3) + 3I_3 = 0$$

$$-100 + 4I_3 + 3I_2 = 0$$

$$P_{CS} = \pm V \cdot I = -5V_x$$

$$\xrightarrow{\text{KVL}} -100 + (I_1 - I_2) + V_x = 0$$

⊗ Past paper:

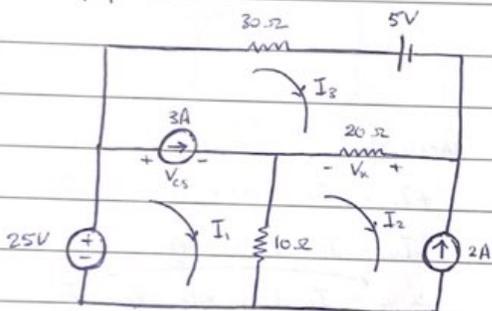

$$I_2 = -2A$$

$$3 = I_1 - I_3$$

$$-25 + 30I_2 + 5 + 20(I_3 - I_2) + 10(I_2 - I_3) = 0$$


$$\xrightarrow{\text{KVL}} I_3 = \frac{-70}{60} = -\frac{7}{6} \Rightarrow I_1 = 3 - \frac{7}{6}$$

$$V_x = RI = -(20)(I_x) = -(20)(I_2 - I_3)$$


$$P_{3A(CS)} = +3(V_{CS})$$

$$\xrightarrow{\text{KVL}} -25 + V_{CS} + 10(I_1 - I_2) = 0$$

⊗ Dependent sources:

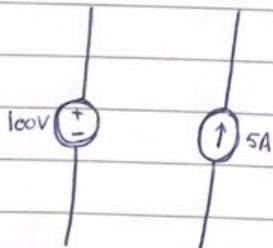


(Independent sources)

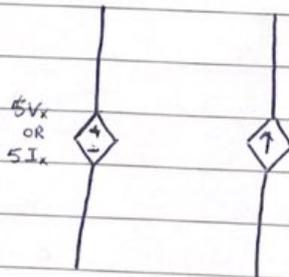

(dependent sources)

\* Past paper:

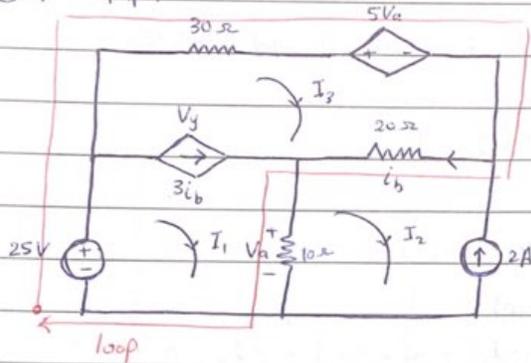

$$I_2 = -2 \text{ A} \dots \textcircled{1}$$

$$3i_b = I_1 - I_2$$

$$i_b = I_3 - I_2$$

$$3(I_3 - I_2) = I_1 - I_2$$

$$4I_3 - 3I_2 - I_1 = 0$$

$$4I_3 - I_1 = -6 \dots \textcircled{2}$$


$$\rightarrow -25 + 30I_2 + 5V_a + 20(I_3 - I_2) + 10(I_1 - I_2) = 0$$

$$V_a = + (I_1 - I_2) 10$$

$$p = + V_y (3i_b)$$

$$\leftarrow \bar{I} \rightarrow i_b = I_3 - I_2$$

\* Past paper:

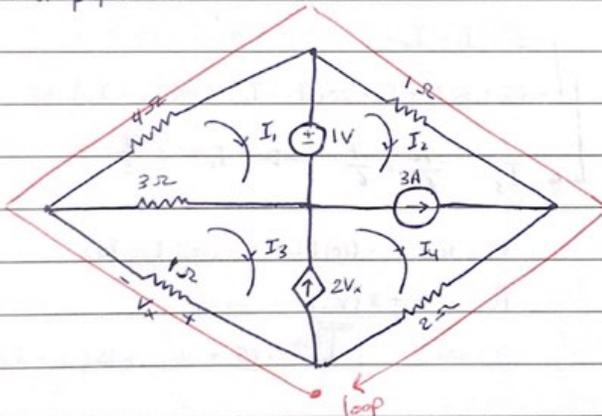

Mesh (1):

$$7I_1 - 3I_2 = 1 \dots \textcircled{1}$$

$$I_4 - I_2 = 3 \dots \textcircled{2}$$

$$2V_x = I_4 - I_2 \Rightarrow V_x = +I_2$$


$$2I_3 = I_4 - I_2$$

$$I_4 - 3I_2 = 0 \dots \textcircled{3}$$

$$I_3 - 4I_1 + I_2 + 2I_4 = 0 \dots \textcircled{4}$$



Example 2:

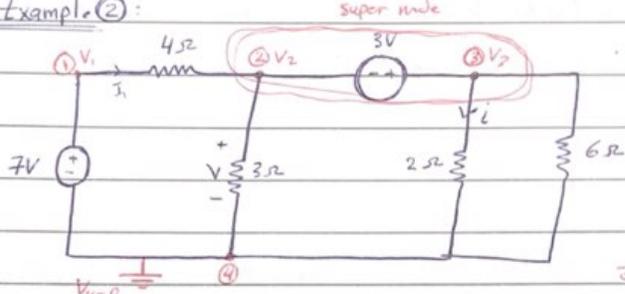

mesh لا يفيق  
ناتج من قبل بال  
super node لا يفيق (super node) لا  
voltage source  
ناتج من قبل بال (voltage source)  
ناتج من قبل بال (voltage source)  
ناتج من قبل بال (voltage source)  
super node لا يفيق

node 1:

$$V_1 - V_4 = 7 \Rightarrow V_1 - 0 = 7 \Rightarrow V_1 = 7V$$

node 2:

$$V_2 - V_2 = 3 \dots \textcircled{1} \quad V_2 = -0.2V$$

node 3:

$$-V_1 \left(\frac{1}{4}\right) + V_2 \left(\frac{1}{4} + \frac{1}{3}\right) + i_V = \text{zero} \quad V_3 = 2.8V$$

node 4:

$$i_V = +V_3 \left(\frac{1}{2} + \frac{1}{6}\right)$$

$$-\frac{V_1}{4} + V_2 \left(\frac{1}{4} + \frac{1}{3}\right) + V_3 \left(\frac{1}{2} + \frac{1}{6}\right) = \text{zero} \dots \textcircled{2}$$

$$I_1 = \frac{V_1 - V_2}{R} = \frac{7 - (-0.2)}{4} = 1.8A$$

$$V = V_2 - V_4 = -0.2 - 0 = -0.2V$$


$$P_{7V} = \pm VI = \pm 7I = -7(1.8) = -12.6 \text{ watt (generated)}$$

$$I = \frac{V_3 - V_4}{R} = \frac{2.8 - 0}{2} = 1.4A$$

$$P_{3V} = -I_V(3) = -(1.4)(3) = 5.7 \text{ watt}$$

by nodal (KCL)  
 $i_V \text{ @ node 2} \Rightarrow i_V + V_2 \left(\frac{1}{4} + \frac{1}{3}\right) - \frac{V_1}{4} = 0$   
 $i_V = 1.9A$

Example 3:

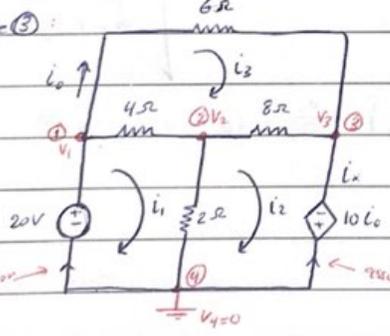

node 2:

$$-V_1 \left(\frac{1}{2}\right) + V_2 \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{2}\right) - V_3 \left(\frac{1}{8}\right) = \text{zero}$$

$$-\frac{V_1}{2} + V_2 \left(\frac{3}{8}\right) - \frac{V_3}{8} = \text{zero} \dots \textcircled{1}$$

$$V_1 - V_4 = 20 \Rightarrow V_1 = 20V$$

$$V_2 \left(\frac{3}{8}\right) - \frac{V_3}{8} = 10 \dots \textcircled{2}$$

$$10i_0 = V_4 - V_3 \Rightarrow -V_3 = 10i_0$$

$$V_2 \left(\frac{3}{8}\right) - \frac{5i_0}{8} = 10$$

$$V_2 = 18.6V$$

$$P_{\text{ind. source}} = -i_1(20) = (-4.65)(-20) = +93 \text{ watt}$$

KCL  $\rightarrow i_1 = V_1 \left(\frac{1}{4} + \frac{1}{2}\right) - V_2 \left(\frac{1}{4}\right) - V_3 \left(\frac{1}{2}\right)$   
 $i_1 = -4.65$

$$i_2 = \frac{V_1 - V_2}{R} = \frac{20 - 18.6}{6}$$

$$-V_2 = 10 \left(\frac{20 - V_2}{6}\right)$$

$$V_2 = 50V$$

$$P_{\text{dep. source}} = +(-i_2)(10i_0)$$

$$= +i_x(10i_0) \Rightarrow i_0 = \frac{V_1 - V_3}{6} = \frac{20 - 50}{6} = -5A$$

$$= (8.9)(10)(-5) \quad i_x \text{ by KCL} = V_3 \left(\frac{1}{2} + \frac{1}{2}\right) - V_2 \left(\frac{1}{8}\right) - V_1 \left(\frac{1}{2}\right)$$

$$= -445 \text{ watt}$$

$$i_x = 8.925A$$


\* Superposition:  $\Rightarrow$  ohm's law

$$V = IR \quad \xrightarrow{\substack{\text{directly} \\ \text{proportional (linear)}}} V \text{ and } I \text{ is proportional}$$

$\downarrow$   
constant

- Just on voltage and current, cannot apply it to calculate the power because it is not directly proportional with  $I$  ( $P = I^2 R$ ).

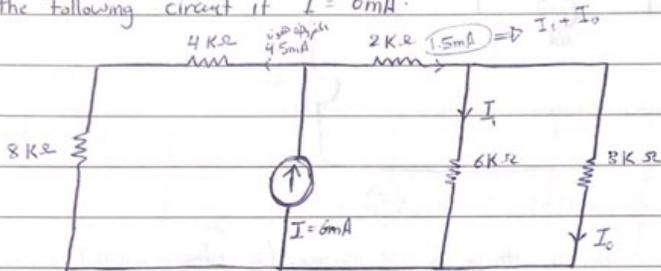Example: Use linearity and the assumption that  $I_0 = 1\text{mA}$  to compute the correct value of  $I_0$  in the following circuit if  $I = 6\text{mA}$ .




To prove the linearity. JUST

$$R = 3\text{k}\Omega \quad I_0 = 1\text{mA} \quad \Rightarrow \quad V_{3\text{k}\Omega} = RI = (3\text{k})(1\text{mA}) = 3\text{V}$$

$$V_{6\text{k}\Omega} = V_{3\text{k}\Omega} = 3\text{V} \quad \Rightarrow \text{parallel}$$

$$I_{6\text{k}\Omega} = \frac{V}{R} = \frac{3}{6\text{k}} = 0.5\text{mA} = I_1$$

\* Simplify the circuit:

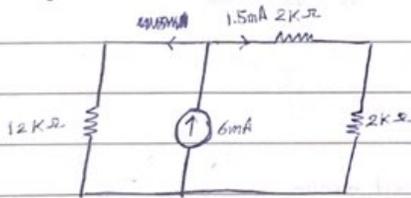

$$R = 4\text{k}\Omega \quad V = ? \quad \Rightarrow \quad V = (4\text{k})(1.5\text{mA}) = 6\text{V}$$



$$I = 1.5\text{mA}$$

المسألة هي ببساطة (6mA) في اليمين واليسار  
4kΩ في اليمين واليسار في اليمين

$$V_{2\text{k}\Omega} = 6\text{V}$$

$$I = \frac{V}{R} = \frac{6}{12\text{k}} = 0.5\text{mA}$$

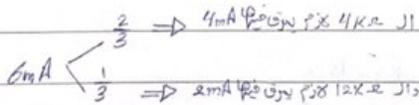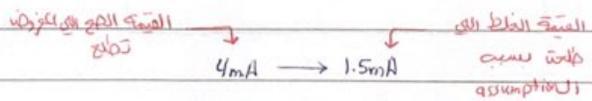(1/3) في اليمين واليسار في اليمين  
في اليمين واليسار في اليمين



المسألة هي ببساطة في اليمين واليسار في اليمين  
المسألة هي ببساطة في اليمين واليسار في اليمين

if  $I_0 = 1\text{mA} \Rightarrow I_2 = 1.5\text{mA}$  (wrong)

$$x = \frac{4}{1.5} = \frac{8}{3}$$

$I_0 = ? \Rightarrow I_2 = 4\text{mA}$

$\Rightarrow I_0 = \frac{8}{3}$


Superposition property:

• Turn off independent sources except one source

~~V~~  $\Rightarrow$  to kill the voltage source, replace it with a short circuit.

~~C~~  $\Rightarrow$  to kill the current source, replace it with an open circuit.


Example:

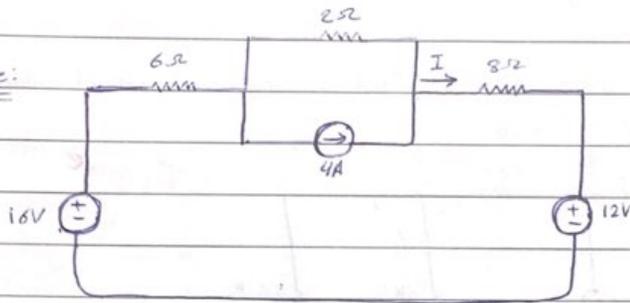

\* We will solve it 3 times because there is 3 sources (2 voltage and 1 current)

$\hookrightarrow$  Everytime we will kill 2 of these sources and keep the third one

# 1 (Keep 16V)

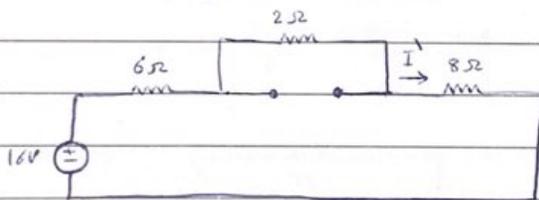


$$R_{eq} = 16 \Omega$$

$$V = 16V$$

$$I' = \frac{V}{R} = \frac{16}{16} = 1A$$


# 2 (Keep 4A)

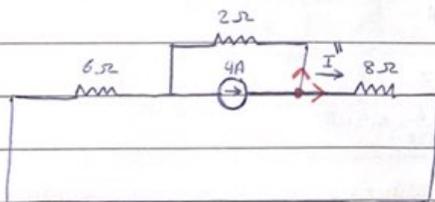

by current division:

$$I'' = 4 \left( \frac{2}{16} \right) = 0.5A$$

# 3 (Keep 12V)

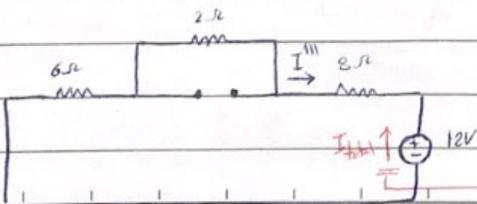


$$R_{eq} = 16 \Omega$$

$$I''' = \frac{-12}{16} = -\frac{3}{4} = -0.75A$$


$$I = 1 + 0.5 - 0.75 = 0.75A$$

\* Source transformation:

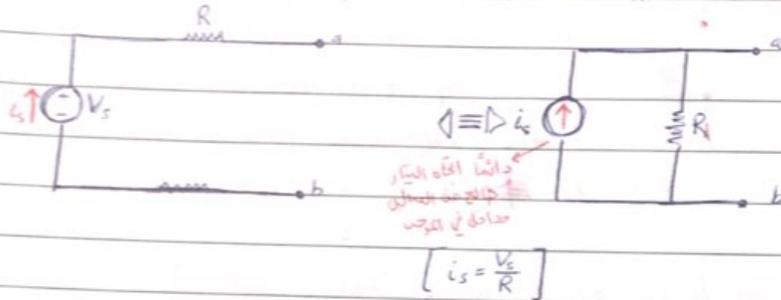↳ refers to the process of replacing a voltage source in series with a resistor R with a current source in parallel with the same resistor and vice versa.



Example:

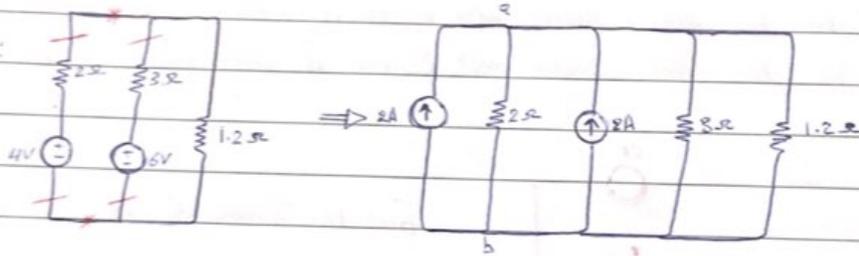


So,


(2, 3, 1.2) → parallel

$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{3} + \frac{1}{1.2} \Rightarrow R_p = 0.6 \Omega$$
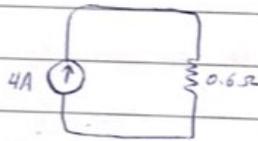
$$I_q = 2 + 2 = 4A \text{ (going in the same node)}$$



\* Thevenin Eq. CKL:

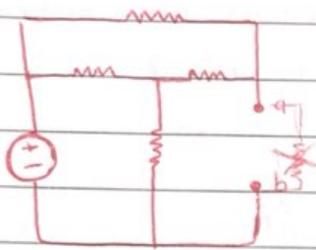

Find  $V_{th}$  seen from a b:


$\Rightarrow$  Remove all elements between a and b and keep it as open circuit and find  $V_{open\ circuit}$  which is  $V_{th}$ .

$R_{th} \Rightarrow$  Req seen from ab

\* We have to kill all the sources (must be independent)


- To kill the voltage source  $\Rightarrow$  Replace it with a short circuit
- To kill the current source  $\Rightarrow$  Replace it with an open circuit.

Ex:

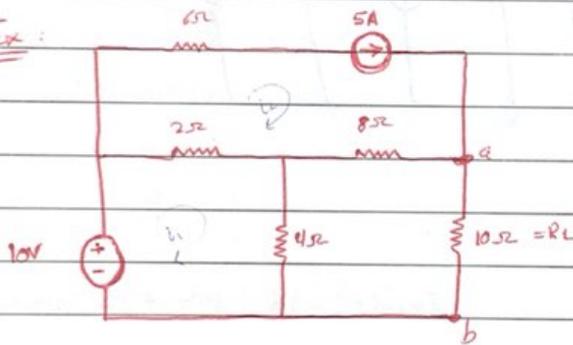

Find the Thevenin Eq CKL seen from ab:

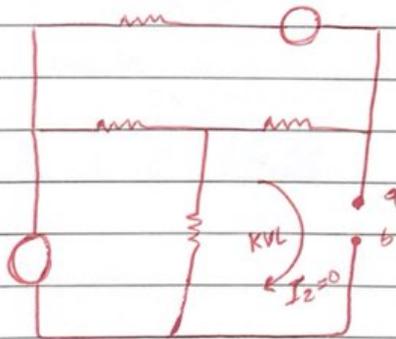\* Remove  $R_L$  and replace it with an open circuit:




$$10 = 6I_1 - 2(5) - 4(0) \Rightarrow I_1 = \frac{20}{6} A$$

$$8(0 - 5) + V_{oc} = 0$$


$$+ 4(I_2 - \frac{20}{6}) = 0$$

$$V_{oc} = 40 + \frac{80}{6} \approx 53 \text{ Volt}$$

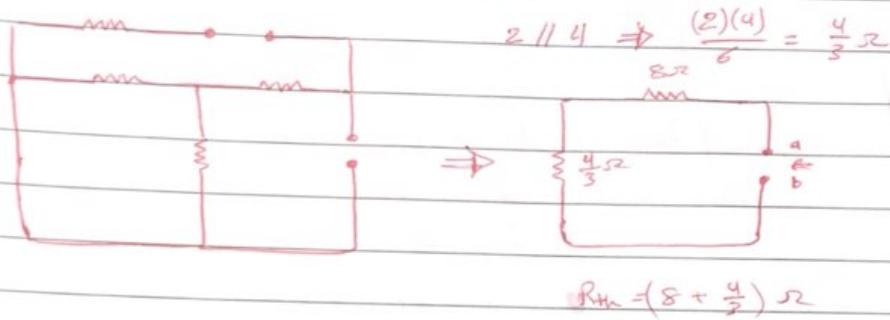\* Remove the voltage and current sources:



\* Put  $R_L$  again:

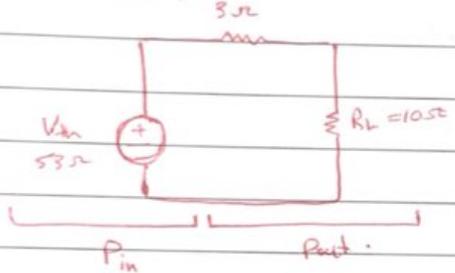

$$P_{RL} = I^2 R_L$$

$$\rightarrow I = \frac{53}{9.375}$$


$$P_{in} = -VI$$

$P_{in} > P_{out} \Rightarrow$  loss of energy because of the 3Ω resistor

So,  $P_{in} = P_{loss} + P_{RL}$

\* efficiency (?) =  $\frac{P_{out}}{P_{in}}$  always  $< 1$

Norton and Thevenin:

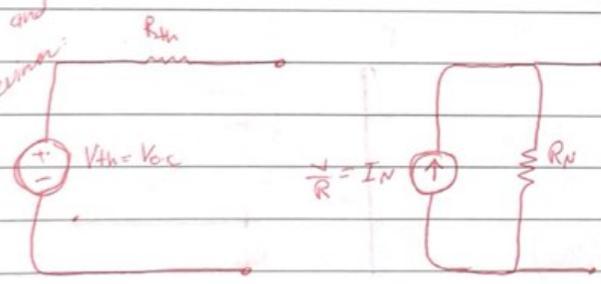

$\Leftrightarrow$   
source transformation

$$\# R_n = R_{th} \# \Rightarrow \frac{V_{oc}}{I_{sc}} = \frac{V_{th}}{I_n}$$


$$\text{So, } I_n = \frac{V_{oc}}{R_{th}}$$

or

Remove  $R_L$  and put short circuit then calculate the current in the short circuit which is  $I_{sc} = I_n$

$\hookrightarrow$  If I don't calculate  $R_{th}$ .

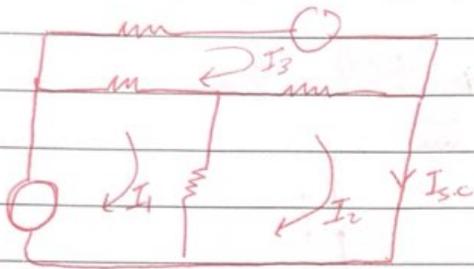~~It is the same as~~  
 ~~$I_n = \frac{V_{oc}}{R_{th}}$~~



$$I_3 = \frac{53}{9.3}$$

by (Mesh):  
 $I_{sc} = I_2$   
 $I_3 = 5$


$$\# 10 = 6I_1 - 4I_2 - 2(5)$$

$$\# 0 = -4I_1 + 12I_2 - 8(5)$$

$$20 = 28I_2 - 20 - 120$$

$$I_2 = \frac{160}{28}$$

\* Maximum power transfer:

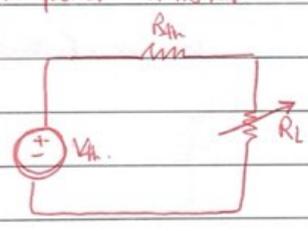


$R_L = ??$

- ①  $P_{RL} = \text{Max}$
- ②  $P_{\text{transferred from the source}} = \underline{\text{Max}}$
- ③  $P_{\text{loss}} = \underline{\text{Min}}$

$$P_{RL} = I^2 R_L$$

$$\text{(for) } P_{RL} = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

↓  
Max

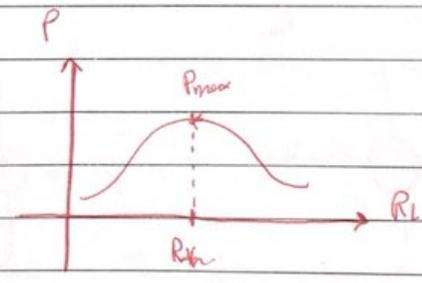


$$f'(x) = 0 \Rightarrow \tau \text{ find } x \text{ (Max)}$$

$$R_L = R_{th}$$

$P_{RL \text{ Max}}$

$$P_{\text{max}} = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_{th} = \frac{V_{th}^2}{4 R_{th}^2} R_{th} = \frac{V_{th}^2}{4 R_{th}} \neq$$

\* Post paper:

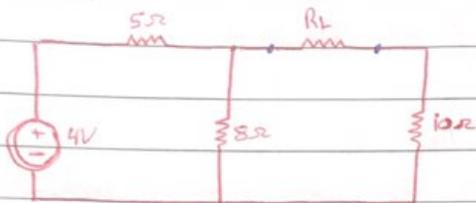


Ⓐ Select a value for  $R_L$  to absorb Max power from the CKL

Ⓑ  $V_{th}$

Ⓒ  $P_{max}$

Ⓓ  $R_{L2} = 10\Omega \Rightarrow P_{RL}$


Ⓐ  $R_L = R_{th}$

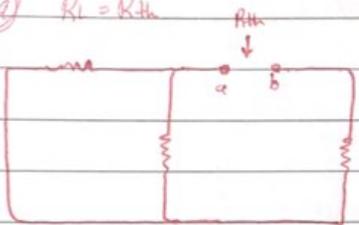

$$5 \parallel 10 \Rightarrow \frac{(5)(10)}{5+10} = \frac{40}{15}$$

$$R_{th} = 10 + \frac{40}{15} = 13$$


Ⓑ put the voltage again

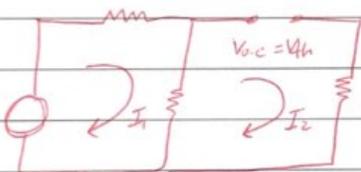

$$4 = 13 I_1 \Rightarrow I_1 = \frac{4}{13} A$$

$$+V_{oc} - 8\left(\frac{4}{13}\right) = 0 \Rightarrow V_{oc} = \frac{32}{13}$$

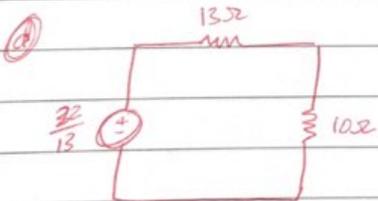
$$\text{Ⓒ } P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{\left(\frac{32}{13}\right)^2}{4(13)} = \frac{(32)(8)}{(13)(13)} \text{ watt.}$$



$$P_{RL} = I^2 R = \left(\frac{\frac{32}{13}}{13+10}\right)^2 10$$

Past papers

②  $R_L \Rightarrow$  Max power

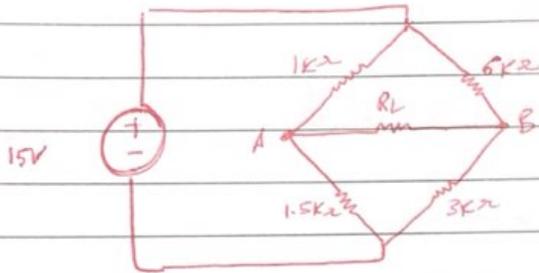


⑥  $P_{max}$

⑦ If the voltage source is replaced with a current source (15A)

Repeat a, b.

②  $R_L = R_{th}$

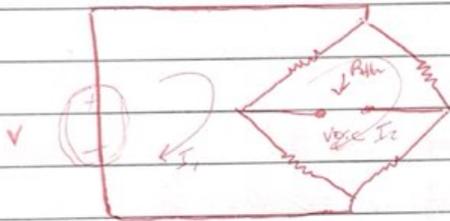

$(1, 1.5) \rightarrow$  parallel

$$\frac{(1)(1.5)}{2.5} = 0.6 \text{ k}\Omega$$

$(6, 3) \rightarrow$  parallel

$$\frac{(6)(3)}{9} = 2 \text{ k}\Omega$$

$(0.6, 2) \rightarrow$  series

$$R_{th} = 0.6 + 2 = 2.6 \text{ k}\Omega$$

⑥  $P_{max} = \frac{V_{th}^2}{4R_{th}} =$

$V_{th} =$  by mesh

voltage source

$$15 = (2.5k)(I_1) - (2.5k)(I_2) \dots (1)$$

$$0 = (-2.5k)(I_1) + (11.5k)(I_2) \dots (2)$$


$$15 = 9kI_2 \Rightarrow I_2 = \frac{15}{9} = \frac{5}{3} \text{ mA}$$

$$6kI_2 - V_{oc} + 1k(I_2 - I_1) = 0 \Rightarrow V_{oc} = V_{th}$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

## Solving problems (Mesh and Nodal)

Ex ①

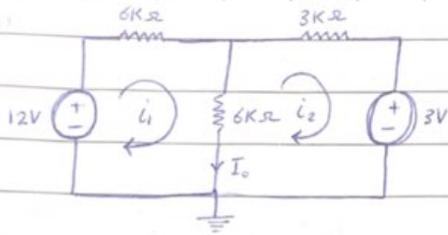

$$i_1(6k + 6k) - i_2(6k) - 12 = 0$$

$$12k i_1 - 6k i_2 = 12 \quad \dots \textcircled{1}$$


$$i_2(6k + 3k) - i_1(6k) + 3 = 0$$

$$9k i_2 - 6k i_1 = -3 \quad \dots \textcircled{2}$$

$$I_{o_2} = i_1 - i_2 = 1.25 - 0.5 = 0.75 \text{mA}$$

$$\Rightarrow \begin{cases} i_1 = 1.25 \text{mA} \\ i_2 = 0.5 \text{mA} \end{cases}$$

Ex ②

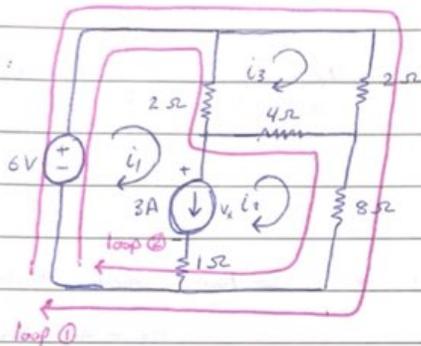

$$i_3(2 + 4 + 2) - i_2(4) - i_1(2) = 0 \quad (\text{Mesh } \underline{3})$$

$$8i_3 - 4i_2 - 2i_1 = 0 \quad \dots \textcircled{1}$$

$$-6 + 2i_3 + 8i_2 = 0 \quad \dots \textcircled{2} \quad (\text{by supermesh loop 1})$$

or

$$-6 + 2(i_2 - i_1) + 4(i_2 - i_3) + 8i_2 = 0 \quad \dots \textcircled{2} \quad (\text{by loop 2})$$

$$3 = i_1 - i_2 \quad \dots \textcircled{3}$$

$$i_1 = 1.10 \text{A} \quad i_2 = 0.47 \text{A} \quad i_3 = 3.47 \text{A}$$

\* Power consumed or delivered by current source (3A):


$$P = +3V_x$$

$$\xrightarrow{\text{by KVL}} 4(i_2 - i_3) + 8i_2 + 1(i_2 - i_1) - V_x = 0$$

$$V_x = -8.87 \text{ Volt}$$

$$P = 3(-8.87) = -26.61 \text{ watt}$$

Ex ③:

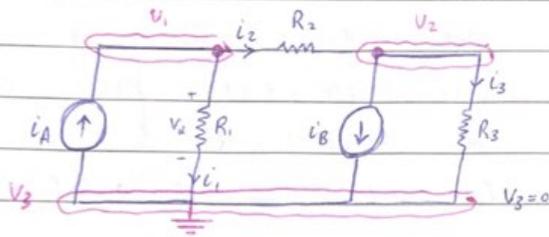

at  $V_1$ :  $i_1 = \frac{V_1 - V_3}{R_1}$   $i_2 = \frac{V_1 - V_2}{R_2}$   $i_A = i_1 + i_2$

$i_A = \frac{V_1 - V_3}{R_1} + \frac{V_1 - V_2}{R_2} \dots (1)$

at  $V_2$ :  $i_2 = \frac{V_2 - V_1}{R_2}$   $i_3 = \frac{V_2 - V_3}{R_3}$   $i_B = -i_2 - i_3$


$V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left( \frac{1}{R_2} \right) - i_A = 0 \dots (1)$

$-V_1 \left( \frac{1}{R_1} \right) + V_2 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) - V_1 \left( \frac{1}{R_2} \right) + i_B = 0 \dots (2)$

OR

$i_B = \frac{V_3 - V_2}{R_3} + \frac{V_1 - V_2}{R_2} \dots (2)$

\* Past paper (2019):

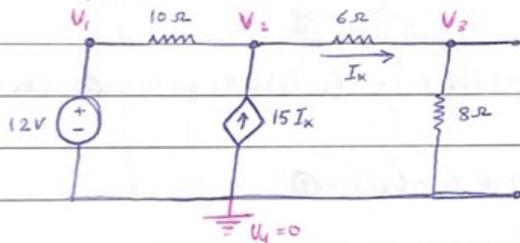

Find: ①  $I_x$  ② Power delivered/absorbed by the dependent source

Can solve it by Mesh analysis  $\rightarrow$  straightforward

by Nodal:


①  $V_1 = 12V$

$V_2 \left( \frac{1}{10} + \frac{1}{6} \right) - V_3 \left( \frac{1}{6} \right) - V_1 \left( \frac{1}{10} \right) - 15I_x = 0$   $I_x = \frac{V_2 - V_3}{6} \dots (1)$

$V_3 \left( \frac{1}{6} + \frac{1}{8} \right) - V_2 \left( \frac{1}{6} \right) = 0 \dots (2)$

②  $P = -15I_x (V_2 - 0)$

\* Past paper:

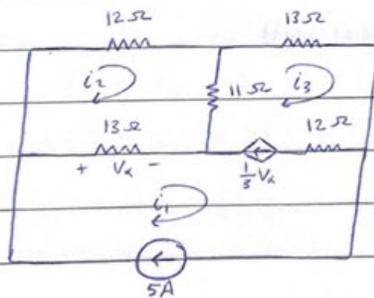

Find:  $i_1, i_2, i_3$  and  $V_x$

by Mesh analysis:


$i_1 = 5A$

$-i_1(13) + i_2(12+11+13) - i_3(12) = 0 \dots (1)$

$\frac{1}{3} V_x = i_3 - i_2 \dots (2)$

$\vec{I} \rightarrow V_x = 13(i_1 - i_2)$

\* Past paper:

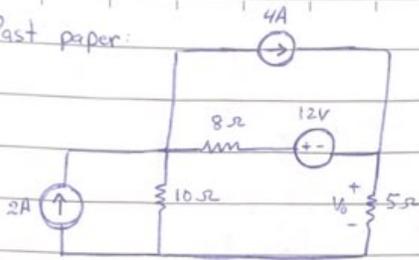


by superposition:

the component  $V_o$  due to 2A current source

↳ by killing all the sources except the (2A) current source.

- Due to (2A)?

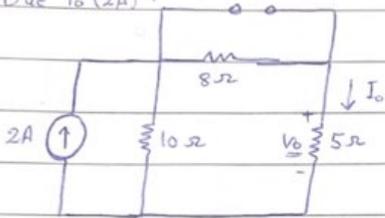

$$I_o' = 2 \left( \frac{10}{23} \right) \Rightarrow V_o' = 5 I_o' = \frac{100}{23}$$

\* We can use the superposition to find

$V (V' + V'' + V''')$  and  $I (I' + I'' + I''')$  because they


are linear but the power non-linear so we cannot

use the superposition to find it by  $(P' + P'' + P''')$

↳ wrong

\* **DONT USE** superposition if there is an independent source.

- Due to (4A)?

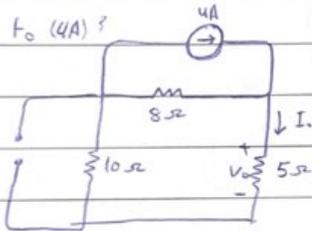


$$I_o'' = \frac{-12}{23} * 5 \Rightarrow V_o'' = \frac{-60}{23}$$

$$V_{out} = V_o' + V_o'' + V_o'''$$


$$P = \frac{V^2}{R} = I^2 R$$

- Due to (12V)?

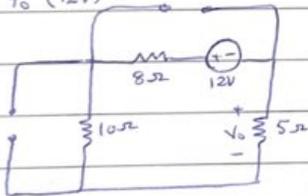


$$V_o''' = \left( \frac{4+8}{23} \right) * 5$$

\* Past paper:


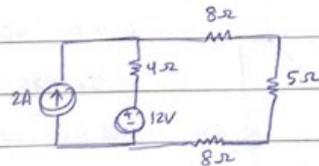


equivalent to

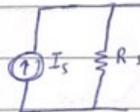

Find:

$I_s$  and  $R_s$ .

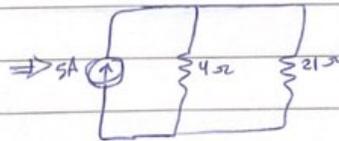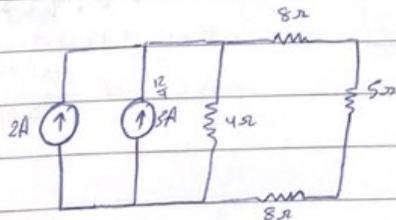


(4/21) → parallel

$$R_s = \frac{(4)(21)}{25} = 3.56 \Omega$$

$$I_s = 5A$$


\* Find  $V_{ab} = ?$   $V_a - V_b$

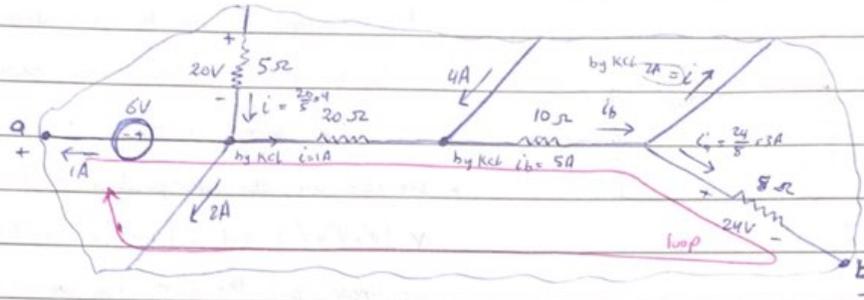

$$-6 + 20 I_{20} + 10 i_b + 20 = V_{ab}$$

$$-6 + 20(1) + 10(5) + 20 = V_{ab}$$

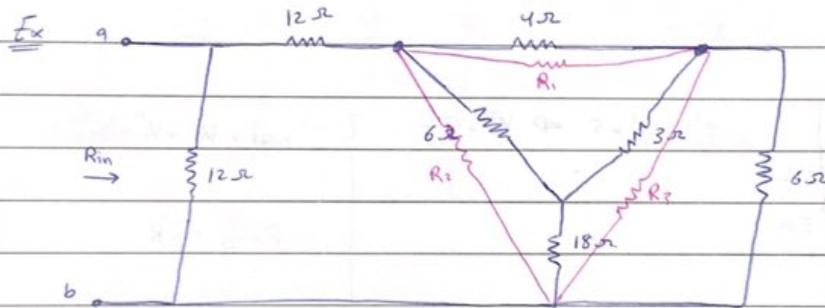
$$-6 + 20 + 50 + 20 = V_{ab} \Rightarrow V_{ab} = 84 \text{ Volts.}$$



$$R_1 = \frac{(3)(18) + (2)(6) + (18)(6)}{18} = \frac{180}{18} = 10 \Omega$$

$$R_2 = \frac{180}{3} = 60 \Omega$$

$$R_3 = \frac{180}{6} = 30 \Omega$$

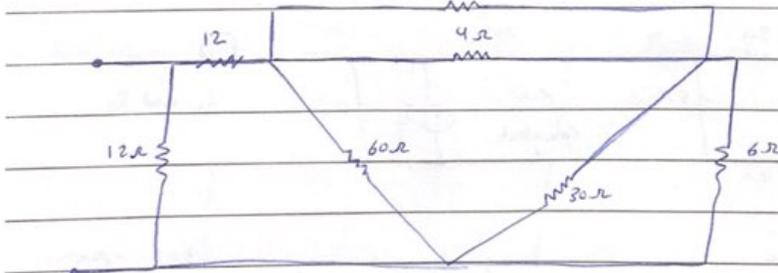

$$6 \parallel 30 \Rightarrow \frac{(6)(30)}{36} = 5 \Omega$$

$$4 \parallel 10 \Rightarrow \frac{(4)(10)}{14} = 2.86 \Omega$$

$$5 + 2.86 = 7.86 \Omega$$


$$7.86 \parallel 60 \Rightarrow \frac{(7.86)(60)}{67.86} = 6.95 \Omega$$

~~$$18.95 \parallel 12 \Rightarrow \frac{(18.95)(12)}{30.95} = 7.35 \Omega$$~~

$$6.95 + 12 = 18.95 \Omega$$


$$18.95 \parallel 12 \Rightarrow \frac{(18.95)(12)}{30.95} = 7.35 \Omega$$

problems (Thevenin and Norton).

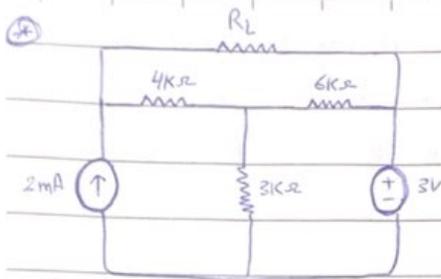

Find the thevenin equivalent circuit seen by  $R_L$ ?

→ Find  $R_{th}$  and  $V_{th}$ .

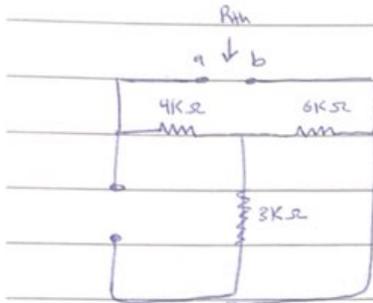


$$6 \parallel 3 \rightarrow \frac{(6)(3)}{9} = 2k\Omega$$

(2, 4) → series

$$2 + 4 = 6k\Omega$$

$$\therefore R_{th} = 6k\Omega$$

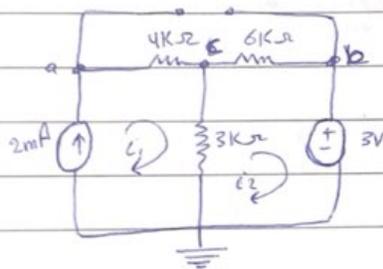

by Nodal

$$V_a \left(\frac{1}{4k}\right) - V_c \left(\frac{1}{4k}\right) = 2m \quad \dots (1)$$

$$-V_a \left(\frac{1}{4k}\right) - V_b \left(\frac{1}{6k}\right) + V_c \left(\frac{1}{4k} + \frac{1}{3k} + \frac{1}{6k}\right) = 0 \quad \dots (2)$$

$$\boxed{V_b = 3V} \quad \# V_{oc} = V_a - V_b \quad \#$$

by Mesh.

~~Mesh analysis~~


$$-2m(3k) + 9k I_2 = -3$$

$$+ V_{oc} - 6k I_2 - 4k I_1 = 0$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} \quad \# \quad \Rightarrow \quad \text{Just if } R_{th} = R_L.$$

$$\text{If not } P = I^2 R_L.$$

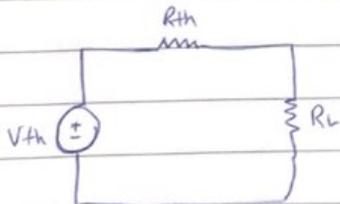If  $R_L = 10\Omega$ , Find  $I_{R_L} = ?$





$$I = \frac{V_{th}}{R_{th} + R_L}$$

$$P_{absorb \text{ by } R_L} = I^2 R_L \quad \text{not} \quad \frac{V_{th}^2}{4R_{th}}$$

$$I_{R_L} = I_{sc} = \frac{V_{th}}{R_{th}}$$

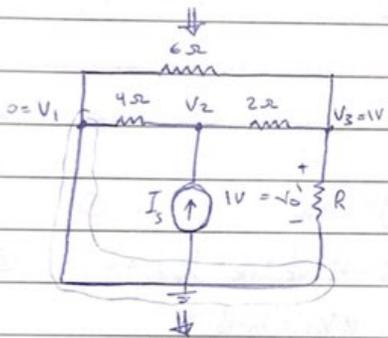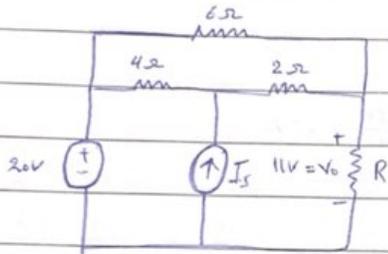\* Using superposition method for the circuit shown below, it was found that the total value of the voltage  $V_0 = 11V$ , and when disconnecting the voltage source (i.e. replaced by short circuit) the voltage was found to be  $V_0 = 1V$ . Hence, the value of the current source ( $I_s$ ) would have to be:





$$V_1 \left( \frac{1}{4} + \frac{1}{2} \right) - V_2 \left( \frac{1}{4} \right) - 1 \left( \frac{1}{2} \right) = 0$$

$$(V_2) = -\frac{4}{2} \text{ volts.}$$


$$V_2 \left( \frac{1}{4} + \frac{1}{2} \right) = V_1 \left( \frac{1}{4} \right) - \frac{V_3}{2} = (I_s)$$

$$V_0'' = V_0 - V_0' = 11 - 1 = 10V$$


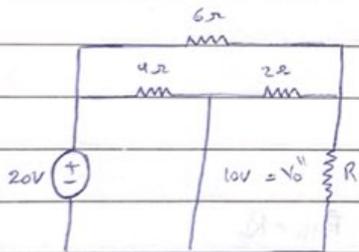


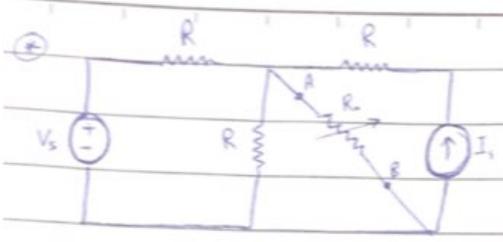

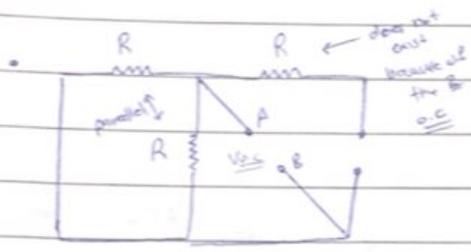- The Norton resistance:
  - The Norton current:
  - The maximum power transferred to  $R_L$
- Seen from  $R_L$




$$R_N = \frac{R}{2}$$

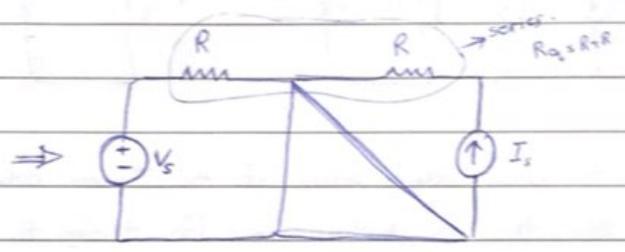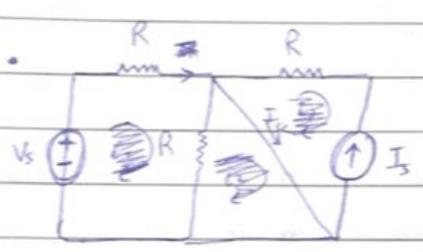

$$I_N = I_s - I_R$$


$$\rightarrow I_R = \frac{V_s}{R}$$

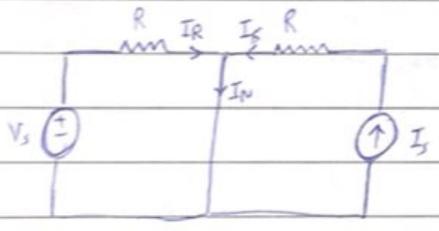


$$P_{max} = \frac{V_{th}^2}{4R_{th}} \rightarrow (V_{th} = R_{th} I_N)$$

⊛ Using the source transformation method, the value of the voltage  $V_x$  (in volt)

in the following circuit:


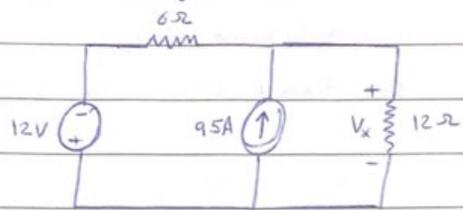


⇓

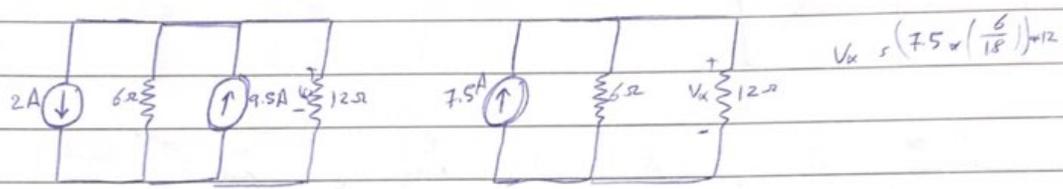

$$V_x = \left( 7.5 + \left( \frac{6}{18} \right) \right) \times 12$$

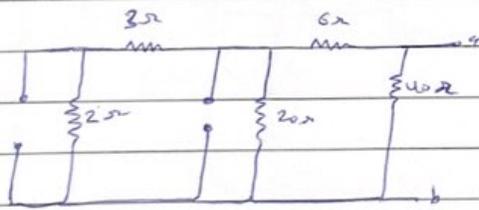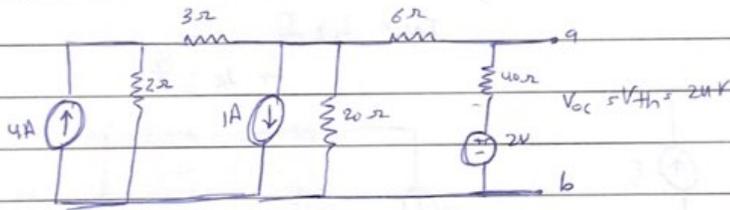⊛ For the circuit shown below, if the Thevenin voltage ( $V_{th}$ ) across the terminals (a) and (b) is 24V, then the Norton current ( $I_N$ ) through the terminals (a) and (b) is:



$$I_N = \frac{V_{th}}{R_{th}}$$

(2, 3) → series

$$2 + 3 = 5 \Omega$$

(5, 20) → parallel

$$\frac{5 \times 20}{25} = 4 \Omega$$

(7, 40) → series


$$4 + 6 = 10 \Omega$$

(10, 40) → parallel

$$\frac{10 \times 40}{50} = 8 \Omega$$

$$R_{th} = 8 \Omega \quad \Rightarrow \quad I_N = \frac{24}{8} = 3A$$

$$V_{th} = 24V$$

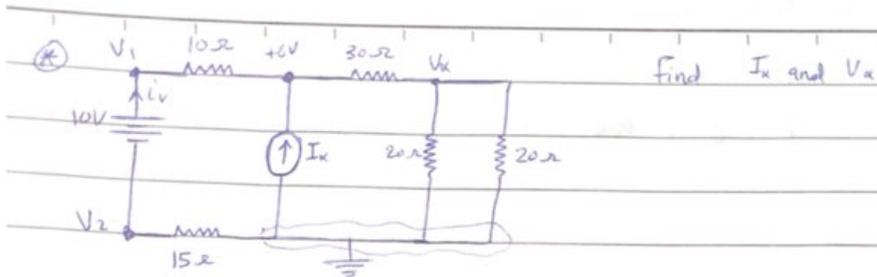


$$V_1 - V_2 = 10$$

$$-V_1 \left(\frac{1}{10}\right) + 6 \left(\frac{1}{10} + \frac{1}{30}\right) - V_x \left(\frac{1}{30}\right) = I_x$$


$$V_x \left(\frac{1}{30} + \frac{1}{20} + \frac{1}{20}\right) - 6 \left(\frac{1}{30}\right) = 0$$

Supernode:  $I_v = V_1 \left(\frac{1}{10}\right) - 6 \left(\frac{1}{10}\right)$
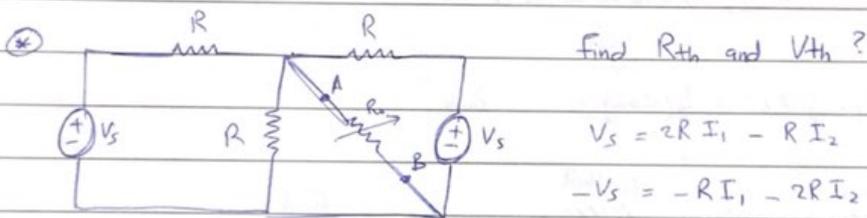
$$V_2 \left(\frac{1}{15}\right) + I_v = 0 \Rightarrow I_v = \frac{-V_2}{15}$$



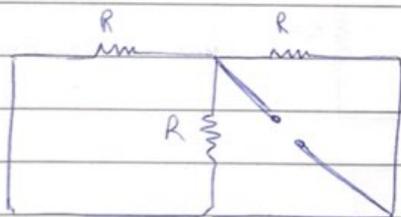
$$\begin{aligned} V_s &= 2RI_1 - RI_2 \\ -V_s &= -RI_1 - 2RI_2 \end{aligned} \Rightarrow \begin{aligned} I_1 &= \frac{3}{5R} V_s \\ I_2 &= \dots \end{aligned}$$



$$R_{th} = \frac{R}{5}$$


$$V_{oc} = R(I_1 - I_2) = V_{th}$$

# Problems (Conductors and Inductors)

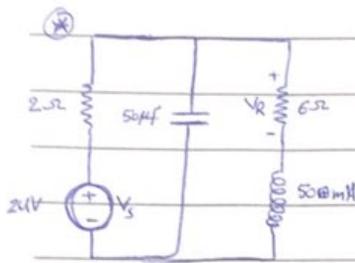

Find:

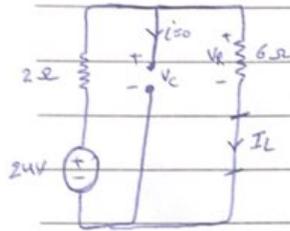$E_C$ ,  $E_L$ ,  $V_R$  Under DC condition.



$$V_R = I_L R$$

$$24 = I_L (8) \Rightarrow I_L = \frac{24}{8} = 3A$$


$$V_R = I_L R$$

$$= (3)(6) = 18 \text{ Volts.}$$

$$E_C = \frac{1}{2} C V_C^2 = \frac{1}{2} (50\mu)(18)^2 \text{ Joules.}$$


by KVL  $\downarrow -V_C + IR = 0 \Rightarrow V_C = V_R = 18 \text{ Volts.}$
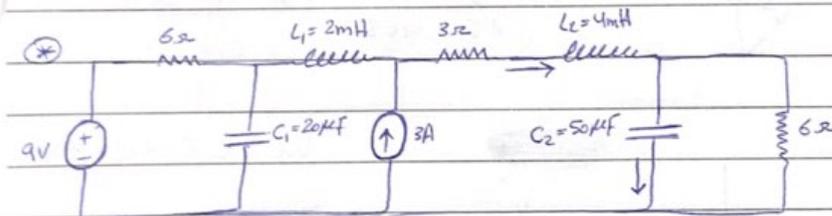
$$E_L = \frac{1}{2} L I^2 = \frac{1}{2} (500m)(3)^2 = \text{Joules.}$$



Find:

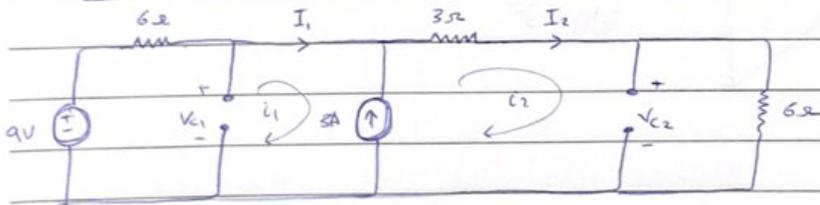$E_{L2}$ ,  $E_{C2}$ ,  $E_{C1}$ ,  $E_{C2}$  under DC condition.



by super Mesh:

$$9 = 6 I_1 + 9 I_2 \dots \textcircled{1}$$

$$3 = -I_1 + I_2 \dots \textcircled{2}$$

$$\Rightarrow I_2 = 1.8A$$

$$E_{L2} = \frac{1}{2} (4m)(1.8)^2$$

$$V_{C2} = 6 I_2 = 6(1.8) = 10.8$$

$$E_{C2} = \frac{1}{2} (50\mu)(10.8)^2$$


$$I_1 = -1.2A$$

$$E_{C1} = \frac{1}{2} (2m)(-1.2)^2$$

$$-9 + 6(-1.8) + V_{C1} = 0$$


\* Past paper:

Find  $I_L$  and  $E_C$ :

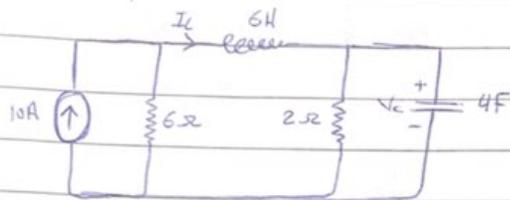

@ DC conditions OR @ Steady state.

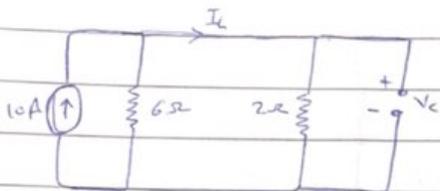Cap.  $\Rightarrow$  O.P  
Ind.  $\Rightarrow$  S.C




$$I_L = 10 \left( \frac{6}{8} \right) = \frac{60}{8}$$

$$V_C = V_{2\Omega} = R I_L = (2) \left( \frac{60}{8} \right)$$

$$E_C = \frac{1}{2} C V^2 = \frac{1}{2} (4) (15)^2$$

\* Past paper:

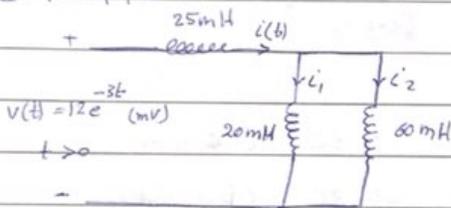


$i_1(0) = -30\text{mA} \rightarrow$  jipppp... (scribbles)

Note that  $i_1(0^-) = i_1(0^+)$

Find:  $i_2(0)$ ,  $i_1(0)$

$i_1(t)$ ,  $i_2(t)$

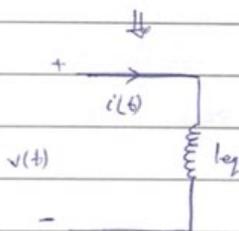


$$V_L = L \frac{di}{dt} \Rightarrow \int_0^t \frac{V_L}{L} dt = \int_0^t di$$

$$\frac{1}{L} \int_0^t V_L dt = i(t) - i(0) \quad \#$$

$$L_{eq} = \frac{20 \times 60}{80} = 15\text{mH} + 25\text{mH} = 40\text{mH}$$


$$\frac{1}{40\text{m}} \int_0^t 12e^{-3t} dt + (-30\text{m}) = i(t)$$

$$i(0) = i_1(0) + i_2(0)$$

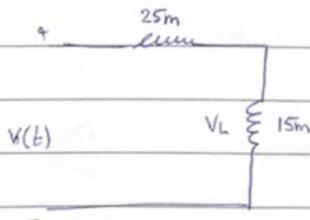


$$V_L(t) = L \frac{di}{dt}$$

⊗ past paper

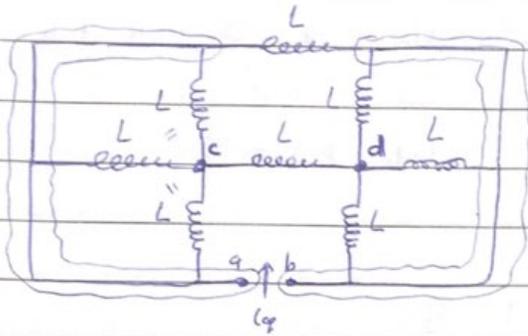


$$L \parallel L \parallel L \Rightarrow \frac{L}{3} \quad (a, c \text{ nodes})$$
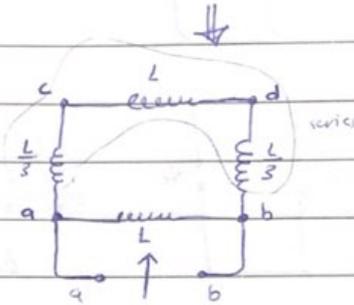
$$L \parallel L \parallel L \Rightarrow \frac{L}{3} \quad (b, d \text{ nodes})$$




$$\frac{L}{3} + L + \frac{L}{3} = \frac{5L}{3}$$
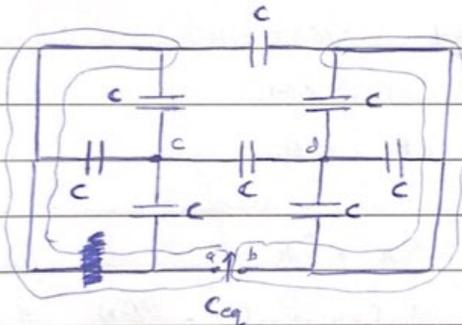
$$\frac{5L}{3} \parallel L \Rightarrow \frac{\frac{5L}{3} \cdot L}{\frac{5L}{3} + L} = \frac{5}{8} L \quad (H)$$



$$C \parallel C \parallel C \Rightarrow 3C \quad (a, c \text{ nodes})$$
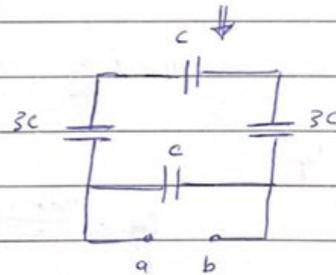
$$C \parallel C \parallel C \Rightarrow 3C \quad (b, d \text{ nodes})$$



$(3C, C, 3C) \rightarrow \text{series}$

$$\frac{1}{3C} + \frac{1}{C} + \frac{1}{3C} = \frac{5}{3C} \Rightarrow \frac{3C}{5}$$

$$\frac{3C}{5} \parallel C \Rightarrow \frac{8}{5} C$$

# Transient


⇒ We use differential equations

1<sup>st</sup> order ⇒  $ax' + bx + c = 0$

$$\frac{dx}{dt} \leftarrow \bar{I} \quad \bar{I} \rightarrow x(t) = A e^{-t/\tau} + B$$

↓ from the circuit

⊗ RL ckt :

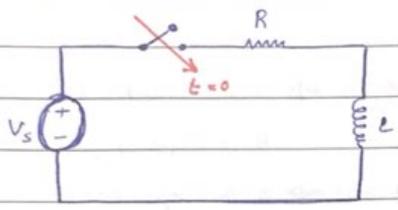

$t < 0 \Rightarrow$  switch is open

$t > 0 \Rightarrow$  switch is closed

$i_L(0^-) = i_L(0^+) \Rightarrow$  Initial condition

$$i(t) = \begin{cases} 0, & t < 0 \Rightarrow i_L(0^-) = 0 \text{ because the switch is open.} \\ ?1, & t \geq 0 \\ \rightarrow \text{by KVL} \Rightarrow V_s = V_R + V_L \end{cases}$$

$$V_s = Ri + L \frac{di}{dt} \Rightarrow \boxed{L \frac{di}{dt} + Ri - V_s = 0} \text{ diff. equation}$$

$$i(t) = A e^{-t/\tau} + B$$

For RL ckt  $\Rightarrow \tau = \frac{L}{R_{th}}$  sec  
 → Thevenin equivalent resistance seen from L

To find A and B:

① Initial condition:

$$i(0^-) = i(0^+) = 0$$

when  $t \geq 0$   $\boxed{A + B = 0}$

② Final condition:


when  $t \rightarrow \infty \Rightarrow$  steady state ( $L \rightarrow s.c$ )

$$i(t \rightarrow \infty) = \frac{V_s}{R}$$

$$\frac{V_s}{R} = A e^{-\infty} + B$$

$$\boxed{B = \frac{V_s}{R}}$$
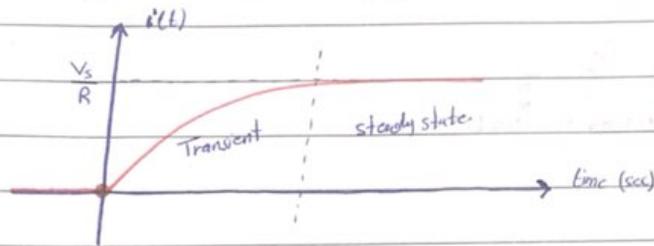
$$i(t) = \frac{-V_s}{R} e^{-\frac{t}{\tau}} + \frac{V_s}{R} = \frac{V_s}{R} [1 - e^{-t/\tau}]$$



$$V_L = L \frac{di}{dt}$$


$$= L \left( \frac{-V_s}{R} \left( -\frac{1}{\tau} \right) e^{-t/\tau} \right)$$

$$V_L = V_s e^{-t/\tau}$$

@  $t = 0$

$$V_L = V_s$$

Ex 1:

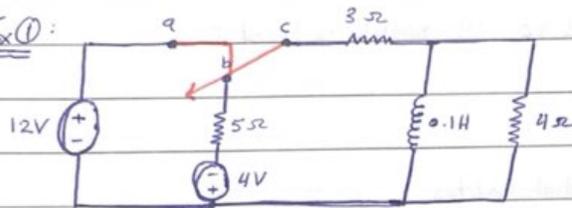

$t < 0 \Rightarrow$  a, b closed

b, c opened




$t \geq 0 \Rightarrow$  a, b opened

b, c closed

@  $t < 0 \Rightarrow$  Initial condition

$$i(0^-) = i(0^+) = 0$$

@  $t \geq 0$

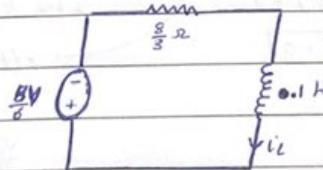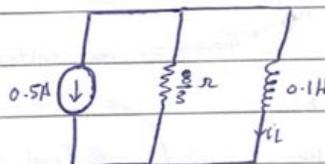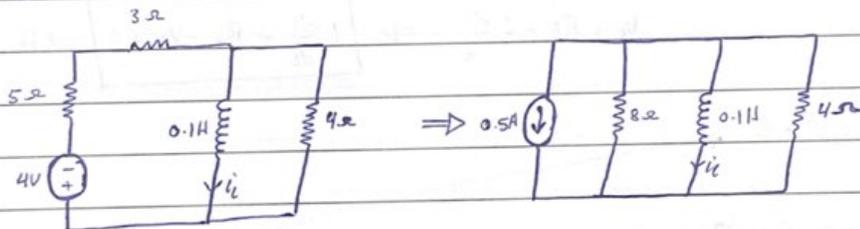

by KVL  $\Rightarrow \frac{8}{5} + \frac{8}{5} i + 0.1 \frac{di}{dt} = 0$


$$i = A e^{-t/\tau} + B \Rightarrow \tau = \frac{0.1}{\frac{8}{5}} = \frac{0.2}{8} \text{ sec}$$

@  $t = 0 \rightarrow A + B = 0 \Rightarrow A = 0.5$

@  $t = \infty \rightarrow B = -0.5$

$$i = (0.5) e^{-t/0.25} + 0.5$$

Ex ②:

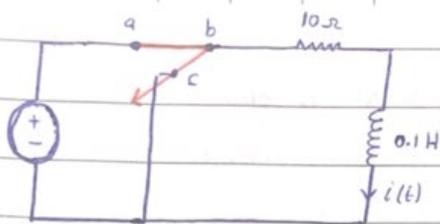

@  $t < 0 \Rightarrow a, b$  closed

@  $t \geq 0 \Rightarrow a, b$  opened

$b, c$  closed.

@  $t < 0 \Rightarrow$  steady state

$$i(0^-) = \frac{10}{10} = 1A$$

$i(0^-) = i(0^+) = 1 \Rightarrow$  Initial condition.

@  $t \rightarrow \infty \Rightarrow$  steady state.

$i(\infty) = 0 \Rightarrow$  Final condition.

$$@ t \geq 0 \Rightarrow 10i + 0.1 \frac{di}{dt} = 0 \Rightarrow A e^{-t/\tau} + B = i(t)$$


$$\tau = \frac{0.1}{10} = 0.01 \text{ sec}$$

Initial condition  $\Rightarrow A+B=1 \Rightarrow A=1$

Final condition  $\Rightarrow B=0$

$$i(t) = e^{-t/0.01}$$

\* RC CKT:

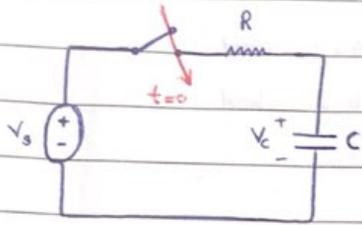

$t < 0 \Rightarrow$  switch is open

$t \geq 0 \Rightarrow$  switch is closed

$$[i_c = C \frac{dV}{dt}]$$

$V_c(0^-) = V_c(0^+) \Rightarrow$  Initial condition:

by KVL:  $V_s = Ri_c + V_c$

$$V_s = RC \frac{dV}{dt} + V_c$$

$$\rightarrow V_c(t) = A e^{-t/\tau} + B \Rightarrow \tau = \frac{RC}{\text{sec}}$$

\* To find A & B:

① Initial condition

$$V_c(0^-) = V_c(0^+)$$

$$\text{@ } t=0 \Rightarrow V_c(0) = A e^{-0/\tau} + B = 0$$

$$A = -B$$

$$A = -V_s$$

② Final condition

$$\text{when } (t \rightarrow \infty) \Rightarrow V_c(\infty) = V_s$$


$$\text{@ } t=\infty \Rightarrow V_c(\infty) = A e^{-\infty/\tau} + B = V_s$$


$$B = V_s$$

$$V_c(t) = -V_s e^{-t/\tau} + V_s$$

$$i_R(t) = i_C(t) = C \frac{dV}{dt} = \frac{CV_s}{\tau} e^{-t/\tau}$$

$$V_c(t) = V_s (1 - e^{-t/\tau})$$

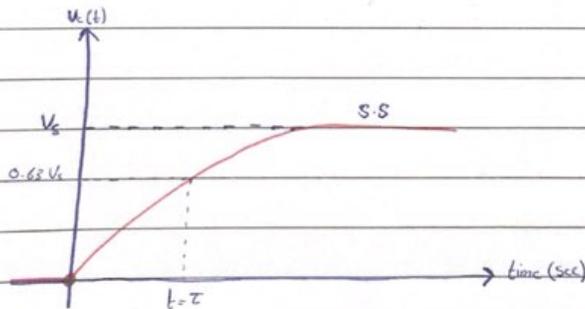

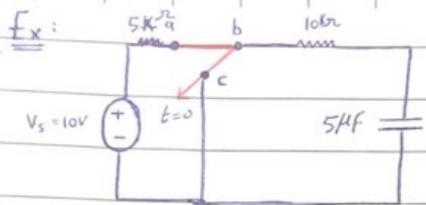

@  $t = 0 \Rightarrow$  a, b (open)

b, c (closed)

Find <sup>(a)</sup>  $V_c(t)$  and <sup>(b)</sup>  $i(t)$

<sup>(c)</sup> @  $t = 5 \rightarrow (+5) \rightarrow (+)$  *(+5) is (+) because...*

by KVL  $\Rightarrow 10i_c + V_c = 0$  @  $t \geq 0$

$$10 \times 5\mu \times \frac{dV_c}{dt} + V_c = 0$$

$$\Rightarrow V_c(t) = A e^{-t/\tau} + B \neq$$

$$@ t \geq 0 \Rightarrow \tau = \frac{1}{RC} = \frac{1}{10k \times 5\mu} = 20 \text{ sec}$$

\* Initial condition


$$V_c(0^-) = V_c(0^+) = 10 \text{ Volts}$$

$$@ t = 0 \Rightarrow V_c(0) = A e^0 + B = 10$$

$$A + B = 10$$

$$A = 10$$

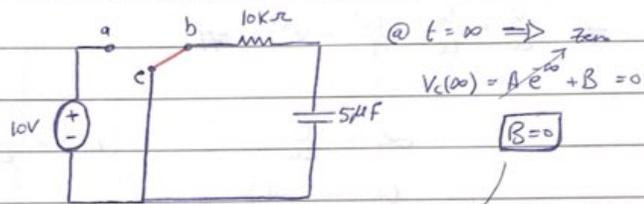\* Final condition:  $V_c(t \rightarrow \infty) = \text{Zero}$




@  $t = \infty \Rightarrow \text{Zero}$


$$V_c(\infty) = A e^{-\infty} + B = 0$$

$$B = 0$$

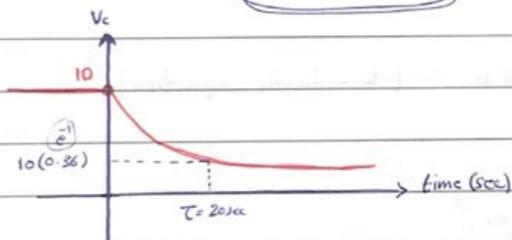
$$\text{(a)} \quad V_c(t) = 10 e^{-t/20}$$


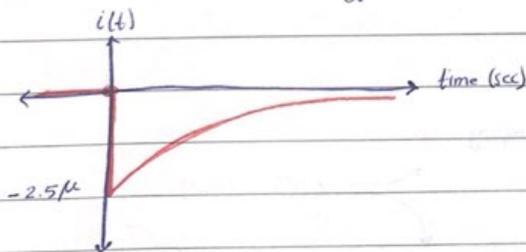
$$\text{(b)} \quad i_c(t) = C \frac{dV}{dt} = 5\mu \left( \frac{-10}{20} e^{-t/20} \right) = -2.5\mu e^{-t/20}$$



\* RLC ckt: (series)

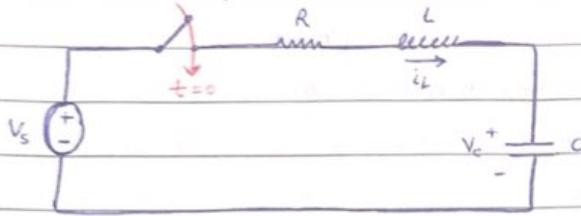

by KVL

$$V_s = V_R + V_C + V_L \rightarrow V_L = L \frac{di}{dt} = LC \frac{d^2V}{dt^2}$$

$$V_s = Ri + RC \frac{dV}{dt} + LC \frac{d^2V}{dt^2} \Rightarrow 2^{nd} \text{ order}$$

$$\# \frac{V_s}{LC} = \frac{VR}{LC} + \frac{RV'}{L} + V'' \quad \#$$

$$\alpha = \frac{R}{2L}$$

(damping ratio)

$$\omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

(natural frequency)

$$\omega_0^2 V_c = V'' + 2\alpha V' + \frac{VR}{LC}$$

$$\Rightarrow S^2 + 2\alpha S + \omega_0^2 = 0 \quad (\text{characteristic equation})$$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\Rightarrow V_c = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

⊕ If  $\alpha > \omega_0$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$V_c(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \Rightarrow \text{over damping.}$$

⊕ If  $\alpha = \omega_0$

$$s_1, s_2 = -\alpha$$

$$V_c(t) = V_s + (A_1 + A_2 t) e^{-\alpha t} \Rightarrow \text{critically damping}$$

$$i_L(0^-) = i_L(0^+) \quad \& \quad V_C(0^-) = V_C(0^+)$$

⊗ If  $\alpha < \omega_0$



$\sqrt{-}$  number  $\Rightarrow$  imaginary number or complex number (not Real number).

$$s_1, s_2 = -\alpha \pm \sqrt{-\alpha^2 - \omega_0^2} = -\alpha \pm \sqrt{-1} \sqrt{\alpha^2 + \omega_0^2} = -\alpha \pm j\omega_d \text{ such that}$$

$$v_c(t) = (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t}$$

$$j = \sqrt{-1}$$
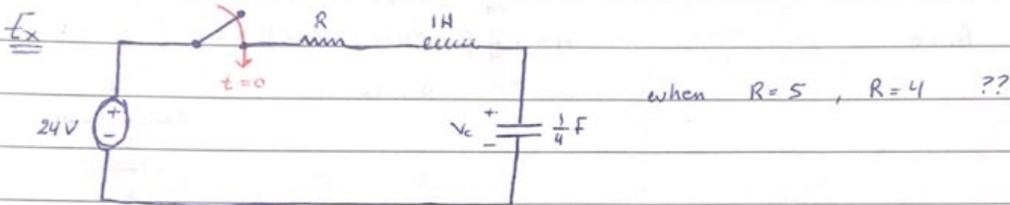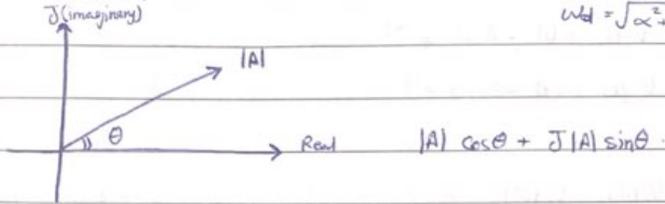
$$\omega_d = \sqrt{\alpha^2 + \omega_0^2}$$



⊗ When  $R = 5$ :

$$\alpha = \frac{R}{2L} = \frac{5}{2} = 2.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4}}} = 2$$

$\alpha > \omega_0 \Rightarrow$  over damping.

$$v_c(t) = 24 + A_1 e^{s_1 t} + A_2 e^{s_2 t} \Rightarrow v_c(t) = 24 + A_1 e^{-t} + A_2 e^{-4t}$$

$$s_1, s_2 = -2.5 \pm \sqrt{(2.5)^2 - (2)^2}$$

$$s_1 = -1, s_2 = -4$$

$$v_c(0^-) = v_c(0^+) = 0$$

$$i_L(0^-) = i_L(0^+)$$

$$v_c(0) = 24 + A_1 e^0 + A_2 e^0 = 0$$

$$i_c = i_L = C \frac{dv}{dt} = \frac{1}{4} (-A_1 e^{-t} - 4A_2 e^{-4t})$$

$$\boxed{A_1 + A_2 = -24}$$

$$i(0) = \frac{1}{4} (-A_1 e^0 - 4A_2 e^0) = 0$$

$$(-\frac{1}{4}A_1 - 1A_2 = 0) \times 4$$

Find  $A_1$  and  $A_2$

$$-A_1 - 4A_2 = 0$$

$$\boxed{A_1 = -4A_2}$$

⊗ When  $R=4$

$$\alpha = \frac{4}{2} = 2 \quad \omega_0 = 2$$

$\alpha = \omega_0 \Rightarrow$  critically damping.

$$V_c(t) = (A_1 + A_2 t) e^{-\alpha t}$$

$$V_c(t) = (A_1 + A_2 t) e^{-2t}$$

$$V_c(0^-) = V_c(0^+) = 0$$

$$V_c(0) = A_1 e^0 = 0$$

$$A_1 = 0$$

$$i_c = i_c = i_c(0^-) = i_c(0^+) = 0$$


$$i_c = C \frac{dV_c}{dt} = \frac{1}{4} \left( (-2e^{-2t}(A_2)) + (A_2 e^{-2t}) \right)$$

$$i_c(0) = \frac{1}{4} \left( (-2e^0)(0) + A_2 e^0 \right) = 0$$

$$A_2 = 0$$

السؤال نفسه  
هنا

\* RLC CKT (parallel)

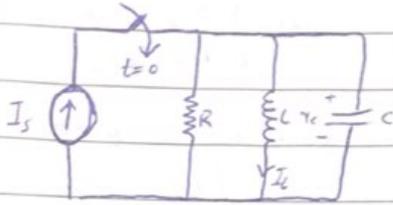

(a)  $v(t) \quad t \geq 0$

(b)  $I_L(t) \quad t \geq 0$

(c)  $I_R(t) \quad t \geq 0$

by KCL

$$I_s = I_R + I_L + I_C$$

~~$I_s = I_R + I_L + I_C$~~

$$V_L = L \frac{di_L}{dt}$$

$$i_C = C \frac{dV_C}{dt}$$

Note that  $V_C = V_L = V_R$

$$I_R = \frac{V_C}{R} = \frac{L \frac{di_C}{dt}}{R}$$

$$i_C = C \frac{dV}{dt} = CL \frac{di_C^2}{dt^2}$$

$$I_s = \frac{L}{R} i_C' + I_L + CL i_C''$$

2<sup>nd</sup> order diff.

$$\Rightarrow i_C'' + \frac{L}{RC} i_C' + \frac{IL}{CL} = \frac{I_s}{CL}$$

$$\alpha_H = \frac{1}{2RC} \quad (\text{Neper freq.})$$

$$i_C'' + \frac{1}{RC} i_C' + \frac{IL}{LC} = \frac{I_s}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec (Natural freq.)}$$

$$i_C'' + 2\alpha i_C' + \omega_0^2 i_C = \omega_0^2 I_s$$

\* To find  $i_C(t) \Rightarrow$  use characteristic equation

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

①  $i_C(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \Rightarrow$  overdamping. ( $\alpha > \omega_0$ )


② ( $\alpha = \omega_0$ )  $\Rightarrow i_C(t) = I_s + (A_1 + A_2 t) e^{-\alpha t} \Rightarrow$  Critical damping.

③ ( $\alpha < \omega_0$ )  $\Rightarrow i_C(t) = I_s + (A_1 \cos \omega_d t + A_2 \omega_d t) e^{-\alpha t}$   $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$   
 $\hookrightarrow$  underdamping.

$$V_L = L \frac{di}{dt} \text{ s } V_C = V_R$$

$$I_R = \frac{V_R}{R} = \frac{V_L}{R}$$

Ex (8.8) Bank

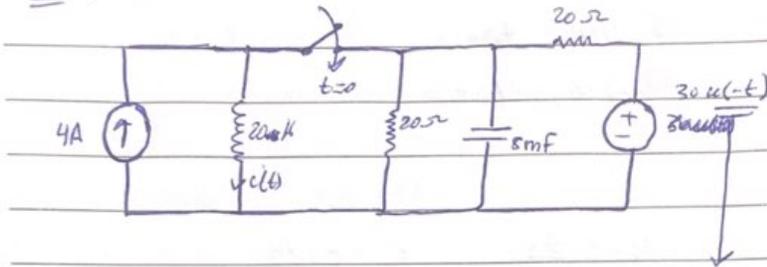

$u(t) \Rightarrow$  unit step function

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$

$$u(t-5) = \begin{cases} 0, & t < 5 \\ 1, & t > 5 \end{cases}$$

$$u(t) = \begin{cases} 0, & t > 0 \\ 1, & t < 0 \end{cases}$$

@  $t > 0$

$\Rightarrow$  close the switch

$\Rightarrow$  voltage source = 0  $\Rightarrow$  short circuit

$$20 \parallel 20 \Rightarrow \frac{(20)(20)}{40} = 10 \Omega = R_{eq}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(10)(5m)} = \frac{1000}{100} = 0.25 \text{ Neper}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5m \cdot 20}} = 2.5 \text{ rad/sec}$$

$\Rightarrow \alpha > \omega_0$   
overdamping.

$$i_L(t) = 4 + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \Rightarrow i_L(t) = 4 + A_1 e^{-12t} + A_2 e^{-0.5t}$$

$$s_1 = -12$$

$$s_2 = -0.5$$

@ Initial condition

$$i_L(0^-) = i_L(0^+)$$

$t < 0 \leftarrow \bar{I}$

$\Rightarrow$  switch open

$\Rightarrow$  voltage source = 30V

$$i_L(0) = 4 \text{ A}$$

$$i_L(0) = 4 + A_1 e^{-12 \cdot 0} + A_2 e^{-0.5 \cdot 0} = 4$$

$$A_1 e^{-12t} + A_2 e^{-0.5t} = 0$$

$$V_L(0^-) = V_L(0^+)$$

$t < 0 \leftarrow \bar{I}$

$$V_L(0) = 30 \text{ V}$$

$$V_L = V_C = L \frac{di_L}{dt} = 20 \left( -12 A_1 e^{-12t} - 0.5 A_2 e^{-0.5t} \right)$$

$$V_L(0) = 20(-12 A_1 - 0.5 A_2) = 30 \text{ #}$$


Find  $A_1$  &  $A_2$

Five Apple

# AC analysis:

↳ periodic

$$f(x) = A \sin(x)$$

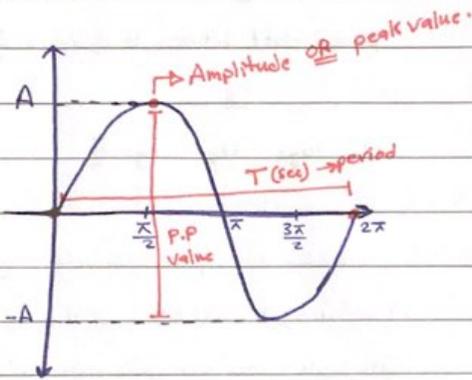

Amplitude = (from avg. → peak)

$$\text{peak value} = A$$

$$\text{Peak to peak value} = 2A$$

↳ (Max → Min)

$$\text{period} = T(\text{sec})$$

$$\text{frequency} = f = \frac{1}{T} \quad (\# \text{ of periods}) \cdot \text{sec}^{-1} (h)$$

$$1 \text{ period} \rightarrow T \text{ sec}$$

$$f \text{ (??)} \rightarrow 1 \text{ sec}$$


$$\text{Avg value} = \frac{1}{T} \int_0^T v(t) dt = \text{Zero}$$

↳ when it's pure sinusoidal function

$$\text{Angular speed} = \text{Angular frequency} = \omega = \frac{2\pi}{T} = 2\pi f \quad (\text{rad/sec})$$

↳ constant
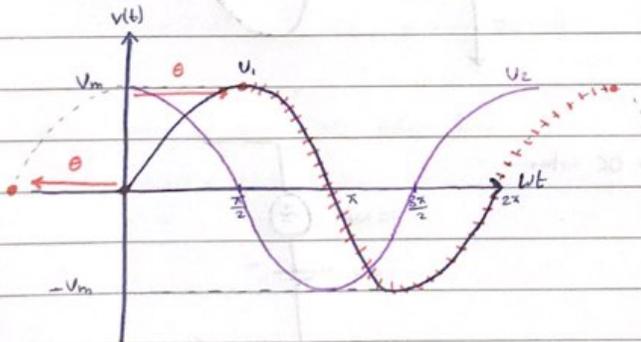
$$\omega = \frac{\alpha(\text{rad})}{T(\text{sec})} \Rightarrow \alpha = \omega t$$



$$V_1 = -V_m \sin(\omega t)$$

$$V_1 = V_m \cos(\omega t - \theta)$$

$$V_1 = V_m \cos(\omega t - \frac{\pi}{2})$$


$$\# \sin(x) = \cos(x - 90) \#$$

$$V_2 = V_m \cos(\omega t)$$

$$V_2 = V_m \sin(\omega t + \theta)$$

$$V_2 = V_m \sin(\omega t + \frac{\pi}{2})$$

\* To find the phase shift:

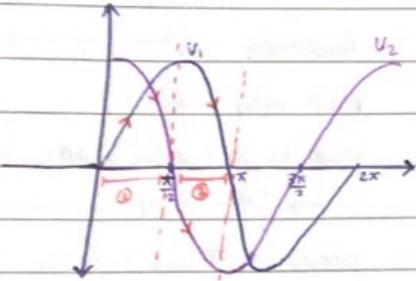

$V_2$  leads  $V_1$  by  $\frac{\pi}{2}$

OR

phase shift between  $V_1$  &  $V_2 = \frac{\pi}{2}$

OR

$V_1$  lags  $V_2$  by  $\frac{\pi}{2}$

\* اختيار فترة ، هاهي الفترة لازم ان 2 function  
 يتصروا نفس التصرف (يا الايجاب لفرقة اولين)  
 بعين بفرقة باقي الفترة منيا بيضوب الصفر بالذات  
 هه الي يكون (leads)  
 \* لا تسي يكون الهم نفس (lag)

\* Ex:  $f(x) = 5 + 10 \sin x$



peak value = 15


p-p value =  $15 - (-5) = 20$

amplitude = 10

$V_{avg} = \frac{1}{T} \int_{\text{period}} v(x) dx$

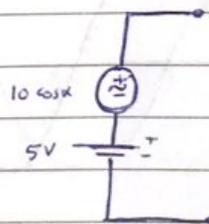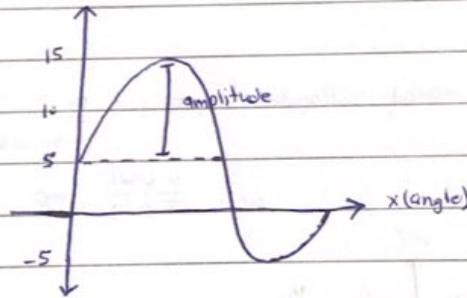$= \frac{1}{T} \int_0^T (5 + 10 \sin x) dx = 5$   
 $\rightarrow$  DC value



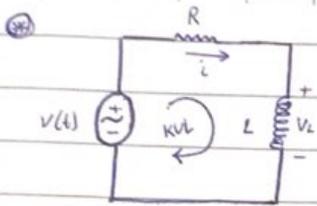

$$v(t) = \cos(\omega t)$$


$$v(t) = iR + v_L = iR + L \frac{di}{dt}$$

$$\cos(\omega t) = iR + L \frac{di}{dt}$$

~~time~~ ~~cos~~  $\Rightarrow$  phasor

$$v(t) = V_m \cos(\omega t + \theta) \Rightarrow \text{phasor } \angle \theta \text{ (phase shift)}$$

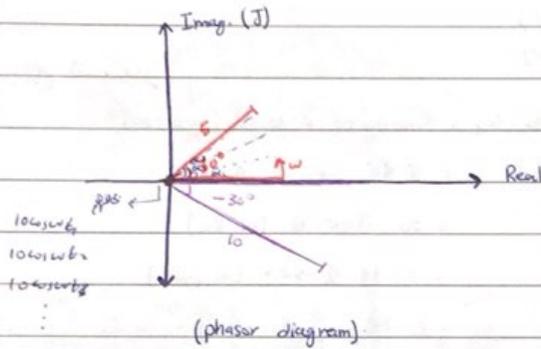(time domain)  $\hookrightarrow$  magnitude =  $V_m$  (as data)



$$5 \angle 30^\circ \Rightarrow 5 \cos(\omega t + 30)$$

$$10 \angle -30^\circ \Rightarrow 10 \cos(\omega t - 30)$$


$\hookrightarrow$  (polar form)

⊗ polar form  $\Rightarrow$  Rectangular form

$$a \angle \theta \Rightarrow a \cos \theta + j a \sin \theta$$

⊗ Rectangular form  $\Rightarrow$  polar form
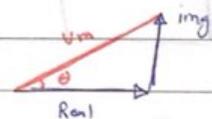
$$\underbrace{a \cos \theta}_{\text{real}} + j \underbrace{a \sin \theta}_{\text{img}}$$



$$V_m = \sqrt{r^2 + \text{img}^2}$$

$$\theta = \tan^{-1} \left( \frac{\text{img}}{\text{real}} \right)$$

⊗ Rectangular form:

$$V_1 = a + j b$$

$$V_2 = c + j d$$

$$V_1 + V_2 = (a + j b) + (c + j d) = (a + c) + j(b + d)$$

$$V_1 V_2 = (a + j b)(c + j d) = ac + jad + jbc + j^2 bd$$

$$= ac + jad + jbc - bd$$

$$= (ac - bd) + j(ad + bc)$$

$$V_1/V_2 = \frac{a + j b}{c + j d} \cdot \frac{c - j d}{c - j d} = \frac{(a + j b)(c - j d)}{c^2 + d^2} \rightarrow \text{Real number}$$

$$(c + j d)^* = c - j d$$

⊗ polar form:

$$\begin{aligned} V_1 &= |V_{m1}| \angle \theta_1 \\ V_2 &= |V_{m2}| \angle \theta_2 \end{aligned} \Rightarrow \begin{aligned} V_1 V_2 &= |V_{m1}| |V_{m2}| \angle (\theta_1 + \theta_2) \\ \frac{V_1}{V_2} &= \frac{|V_{m1}|}{|V_{m2}|} \angle (\theta_1 - \theta_2) \end{aligned}$$

$V_1 \pm V_2 \Rightarrow$  ① polar form  $\rightarrow$  Rectangular form

$V_1 \pm V_2$  (in Rect)

Rectangular form  $\rightarrow$  polar form.

Ex:  $V(t) = 5 \cos(100t) + 30 \sin(100t + 30^\circ)$   
 $\xrightarrow{\bar{L}} \cos(x-90^\circ)$


$$= 5 \cos(100t) + 30 \cos(100t + 30 - 90) = 5 \cos(100t) + 30 \cos(100t - 60)$$

$$= 5 \angle 0^\circ + 30 \angle -60^\circ$$

$$= 20 - j25.98 \text{ (in Rect)}$$

$$= 32.78 \angle -52.4^\circ \text{ (in polar)}$$
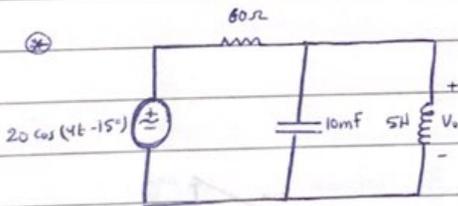
$$= 32.78 \cos(100t - 52.4) \text{ (in time domain)}$$



phasor:

source  $\Rightarrow 20 \angle -15^\circ$

impedance =  $Z$  ( $\Omega$ )


$R \Rightarrow Z_R = R \Omega = 60 \Omega$

for  $C \Rightarrow Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C} \Omega = -j25 \Omega$

for  $L \Rightarrow Z_L = j\omega L = +j20 \Omega$


$L \parallel C \Rightarrow \frac{(j20)(-j25)}{-j5} = \frac{100}{-j} = j100$

Remember:  
 $\frac{1}{j} = -j$

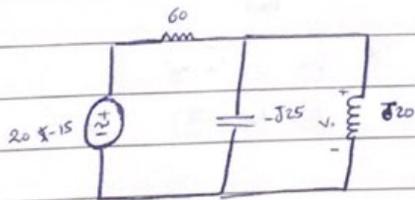

$$V_o = \frac{20 \angle -15^\circ (j100)}{60 + j100} = \frac{2000 \angle 75^\circ}{60 + j100} = \frac{2000 \angle 75^\circ}{\sqrt{3200+10000} \angle \tan^{-1}(\frac{100}{60})}$$

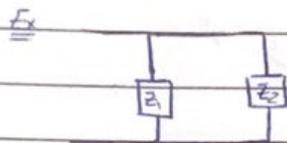\* To find  $Z_{eq} \Rightarrow$  same as Req.



$$\Rightarrow Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(5 + j5)(10 - j4)}{(5 + j5) + (10 - j4)} = \frac{460 + j104}{15 + j1} = \frac{460}{15} + j \frac{104}{15}$$

Real  $\leftarrow$   $\frac{460}{15}$        $\frac{104}{15}$   $\leftarrow$  Imag.

$$Z_1 = 5 + j5$$

$$Z_2 = 10 - j4$$

In general:

$$Z = R \pm jX$$


resistance  $(R)$   $\leftarrow$  always positive      reactance  $(X)$   $\leftarrow$  always positive

if (+)  $\Rightarrow$  inductive load

(-)  $\Rightarrow$  capacitive load

$X=0 \Rightarrow$  Resistive load

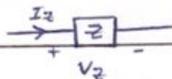\*  $Z = R + jX \Rightarrow$  Inductive load




$I_2$  lags  $V_2$  by  $\theta_z = \theta_v - \theta_i$


$$V = IZ \Rightarrow |V| \angle \theta_v = (|I| \angle \theta_i)(|Z| \angle \theta_z)$$

$$\frac{|V| \angle \theta_v - \theta_i}{|I|} = |Z| \angle \theta_z$$

if  $\theta_v = 0$

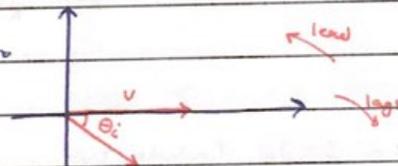

if  $\theta_v = 30^\circ$

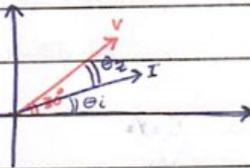


\*  $Z = R - jX \Rightarrow$  Capacitive load

$$= |Z| \angle \theta_z$$

$\hookrightarrow \theta < 0$

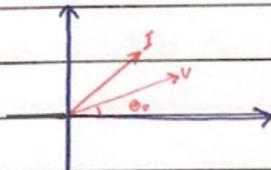
$I_2$  leads  $V_2$  by  $\theta_z = \theta_v - \theta_i$



⊕  $Z = R \Rightarrow$  Resistive load

$I_2$  in phase  $V_2 \Rightarrow \theta_v - \theta_i = 0$


$$\theta_v = \theta_i$$

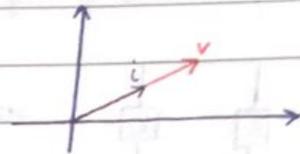

⊕  $Z = jX \Rightarrow$  pure inductor

$I_2 \times 90^\circ$


$I_2$  lags  $V$  by  $90^\circ$

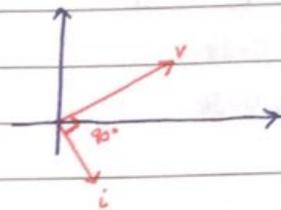

⊕  $Z = -jX \Rightarrow$  pure capacitor

$I_2 \times -90^\circ$

$I$  leads  $V$  by  $90^\circ$

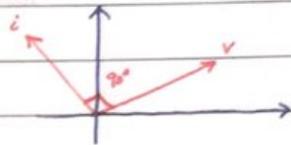

⊕ Admittance  $= Y = \frac{1}{Z}$

$$Z = R + jX \text{ (inductive)} \Rightarrow Y = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$$

$$Y = \frac{R - jX}{R^2 + X^2} = \frac{R}{R^2 + X^2} - j \frac{X}{R^2 + X^2} \text{ (inductive)}$$

$\underbrace{\hspace{2cm}}_G \quad \underbrace{\hspace{2cm}}_B$   
 (conductance)

$$Y = G - jB \text{ (inductive)}$$

$$Y = G + jB \text{ (capacitive)}$$

$$Y = G \text{ (Resistive)}$$


$$Y = -jB \text{ (pure inductor)}$$

$$Y = jB \text{ (pure capacitor)}$$

$$Y_{eq} \begin{cases} \rightarrow \text{parallel} = Y_1 + Y_2 \\ \rightarrow \text{series} = \frac{Y_1 Y_2}{Y_1 + Y_2} \end{cases}$$

\*  $f = \text{zero} \Rightarrow$  DC

Example:

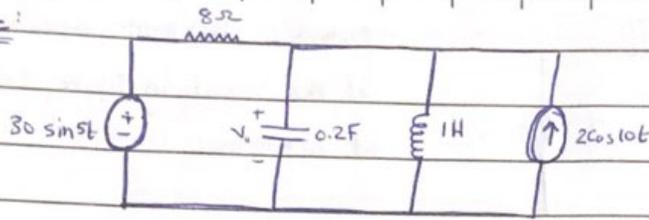


Calculate  $V_o$ ?

# We can use the superposition method ONLY because the sources are with different frequencies. #

Answer:

phasor:

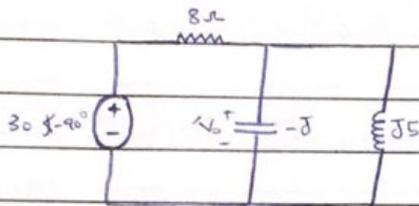① Kill current source  $\Rightarrow$  ~~short~~ open circuit.



$$30 \sin 5t \Rightarrow \omega = 5 \text{ rad/s}$$

$$30 \sin 5t = 30 \cos(5t - 90^\circ) = 30 \angle -90^\circ$$


$$C = 0.2F \Rightarrow Z_c = \frac{1}{j(5)(0.2)} = -j \Omega$$

$$L = 1H \Rightarrow Z_L = j(5) = j5 \Omega$$

$$(-j \parallel j5) \Rightarrow \frac{(-j)(j5)}{j4} = \frac{-j5}{4} = -j1.25 \Omega$$

$$V_o' = \left( \frac{-j1.25}{8 - j1.25} \right) (30 \angle -90^\circ) = 4.631 \angle -171.12^\circ$$

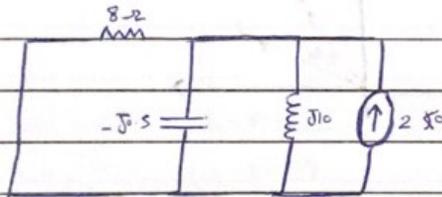② Kill voltage source  $\Rightarrow$  short circuit.



$$2 \cos 10t \Rightarrow \omega = 10 \text{ rad/s}$$

$$2 \cos 10t = 2 \angle 0^\circ$$

$$Z_c = \frac{-j}{(10)(0.2)} = -j0.5 \Omega$$


$$Z_L = j10 \Omega$$

$$(8 \parallel j10) \Rightarrow \frac{(8)(j10)}{8 + j10} = \frac{j80}{8 + j10}$$

$$V_o'' = \left( \frac{j80 / (8 + j10)}{-j0.5} \right) (2 \angle 0^\circ) = 1.05 \angle -86.24^\circ$$
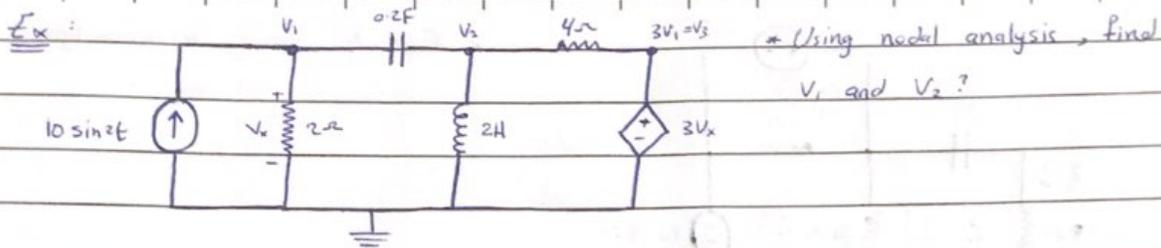
#  $V_o = V_o' + V_o'' \Rightarrow$  time domain phasor to time domain phasor  
 • using frequencies phasor





Answer:

$$10 \sin 2t \Rightarrow \omega = 2 \text{ rad/s}$$

$$10 \sin 2t = 10 \cos(2t - 90^\circ) = 10 \angle -90^\circ$$

$$0.2F \Rightarrow \frac{1}{j(\omega)(2)} = -j2.5 \Omega$$

$$2H \Rightarrow j(2)(2) = j4$$

by nodal:

$$V_1 \left( \frac{1}{2} + \frac{1}{-j2.5} \right) - V_2 \left( \frac{1}{-j2.5} \right) = 10 \angle -90^\circ \dots \textcircled{1}$$

$$V_1 (0.5 + j2.5) - j0.4 V_2 = -j10$$


$$V_2 = \frac{V_1(0.5 + j2.5) + j10}{j0.4}$$

$$V_2 \left( \frac{1}{-j2.5} + \frac{1}{j4} + \frac{1}{4} \right) - V_1 \left( \frac{1}{-j2.5} \right) - 3V_1 \left( \frac{1}{4} \right) = 0 \dots \textcircled{2}$$

$$V_1(t) = 11.32 \sin(2t + 60.01^\circ)$$

$$V_2(t) = 33.02 \sin(2t + 57.12^\circ)$$

Ex:

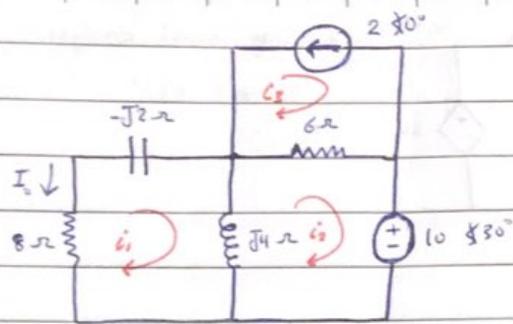

\* Find  $I_o$  using mesh analysis:

Answer:

$$i_2 = -2 \angle 0^\circ$$

$$i_1(8 - j2 + j4) - i_2(j4) = 0$$

$$i_1(8 + j2) - i_2(j4) = 0$$


$$i_2 = \frac{i_1(8 + j2)}{j4} = i_1(-j2 + 0.5) \dots \textcircled{1}$$

$$i_2(j4 + 6) - i_1(j4) - i_3(6) = -10 \angle 30^\circ$$

Find  $i_1$


$$\Rightarrow I_o = -i_1 = 1.194 \angle 65.44^\circ$$

Ex:

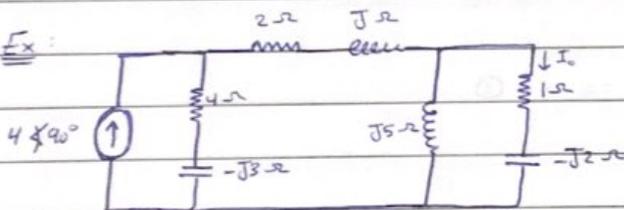

\* Find  $I_o$  using source transformation:

Answer:

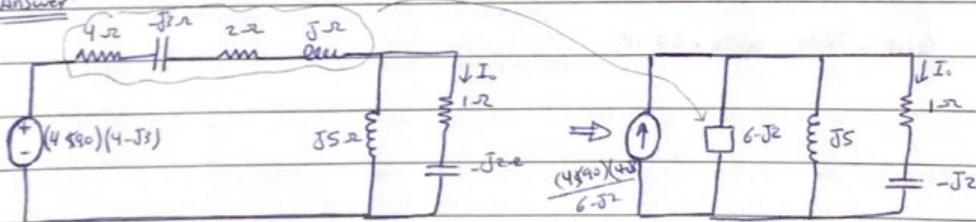

by current division find  $I_o$

$$I_o = 3.288 \angle 99.46^\circ$$

⊙ Thevenin and Norton equivalent:

$Z_{th} \Rightarrow$  Kill all sources

V.S  $\rightarrow$  S.C


C.S  $\rightarrow$  O.C

$V_{th} = V_{o.c}$

$I_N = I_{s.c}$


$$\Rightarrow \frac{V_{o.c}}{I_{s.c}} = Z_{th} = Z_N$$

Example:

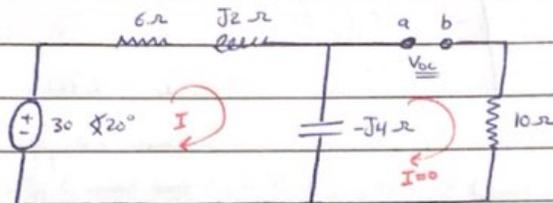

\* Find the Thevenin equivalent at terminals a-b

Answer:

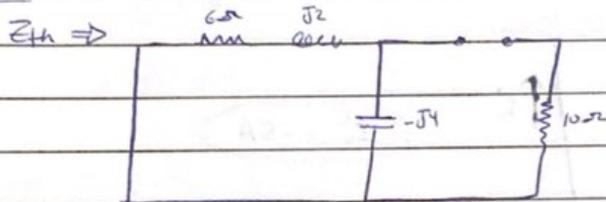

$(6, j2) \Rightarrow$  series

$$6 + j2$$


$(6 + j2, -j4) \Rightarrow$  parallel  $\Rightarrow$  series with  $10\Omega$

$$Z_{th} = \frac{(6 + j2)(-j4)}{6 - j2} + 10 = 12.4 - j3.2$$

$V_{th} \Rightarrow$  by KCL

$$I = \frac{30 \angle 20^\circ}{6 - j2}$$
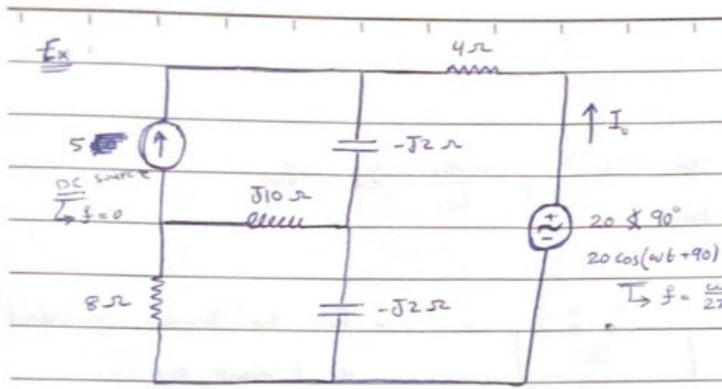
$$V_{th} = V_{o.c} = V_{-j4} = (-j4) \left( \frac{30 \angle 20^\circ}{6 - j2} \right) = 18.97 \angle -51.57^\circ$$



find  $I_o$ :


Note that the 2 sources have different frequencies.  
 ↳ by superposition only

$$I_o = I_o'(t) + I_o''(t)$$

phasor & time domain  
 ←  
 ←  
 ←


⊗ Kill the voltage source ⇒ short circuit

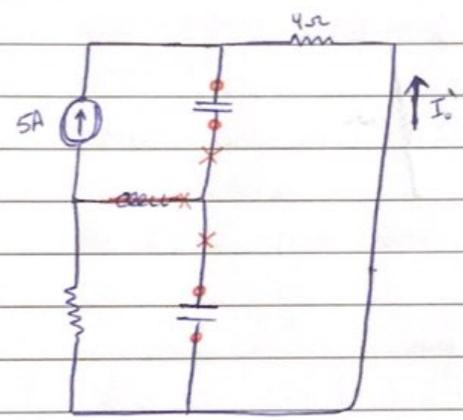$L \Rightarrow S.C$      $C \Rightarrow O.C$



$$I_o' = -5A$$

⊙ Kill the current source ⇒ open circuit

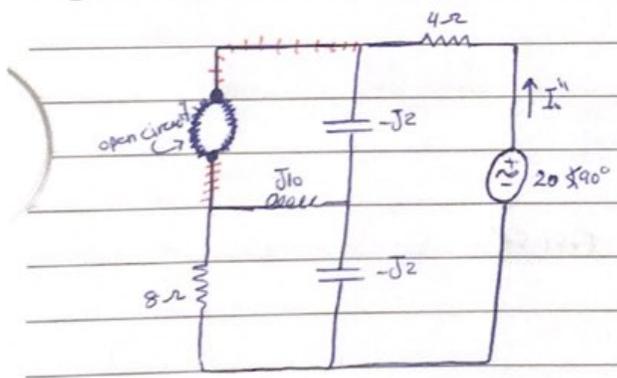

$(8, j10) \rightarrow$  series

$$8 + j10$$

$(8 + j10, -j2) \rightarrow$  parallel

$$\frac{(8 + j10)(-j2)}{8 + j8} \Rightarrow \text{series with } -j2 \text{ \& } 4\Omega$$


$$Z = 0.25 - 2.25j - 2j + 4$$

$$Z = 4.25 - j4.25$$

$$I_o'' = \frac{20 \angle 90^\circ}{4.25 - j4.25} = -2.35 + j2.35 = 3.3 \angle 135.3^\circ$$

$$I_o = I_o' + I_o'' = -5 + 3.3 \angle 135.3^\circ$$

Fix:

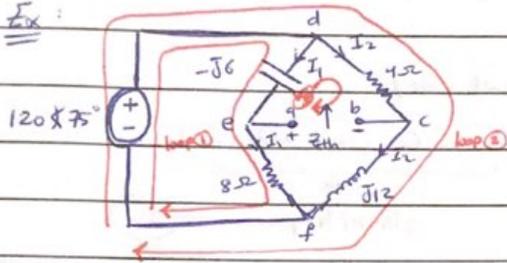

Find  $Z_{th}$   $\uparrow$   $V_{oc}$  seen from ab:

$$(-j6, 8) \rightarrow \text{parallel}$$

$$(4, j12) \rightarrow \text{parallel}$$

$$\frac{(-j6)(8)}{8-j6} = 2.88 - j3.84$$

series  $\Leftrightarrow$

$$\frac{(4)(j12)}{4+j12} = 3.6 + j1.2$$

$$Z_{th} = 2.88 - j3.84 + 3.6 + j1.2 = 6.48 - j2.64$$

$$\text{Loop (1)} \Rightarrow I_1 = \frac{120 \angle 75^\circ}{8-j6} = -4.47 + j11.1$$

$$\text{Loop (2)} \Rightarrow I_2 = \frac{120 \angle 75^\circ}{4+j12} = 9.47 + j0.57$$

$$\text{loop (3)} \Rightarrow I_2(4) - V_{oc} - I_1(-j6) = 0$$

$$V_{oc} = 4(9.47 + j0.57) - (-4.47 + j11.1)(-j6)$$

$$= (37.88 + j2.28) - (66.6 + j26.82) = -28.72 - j24.54$$

$$I_N = I_{sc} = \frac{V_{th}}{Z_{th}} = \frac{-28.72 - j24.54}{6.48 - j2.64} = -5.12 - j1.7$$

⊕ Instantaneous and Average power:

$$p(t) = v(t) i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

same as  $P_{avg}$ .

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

(active or real power):  $\begin{matrix} \nearrow \text{inductance} \\ \searrow \end{matrix}$

Constant power

sinusoidal power at  $2\omega$

$\hookrightarrow$  2 periods  $\rightarrow 1T$

$$P_{max} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \quad \text{such that } [\cos(2\omega t + \theta_v + \theta_i) = 1]$$

$$P_{min} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) - \frac{1}{2} V_m I_m \quad \text{such that } [\cos(2\omega t + \theta_v + \theta_i) = -1]$$

$$\text{peak to peak value} = P_{max} - P_{min} = V_m I_m$$

$p(t) > 0 \Rightarrow$  absorbed power by the circuit

$p(t) < 0 \Rightarrow$  absorbed power by the source.

⊕ In  $P_{avg}$ :  $P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$

$\theta_v - \theta_i > 0 \Rightarrow i$  lags  $v \Rightarrow$  inductive load  $\Rightarrow P_{avg} > 0$

$\theta_v - \theta_i < 0 \Rightarrow i$  leads  $v \Rightarrow$  capacitive load  $\Rightarrow P_{avg} > 0$

$\theta_v = \theta_i \Rightarrow i$  &  $v$  in phase  $\Rightarrow$  resistive load  $\Rightarrow P_{avg} = \frac{1}{2} V_m I_m$

$\theta_v - \theta_i = \pm 90 \Rightarrow$   $\begin{matrix} \leftarrow \text{pure inductance} \\ \leftarrow \text{pure capacitor} \end{matrix} \Rightarrow P_{avg} = \text{Zero}$

$Z_L = Z_{Th}^* \Rightarrow$  maximum average power


$$P_{max} = \frac{V_{Th}^2}{8R_{Th}}$$

⊛ Complex power:

$$S = \text{Complex power} = |S| \angle \theta_s \Rightarrow \text{unit (V.A)}$$

$$\vec{I} \rightarrow \text{Apparent power} = \frac{1}{2} |V_m| |I_m| \angle (\theta_v - \theta_i) = \frac{1}{2} \vec{V} \vec{I}^*$$

in Rectangular form  $\Rightarrow S = |S| \cos \theta_s + j |S| \sin \theta_s$

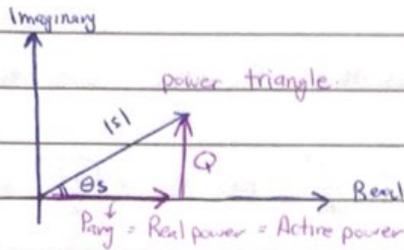

$$|S| = \sqrt{P^2 + Q^2}$$

$$S = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + j \frac{1}{2} V_m I_m \sin(\theta_s)$$

$P_{avg} \Rightarrow \text{unit (watt)}$      $Q = \text{reactive power} \Rightarrow \text{unit (V.Ar)}$

$$\otimes \text{ Power factor} = PF \triangleq \frac{P_{avg}}{|S|} = \frac{\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)}{\frac{1}{2} V_m I_m} = \cos(\theta_v - \theta_i)$$

$$-90^\circ < \theta_v - \theta_i < 90^\circ \Rightarrow 0 < \text{power factor} < 1$$

⊛ if power factor = 1  $\Rightarrow$  unity power factor

$$\theta_v - \theta_i > 0 \Rightarrow i \text{ lags } v \Rightarrow \text{Inductive} \Rightarrow PF < 0$$


$$\theta_v - \theta_i < 0 \Rightarrow i \text{ leads } v \Rightarrow \text{capacitive} \Rightarrow PF < 0$$

$$\theta_v - \theta_i = 0 \Rightarrow \text{pure resistive} \Rightarrow PF = 1$$

$$\theta_v - \theta_i = \pm 90 \Rightarrow PF = 0 \text{ (the worst case)}$$

⊛  $\Rightarrow$  zabi p'az p'az i'az u'az  
 b' t'az b' i, PF j' i'az  
 leading j' lagging
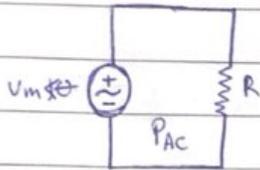
$$\otimes \text{ Root mean square} = RMS = \sqrt{\frac{1}{T} \int_0^T v^2 dt} = \text{Volts (Vrms)}$$




$$P_{avg} = \frac{1}{2} V I \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} V \left(\frac{V}{R}\right) (1)$$

↳ because it is a pure resistance.

$$P_{avg} = \frac{1}{2} \frac{V^2}{R}$$

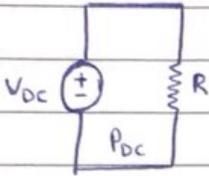

find  $(V_{DC})$  such that  $P_{AC} = P_{DC}$  with the same  $R$ ?

$$P_{DC} = \frac{V_{DC}^2}{R} = \frac{1}{2} \frac{V^2}{R} \Rightarrow V_{DC} = \sqrt{\frac{V^2}{2}} = \frac{V_m}{\sqrt{2}} = V_{rms}$$

\* RMS:


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$|S| = \frac{1}{2} V_m I_m = |V_{rms}| |I_{rms}|$$
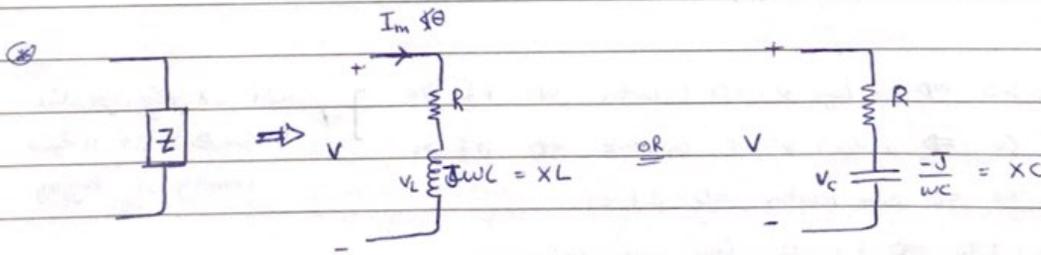
$$Q = \frac{1}{2} V_m I_m \sin \theta_s = V_{rms} I_{rms} \sin \theta_r$$



$$P_{avg} = \frac{1}{2} |I_m|^2 R = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

$$Q = \frac{1}{2} |I_m|^2 X = I_{rms}^2 X = \frac{|V_{rms}|^2}{X}$$

or


$$= -\frac{|V_{rms}|^2}{X}$$

$$S = (|V_{rms}| \angle \theta_v) (|I_{rms}| \angle \theta_i) = V_{rms} I_{rms} \angle \theta_v - \theta_i$$

\*  $\text{P}_{\text{avg}}$  و  $\text{Q}$  و  $\text{S}$  power ال  $\text{z}$   $\text{z}$  \*

## Three phase

Y-Connection sources:

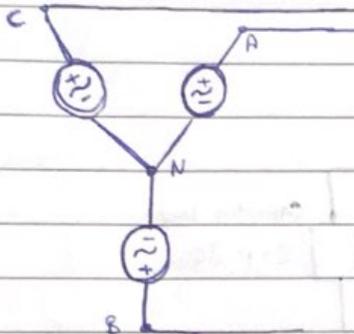


$$V_{AN} = V_{phase}$$

$$V_{AB} = V_{LL} \text{ (line to line)}$$

$$[V_{LL} > V_{phase}]$$

$$\left. \begin{aligned} V_{phase} \Rightarrow V_{AN} &= |V_p| \angle \theta_p \\ &= V_{BN} = |V_p| \angle \theta_p - 120^\circ \\ &= V_{CN} = |V_p| \angle \theta_p + 120^\circ \end{aligned} \right\} \Rightarrow \Sigma = \text{Zero}$$

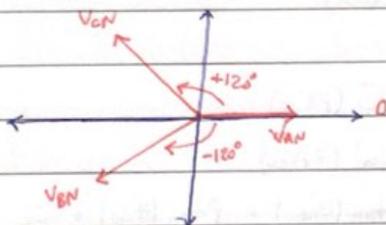

ABC  $\Rightarrow$  positive sequence  
(PCCS)

$$V_{LL} \Rightarrow V_{AB} = |V_{LL}| \angle \theta_{AB}$$

$$V_{BC} = |V_{LL}| \angle \theta_{AB} - 120^\circ$$


$$V_{CA} = |V_{LL}| \angle \theta_{AB} + 120^\circ$$

In a balanced system:

$$\frac{V_p}{V_{AN} = |V_p| \angle \theta_p} \Rightarrow \frac{V_{LL}}{V_{AB} = \sqrt{3} |V_p| \angle \theta_p + 30^\circ}$$

$$V_{BN} = |V_p| \angle \theta_p - 120^\circ \Rightarrow V_{BC} = \sqrt{3} |V_p| \angle \theta_p - 120^\circ + 30^\circ$$

$$V_{CN} = |V_p| \angle \theta_p + 120^\circ \Rightarrow V_{CA} = \sqrt{3} |V_p| \angle \theta_p + 120^\circ + 30^\circ$$

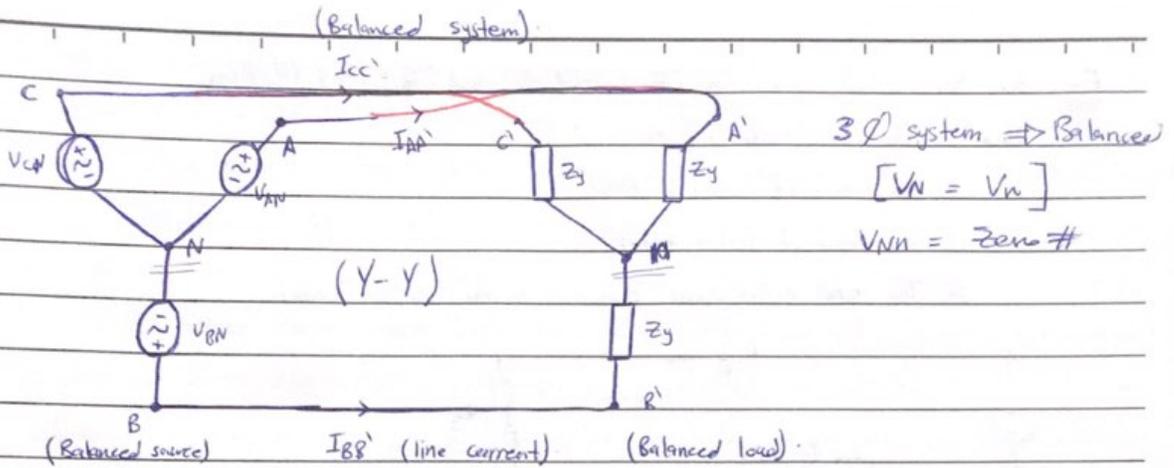


\* Line currents:

$$I_{AA'} = |I_{line}| \angle \theta_{line}$$

$$I_{BB'} = |I_{line}| \angle \theta_{line} - 120^\circ$$

$$I_{CC'} = |I_{line}| \angle \theta_{line} + 120^\circ$$

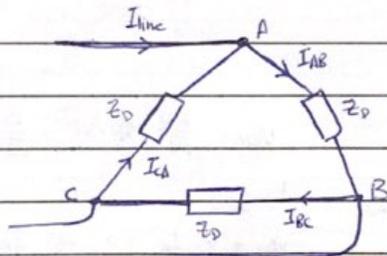\* phase current  $\Rightarrow$  in delta connection:



$$I_{AB} = |I_d| \angle \theta_d$$

$$I_{BC} = |I_d| \angle \theta_d - 120^\circ$$

$$I_{CA} = |I_d| \angle \theta_d + 120^\circ$$

$I_{phase}$

$$I_{AB} = |I_d| \angle \theta_{AB}$$

$$I_{BC} = |I_d| \angle \theta_{AB} - 120^\circ$$

$$I_{CA} = |I_d| \angle \theta_{AB} + 120^\circ$$

$I_{line}$

$$I_{AA'} = \sqrt{3} |I_{AB}| \angle \theta_{AB} - 30^\circ$$

$$I_{BB'} = \sqrt{3} |I_{BC}| \angle \theta_{BC} - 120^\circ - 30^\circ$$

$$I_{CC'} = \sqrt{3} |I_{CA}| \angle \theta_{CA} + 120^\circ - 30^\circ$$

by KCL @ node A:

$$I_{line} = I_{AB} - I_{CA}$$

\* Power in 3 phase:


$$P_{3\phi} = 3 P_{1\phi}$$

$$Q_{3\phi} = 3 Q_{1\phi}$$

$$S_{3\phi} = 3 S_{1\phi}$$

Ex For the circuit shown, if  $(Z_Y = 4 + j3)\Omega$  and  $(I_B = |I_B| \angle \theta) \text{ Arms}$ .


- Find:
- ① The power factor of the load.
  - ② The value of  $|I_B|$  (in Arms).
  - ③ The value of  $\theta$  (in degree).
  - ④ The total active power consumed by the load (in watt).

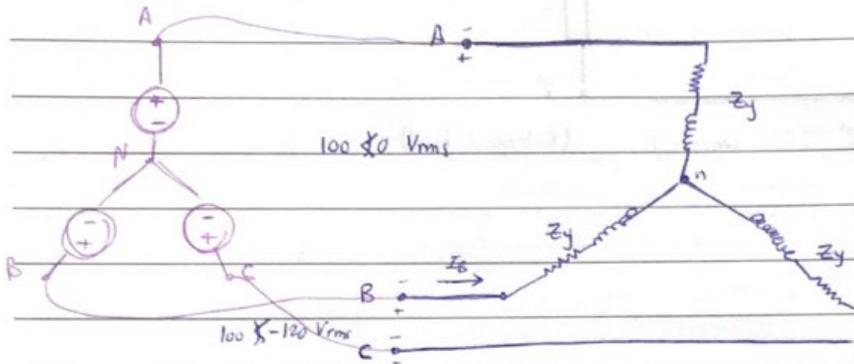

Answer:

$$\textcircled{1} \text{ PF} = \cos(\theta_2) \quad Z_Y = 5 \angle 36.87^\circ$$
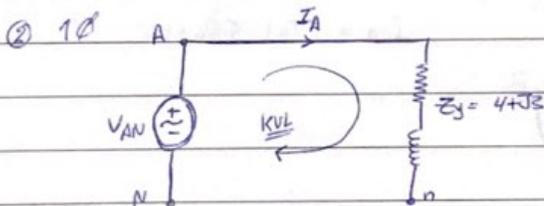
$$= \cos(36.87^\circ) = 0.8 \text{ lagging.}$$



$$V_{AN} = \frac{100}{\sqrt{3}} \angle 0 - 30^\circ = \frac{100}{\sqrt{3}} \angle -30^\circ$$

by KVL

$$-V_{AN} + Z_Y I_A = 0 \Rightarrow I_A = \frac{V_{AN}}{Z}$$

$$I_A = \frac{\frac{100}{\sqrt{3}} \angle -30^\circ}{4 + j3} = 11.46 - j1.38$$

$$I_A = 11.54 \angle -6.87^\circ$$

$$I_B = |I_A| \angle \theta_A - 120^\circ = 11.54 \angle -126.87^\circ$$

$$P_A = \frac{2}{\sqrt{3}} (V_{\text{rms}} \cos(\theta_v - \theta_i)) = \frac{2}{\sqrt{3}} \left( \frac{100}{\sqrt{3}} \right) (11.54) \cos(-30 + 6.87) = 612.7 \text{ watt.}$$

$$P \text{ for } 3\phi = 3P_A = 3 \left( \frac{612.7}{\sqrt{3}} \right) = 1838 \text{ watt.}$$

$$\text{OR } P_{1\phi} = I_{\text{rms}}^2 R = \left( \frac{100}{\sqrt{3}} \right)^2 (4)$$

$$P_{3\phi} = 3P_{1\phi}$$

$$Q_{1\phi} = I_{\text{rms}}^2 X$$

$$Q_{3\phi} = 3Q_{1\phi}$$


$$S_{1\phi} = VI^* = \left( \frac{100}{\sqrt{3}} \angle -30^\circ \right) \left( \frac{100}{\sqrt{3}} \angle (30 - \cos^{-1}(\frac{4}{5})) \right)^*$$

$$S_{3\phi} = 3S_{1\phi} = 3 \left( \dots \right)$$

$$S = P + jQ$$

Ex: The figure shows a phasor diagram for a circuit. The voltage and the current scales are 1V/division and 1A/division respectively and  $i(t) = I \cos(\omega t + \theta_i)$  and  $v(t) = V \cos(\omega t + \theta_v)$ .

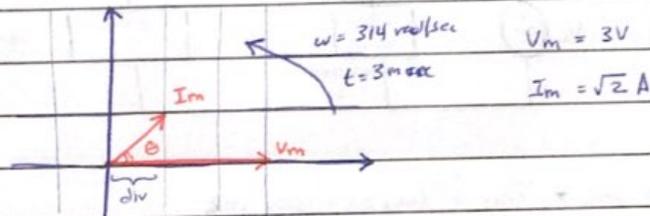- Find:
- ① The value of  $I$ .
  - ② The value of  $\theta_v$
  - ③ The apparent power consumed by the circuit (in VA)
  - ④ The power factor of the circuit



①  $I = \sqrt{2} \text{ A}$

②  $\omega t + \theta_v = 0$  |  $t = 3 \text{ ms}$

$$\theta_v = -\omega t = -(314)(3 \text{ ms}) = -0.942 \text{ rad} * \frac{180}{\pi} = -54^\circ$$

$$\theta_z = \theta_v - \theta_i = -45^\circ \quad (i \text{ leads } v \text{ by } 45^\circ)$$

$$\theta_i = -54 + 45 = -9^\circ$$

OR

$$\omega t + \theta_i = 45$$

$$(314)(3 \text{ ms}) \left( \frac{180}{\pi} \right) + \theta_i = 45$$

$$\theta_i = 45 - 54 = -9^\circ$$

③  $|S| = \frac{1}{2} |V_m| |I_m| = \frac{1}{2} (3)(\sqrt{2}) = \frac{3}{\sqrt{2}}$

$$\vec{S} = \frac{1}{2} \vec{V} \vec{I}^* = \frac{1}{2} (3 \angle -54) (\sqrt{2} \angle -9)^* = 1.5\sqrt{2} \angle -45$$

$$P = 1.5\sqrt{2} \cos(-45) = 1.5 \text{ W}$$

$$Q = 1.5\sqrt{2} \sin(-45) = -1.5 \text{ VAR} \Rightarrow \text{capacitive load}$$

④  $\text{pf} = \cos(-45) = 0.707 \text{ leading}$

$$Z = \frac{V}{I} = \frac{3 \angle -54}{\sqrt{2} \angle -9} = \frac{3}{\sqrt{2}} \angle -45^\circ$$


Ex: For the circuit shown, if  $V_s = 100 \angle 0^\circ$  Vrms and  $I_s = 30 \angle -30^\circ$  Arms

Find: ① The apparent power supplied by the source

② The reactive power supplied by the source

③ The value of  $P_2$  (watt)

④ The value of  $Q_3$  (VAR)

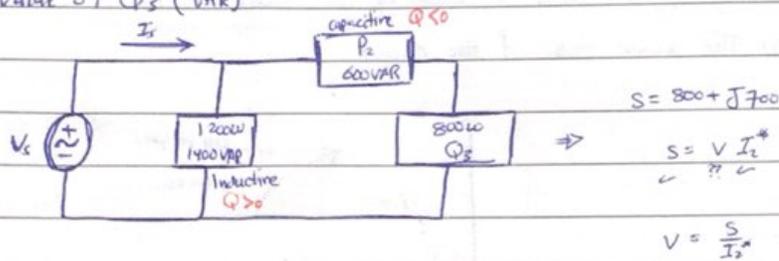

Answer

①  $|S| = V_{rms} * I_{rms} = (100)(30) = 3000 \text{ VA}$

②  $\vec{S} = \vec{V}_{rms} * \vec{I}_{rms}^*$   
 $= (100 \angle 0^\circ)(30 \angle -30^\circ)^* = 3000 \angle 30^\circ \text{ VA}$

$S_{\text{source}} = 2598 + j1500$

③  $\sum P_{\text{supplied}} = \sum P_{\text{consumed}}$

$2598 = 1200 + P_2 + 800$

$P_2 = 598 \text{ watt}$

④  $\sum Q_{\text{supplied}} = \sum Q_{\text{consumed}}$

$1500 = 1400 - 600 + Q_3$


$Q_3 = +700 \text{ VAR} \Rightarrow$  Inductive load.

$I_1 \Rightarrow S_1 = 1200 + j1400 = 1844 \angle 49.4^\circ = V_{rms} * I_{rms}^*$

$\Rightarrow I_{rms} = \left(\frac{S_1}{V}\right)^* = \left(\frac{1844 \angle 49.4^\circ}{100 \angle 0^\circ}\right)^* = 18.44 \angle -49.4^\circ$

$I_2 = I_s - I_1 = (30 \angle -30^\circ) - (18.44 \angle -49.4^\circ)$

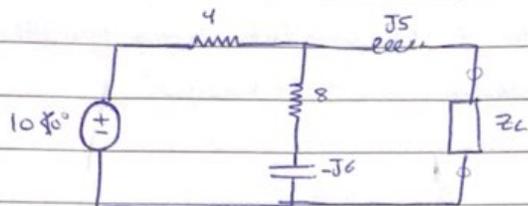Ex: Find  $Z_L$  which transfer the maximum power from ckt: & find the  $P_{max}$ ?



Answer:

$$\textcircled{1} Z_L = Z_{Th}^*$$

$$\textcircled{2} P_{max} = \frac{|V_{Th(m)}|^2}{8 R_{Th}} \Rightarrow \text{Note that } V_{Th} = V_m \text{ NOT } V_{rms}$$

$$(4 \parallel 8 - j6)$$

$$\frac{(4)(8 - j6)}{12 - j6} + j5 = 2.93 + j4.47$$

$$V_{oc} = \left( \frac{8 - j6}{12 - j6} \right) (10\angle 0^\circ) = 7.33 - j1.33$$


$$= 7.45 \angle -10.23^\circ$$

$$Z_L = Z_{Th}^* = 2.93 - j4.47$$



$\xrightarrow{R_{Th}}$

$$P_{max} = \frac{(7.45)^2}{8(2.93)} = 2.37 \text{ watt.}$$

(Y-Y) connection:

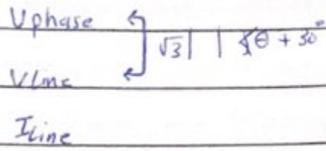

(Y-Δ) connection:

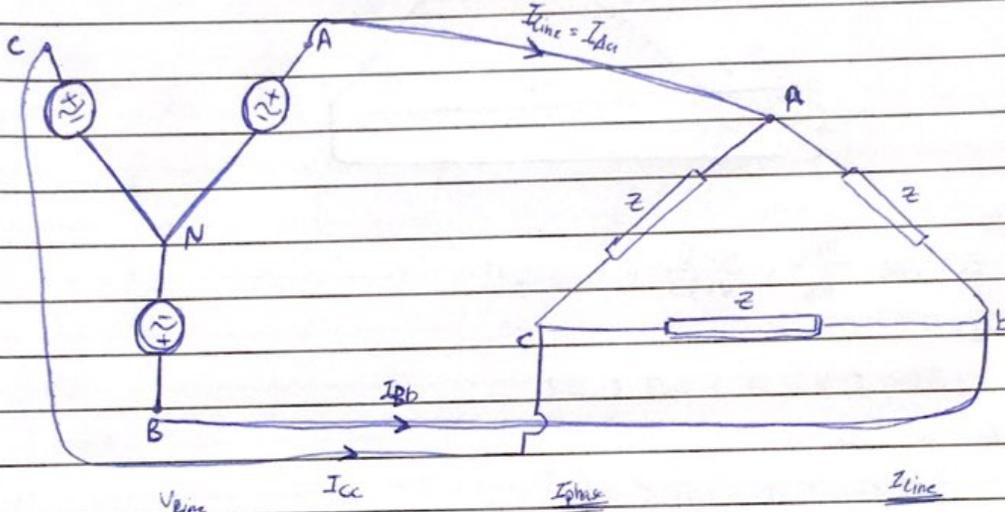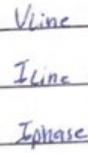

$V_{ab} = | | \angle \theta$   
 $V_{bc} = | | \angle \theta - 120^\circ$   
 $V_{ca} = | | \angle \theta + 120^\circ$

$I_{ab} = | | \angle \theta_{ab}$   
 $I_{bc} = | | \angle \theta_{ab} - 120^\circ$   
 $I_{ca} = | | \angle \theta_{ab} + 120^\circ$


$I_{Aa} = | I_{ab} | \sqrt{3} \angle \theta_{ab} - 30^\circ$   
 $I_{Bb} = | I_{bc} | \sqrt{3} \angle \theta_{ab} - 120^\circ - 30^\circ$   
 $I_{Cc} = | I_{ca} | \sqrt{3} \angle \theta_{ab} + 120^\circ - 30^\circ$

Ex For the circuit shown, if  $(Z_A = 4 + j3) \Omega$  and  $(I_B = |I_B| \angle \theta) \text{ Arms}$ .

Find: (1) The value of  $|I_B|$  (in Arms).

(2) The value of  $\theta$  (in degree).

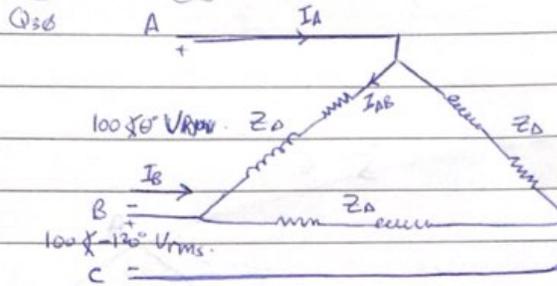(3) The (total) reactive power consumed by the load (in VAR)



Answer:

$$I_B = I_{AB} = \frac{V_{AB}}{Z_A} = \frac{100 \angle 0^\circ}{4 + j3} = 20 \angle -36.7^\circ$$

$$I_A = \sqrt{3} |I_B| \angle \theta_{I_A} - 30^\circ$$

$$= \sqrt{3} (20) \angle -36.7 - 30 = 20\sqrt{3} \angle -66.7^\circ$$

(1)  $I_B = |I_B| \angle \theta_{I_B} - 120^\circ$

$$= 20\sqrt{3} \angle -66.7 - 120 = 20\sqrt{3} \angle -186.7^\circ$$

(2)  $Q_{1\phi} = I_B^2 X = (20)^2 (3) = 1200 \text{ VAR}$

$Q_{3\phi} = 3 Q_{1\phi} = 3(1200) = 3600 \text{ VAR}$

(4) Total complex power:

$$S_{3\phi} = P_{3\phi} + jQ_{3\phi}$$

$$P_{1\phi} = I^2 R = (20)^2 (4) = 1600 \text{ watt}$$

$$P_{3\phi} = 3 P_{1\phi} = 3(1600) = 4800 \text{ watt}$$

$$S_{3\phi} = 4800 + j3600$$

OR

$$S_{1\phi} = VI^* = (100 \angle 0^\circ)(20 \angle -36.7^\circ)^*$$

$$= 2000 \angle 36.7^\circ$$


$$S_{3\phi} = 3 S_{1\phi} = 3(2000 \angle 36.7^\circ) = 6000 \angle 36.7^\circ$$

(5) Power factor of the load  $\Rightarrow \text{pf} = \cos(\theta_z) = \cos(36.7) = 0.8$  lagging.

(6) Apparent power  $= |S| = 6000 \text{ VA}$

Ex: From the circuit below:

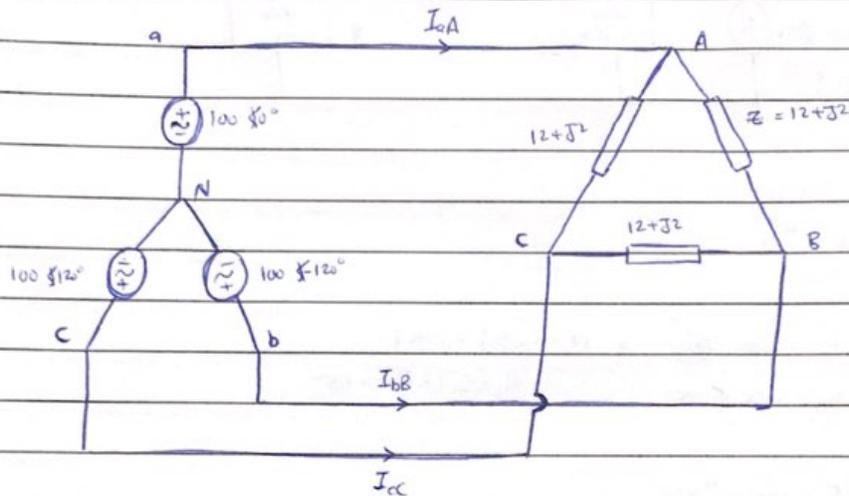Find: (1)  $I_{aA}$  (2)  $I_{cC}$  (3) Complex power consumed by the load (4) PF load



Answer:

$$\textcircled{1} V_{an} = 100 \angle 0^\circ \Rightarrow V_{AB} = |V_{an}| \times \sqrt{3} \angle \theta_{an} + 30^\circ = 100\sqrt{3} \angle 30^\circ$$

$$I_{AB} = \frac{V_{AB}}{Z} = \frac{100\sqrt{3} \angle 30^\circ}{12 + j2} = \frac{100\sqrt{3}}{12.2} \angle 20.5^\circ$$

$$I_{aA} = \sqrt{3} I_{AB} \angle \theta_{AB} - 30^\circ = \sqrt{3} \left( \frac{100\sqrt{3}}{12.2} \right) \angle 20.5 - 30^\circ$$

$$\textcircled{2} I_{cC} = |I_{aA}| \angle \theta_{aA} + 120^\circ = \sqrt{3} \left( \frac{100\sqrt{3}}{12.2} \right) \angle -9.5 + 120^\circ$$

$$\textcircled{3} S_{1\phi} = V_{AB} I_{AB}^* = (100\sqrt{3} \angle 30^\circ) \left( \frac{100\sqrt{3}}{12.2} \angle 20.5 \right)^*$$

$$S_{3\phi} = 3 S_{1\phi} = 3 \left( 100\sqrt{3} \angle 30^\circ \right) \left( \frac{100\sqrt{3}}{12.2} \angle 20.5 \right)^* \text{ VA}$$

$$\textcircled{4} \text{PF} = \cos(\theta_2) = \cos(9.5) = 0.986 \text{ lagging.}$$

Find  $I_{AC} = ?$

$$I_{AC} = -I_{CA}$$


$$I_{CA} = |I_{AB}| \angle \theta_{AB} + 120^\circ$$

$$= \frac{100\sqrt{3}}{12.2} \angle 20.5 + 120^\circ$$

$$I_{AC} = \left( \frac{100\sqrt{3}}{12.2} \right) \angle 20.5 + 120^\circ \xrightarrow{\uparrow 180^\circ}$$

$$I_{AC} = \frac{100\sqrt{3}}{12.2} \angle 20.5 + 120 - 180^\circ$$

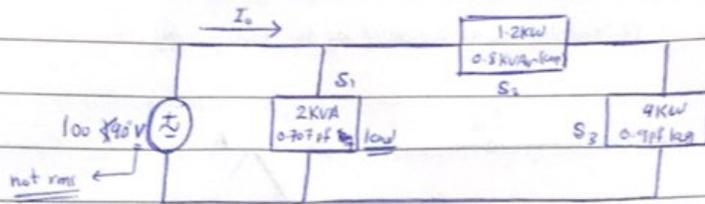Ex: From the circuit below, find  $I_0$  and the overall complex power supplied.



$$S_{total} = S_1 + S_2 + S_3$$

$$S = V I_0^*$$

$$S_1 = 2000 \angle -45^\circ \rightarrow \text{PF} = \cos(\theta_1) = 0.707$$

$$S_1 = 2000 \angle -45^\circ \quad \theta_1 = \cos^{-1}(0.707) = -45^\circ$$

$$S_2 = 1200 - j800$$

$$S_2 = 1442.2 \angle -33.69^\circ$$


$$S_3 \Rightarrow P = 4000 \text{ watt}$$

$$\text{PF} = \cos^{-1}(0.9) = +25.8^\circ$$

$$\cos(25.8^\circ) = \frac{4000}{|S|}$$

$$|S| = 4442.87$$

$$S_3 = 4442.87 \angle 25.8^\circ$$

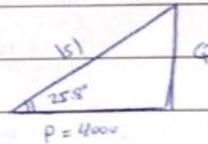

$$S_{total} = (2000 \angle -45^\circ) + (1442.2 \angle -33.69^\circ) + (4442.87 \angle 25.8^\circ)$$

$$I_0 = \left( \frac{S_{total}}{V} \right)^*$$