

\* Machines → Motors  
↳ Generators

→ They both can be AC or DC based machines.

\* A machine acts as a transformer: it transforms energy from a form to another.

↳ An electrical machine is a device that converts electrical energy to mechanical energy and vice versa.

↳ Motor: Electrical to Mechanical energy.

↳ Generator: Mechanical to Electrical energy.

Machines - Lecture 2

\* Motion → Linear motion. → Special type of motors (not common).

↳ Rotational motion. → Most motors works and uses the concept of rotational motion.

\* Machines have input and output power → we care about power when we consider the efficiency.

↳ In the ideal case, when a motor gets 40 Watts of power as an input, it must output an equivalent amount to it.

↳ While in reality, we have losses.

\* A transformer converts AC current from one voltage level to another.

low voltage high current → high voltage low current

\* From high-to-low ⇒ is called "Down transformer".

\* Examples of electrical machines:


Hard disk, cars motors, Air conditioner, ... [Ch1, slide 4].



Linear motion

Rotational motion.

Position  
[Displacement]

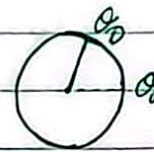

$$\Delta X = X_D - X_0$$

(m)

$$\Delta \theta = \theta_D - \theta_0$$

(rad)

→ when the motor keeps turning continuously,  $\theta$  is useless.

velocity

$$v = \frac{x}{t} \text{ (m/s)}$$

$$\omega \text{ (rad/sec)}$$

Acceleration

$$a = \frac{v_D - v_i}{t} \text{ (m/s}^2\text{)}$$

$$\alpha \text{ (rad/sec}^2\text{)}$$

Mass

$$m$$

$I \equiv$  Inertia

$$F = ma$$

$$\text{(Nm)} \tau = I\alpha$$

\* Inertia is not directly the mass, it depends on other things such as: the radius & the center of mass.

Work

$$Fd$$

$$\tau\theta$$

Kinetic energy

$$\frac{1}{2}mv^2$$

$$\frac{1}{2}I\omega^2$$

\*\* Power


$$Fv$$


$$\tau\omega$$


↳ 1 rotation =  $2\pi$   
(revolution per minute).



## \* Magnetic field basics:

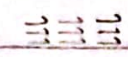→ Materials in nature can be: ① Natural magnets. 

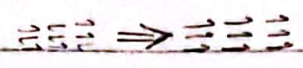Temporary  $\curvearrowright$  ② Ferromagnetic. 

③ Non-magnetic. 

advantage:

it's available

almost everywhere.

## \* Properties of magnetic field lines:

↳ From north to south outside of the magnet & from south to north inside it.

↳ 3D closed loop path.

↳ Stronger near the magnet.

## Quiz 1:

→ What is the difference between voltage electricity and a transformer?

Solution: The transformer converts AC current from one voltage level to another (high  $\rightarrow$  low or low  $\rightarrow$  high) to be used in electrical machines without harming them (ex: used in laptop chargers), while the electricity converts from AC to DC and vice versa.

→ Youtube video #1: Solenoid basics explained.

↳ Permanent magnet disadvantage:

You cannot control it → That's why Ferromagnetic materials

↳ Ampere's law are used more.

→ When a current passes through a wire, it creates a magnetic field

لذا يسهل ان يمدد سلك الجهد في كل loop في كل دائرة  $I$  و  $n$  (n-turns)

↳ Gives the same effect as a permanent magnet (From ferro to permanent).

→ To get the direction → Use right hand rule.

⇒ Solenoid valve: is used to control the current in a coil and therefore the magnetic material.

⇒ A current-carrying wire in the presence of a magnetic field has a force induced on it.

↳ Magnetic field + Induced force + Electric field.

current  $\times N$  : total current in coil  $\times$  current  $\times$  number of turns

$\times$  length of wire  $l$  :  $l$  length of wire

$\times$  Ferromagnetic material :  $\times$  Ferromagnetic material

يكون زيارته المغناطيسية  $\times$   $l$  :  $l$  length of wire (outside of the material)

↳ The air is considered as an isolator → air is not ferro

∴ The flux passes through the lower resistance which is through the ferro magnetic material. The flux that passes through the air is neglected since it's very low (very high resistance).




\*  $H = \frac{Ni}{L_c}$

→ The flux is similar to the current.

→ The wire acts as a battery.

→ The current is similar to  $N \times i$ .

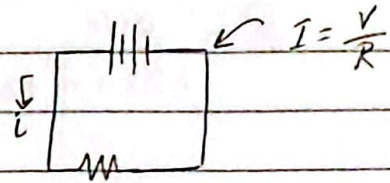→ The resistance is similar to the reluctance.



→ Magnetic field strength (H) is similar to the Electric field strength.

\* Magnetic Flux density (B) =  $\Phi/A$  (Tesla).

\* Permeability ( $\mu$ ) =  $B/H$ .

↳  $\mu_0$  is the permeability of the air =  $4\pi \times 10^{-7}$

↳  $\mu_r$  is the relative permeability, the higher it gets the higher the magnetic flux passes through the material.

↳  $\mu_r = \mu/\mu_0$

⊠ Magneto Motive Force MMF: is equivalent to the Electro Motive Force.

Permeability  $\mu$ , MMF, and magnetic field strength  $H$ .

→  $H$  is the magnetic field strength, and  $\mu$  is the permeability.

→  $\mu$  is the permeability, and  $H$  is the magnetic field strength.

→ Reluctance =  $\frac{L_c}{\mu A}$

⊠  $F = \Phi R = NI$

سببها: التفاعل الأحيائي الذي يجرى

بالطارية ينتج عنه قوة دافعة

كهربائية تكون لها القدرة على

الدفعونات تنقل عبر البطارية لتولد

التيار.

\* كيف يمكن أن تزيد ال  $\Phi$  ؟ ① بزيادة عدد اللفات بال coil.

② بزيادة material المتأصلة بغيرها أو أنه في غير سائر الأعلى.



Example 1 slide 14: Another possible ~~solution~~ way to solve:



$$R = \frac{0.16}{1.818 \times 10^{-3} \times 2 \times 10^{-3}} = \frac{8}{1.818} \times 10^4 = 4.4 \times 10^4 \text{ AT/Wb}$$

$$4 \times 10^{-4} \times 4.4 \times 10^4 = N_i$$

$$N_i = 17.6$$

$$\Rightarrow I = \frac{17.6}{400} = \boxed{44 \text{ mA}}$$


$\Rightarrow$  Other possible questions:

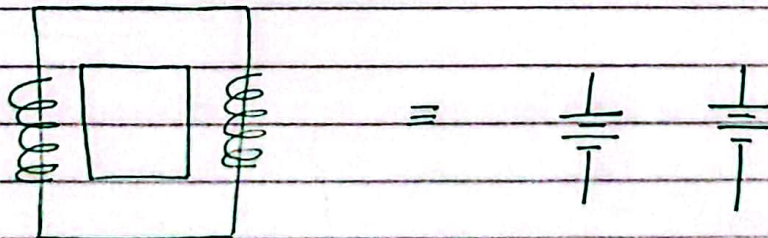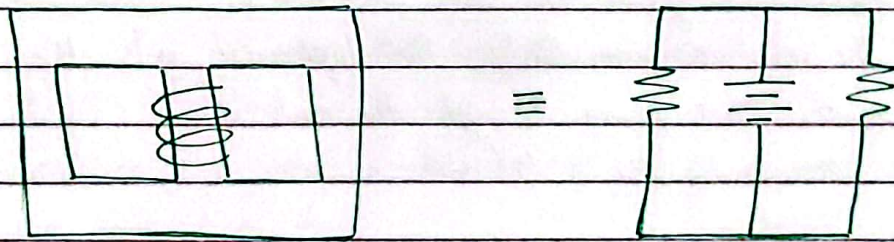

Quiz 2: From the same example in slide 14 but:  $\phi = 8 \times 10^{-4}$ ,  
Find the radius:

Answer:  $L_c = 2\pi r$ , given  $L_c = 0.16$

$$\therefore r = \frac{0.16}{2\pi}$$

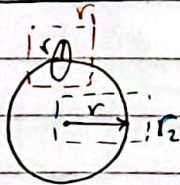

→ In the previous example, there are two  $r$  in it:

$$r_1 \Rightarrow A = \pi r^2$$

$$A = 2 \times 10^{-3} \Rightarrow \text{we can find } r_1.$$


$$r_2 \Rightarrow L_c = 2\pi r$$

$$L_c = 0.16 \Rightarrow \text{we can find } r_2.$$


→ we were asked to find this  $r$ .

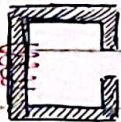Example 2 slide 15:

$$R = \frac{L_c}{\mu A}, \quad B = \frac{\phi}{A}$$



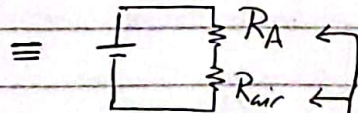→ not continuous, there's air resistance here.



in series

since the flux goes through them → →.

→ Part 1:

$$\phi = AB = 1 \times 9 \times 10^{-4} = 9 \times 10^{-4} \text{ Wb.}$$

$$R_{air} = \frac{0.0005}{\underbrace{4 \times \pi \times 10^{-7}}_{\mu_0} \times 9 \times 10^{-4}} = 442.1 \text{ K}$$

$$R_A = \frac{0.3}{7000 \times 4 \times \pi \times 10^{-7} \times 9 \times 10^{-4}} = 3.8 \text{ K}$$

→  $1.05 \rightarrow A + A \times 0.05A$   
factor of 1.05 is the flux in the air.  
→ bring effect of the air.






$$\rightarrow N_i = \Phi R = 0.003 * 201.7 * 10^3 = 603$$


$$i = \frac{603}{500} = \boxed{1.2 \text{ A}}$$

Slide 17:

Ex 1:

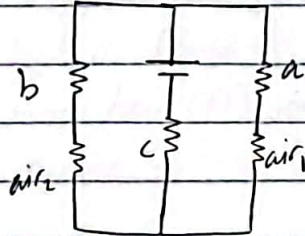

Ex 2:

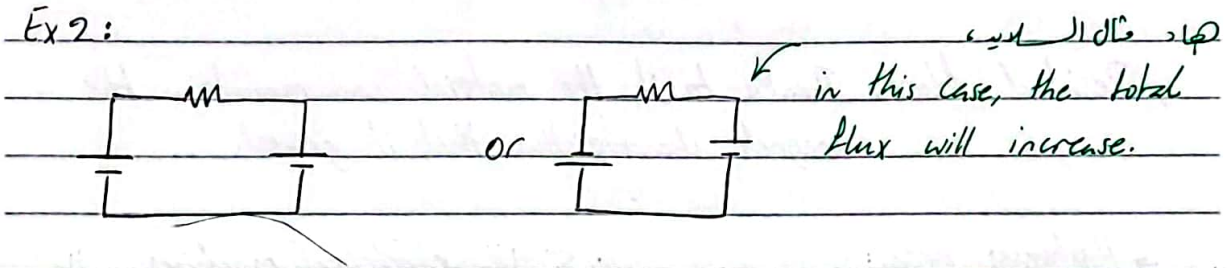

Lecture 5

13/3/2023

Hysteresis:

Assume that we have a Ferro-magnetic material that is not magnetized, in order to arrange its particles, we will need to pass a magnetic field through it to get a magnet out of it.

لدى بطور field كى ما ايدى نقطة بطل فيه particles ليترتبوا، چون لا ايدى ايدى ايدى، و ايدى، لا ايدى ايدى field ايدى path معين، لا ايدى ايدى ايدى ايدى ايدى field ايدى path ايدى.


Retentivity:

قدرة المادة انها تحافظ على المغناطيسية ايدى ايدى حتى بعد زوال المجال ايدى ايدى عليها لتتحول مغناطيسية. لى ايدى ايدى H ايدى ايدى.



ما يوقفه، بلزني انو انفسه polarity نبعها يعني اذا كان اتجاه ال field الذي انطبق عليها  $N \rightarrow S$  يعني اقله غير  $N \rightarrow S$  فينفسه انطبقا field بالجهة العكسة.

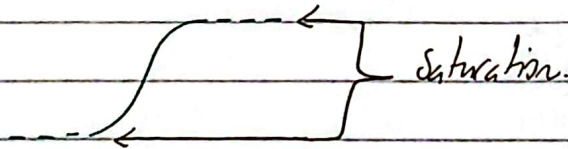له بعد صحت كذا ترجع لا state التي ما كان فيها اي عليه شحن. له لان موصل المطلوب، المطلوب فانه نفس polarity كاملة، فينك قد تزيد كذا نفس الانقلاب وتوصل لانه حتى موجود من جهة الالب.




\* Youtube video #2: Magnetic Energy of Hystereses.

→ Residual Flux: Thanks to it, the material can maintain the magnetic characteristics that it gained.

→ Hystereses area:

losses

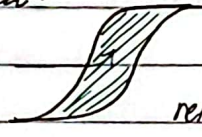

بال electrical machines بقد تكون ال Area اصغر ما يمكن، يعني كهنسة حسب بقد انها تكون كبرك و ال relativity تكون كبر عالية.

له فالتا، اجته عال hard disk و تحينه 1 و 0، ال polarization و ال polarization على جسم ال head ال 1 زي 0 و بيدي # ال [can maintain the bits to stay 1 or 0 for a longer time.] ينال ال head بقد القيمة موجودك عندي. له بال machines كل ما زادت ال Area بترتبه ال losses. ال Relativity، بين الانقلاب بتوفر ال loss فيرجع.

\* Youtube video #3: SSD vs. Hard Drive.

- ① بتخزين ال data فيها.
- ② بالطرق (bit it with hammer).
- ③ By giving it a DC source to alternate the charging

∴ Area = losses.

له يعني بقد ال polarity.



→ Energy losses are due to producing & consuming power.

HDD :

- ✓ has a magnetic disk.
- ✓ cheaper.
- ✓ The head moves to write 1's & 0's. [could have many heads (6)].
- ✓ Higher space.

SSD :

- ✓ Much faster.
- ✓ Electronics (RAMs).
- ✓ For frequently accessed data.

→ Eddy current:

← التيار في الـ coil بـ مجال مغناطيسي ، المجال المغناطيسي بولد تيار .

→ The current inside the coil (current)

التيار يعني : التيار المتولد من الـ flux ، فمعاكس التيار ، و اتصال في عنده تيار و

مقاومة الـ coil فـ  $I^2 R$  الـ power .

لـ يعني الـ power dissipation ، و تحت الـ motor .

← لـ لازم انك نقل الـ power dissipation ، كـ ما زاد التيار زيـ الـ eddy current فـ زيـ

الـ losses ، كـن بـيـ أقل الـ losses بيـون ما أقل الـ flux ، كـان ما أكثر الـ

قل الـ eddy current ، بـيـ أقل الـ eddy current .


Answer : By lamination [slicing].

← الـ eddy current و الـ core losses ( الـ hysteresis ) .

→ Eddy current causes heating which leads to losses, that's why we need to reduce it.


Faraday's Law:

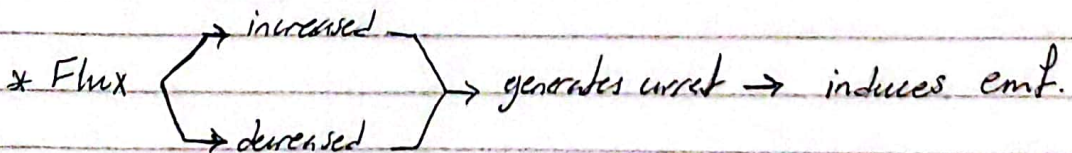\* يعني اذا صار في عنده تغير الـ flux الموجود بـ core و عنده .



Faraday's law  $\rightarrow$  induced emf

Lenz's law  $\rightarrow$  polarity

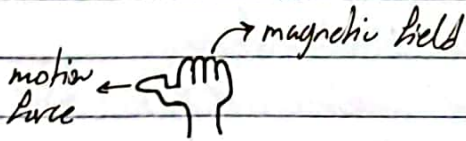

Palm of the hand = current.

\*\*  $\rightarrow$  Motor or Generator effect?

left hand

Right hand.

Lecture 6

15/3/2023

\* بنظرة فاعلة الى اليمين لفرد اتجاه التيار العاكس الى اليمين يولد معنا.

Motor action:

\* Motor: from electrical to mechanical energy

المحرك ال motor انك بعد flow لا current في wire موجود magnetic flux output ال force يولد flux ال موجود ال flowing للتيار مع وجود ال flux ال يولد force output ال (حركة).

Generator effect:

المولد ال generator ال يكون عندك current موجود في wire انت بتحرك داخل مجال مغناطيسي (بجهد velocity معينة يولد induced emf فينزل كبريا).

\* Transformers are AC or DC?

Faraday's law is all about the change in flux, therefore; if it was DC and the current is fixed the flux will also be fixed which will give no change in the current,  $\therefore$  induced emf will always be zero.

Therefore, All transformers are AC. "Must have AC signal"





→ B:

لما بتوصل لـ steady state؟ لما السارعة = 0 يعني مجموع ال forces = 0  
 يعني طالما في 30N جهة اليمين لازم نتج induced force يكون مقدارها 30N  
 و جهة اليسار عشان تعاكسها.

$$i = \frac{F}{L \times b} = \frac{30}{10 \times 0.1} = 30 \text{ A}$$

لما ال battery + (0.3 \* 30) resistance : عشان ال 129

$$\therefore V_{ss} = \frac{129}{10 \times 0.1} = 129 \text{ m/s}$$

$$\Rightarrow \text{bar power} = V_{ind} \times i = 129 \times 30 = 3870 \text{ W}$$

$$\Rightarrow \text{battery power} = V_B \times i = 120 \times 30 = 3600 \text{ W}$$

الفرق بينهم راجع عا  
 كسلا  
 اللي سبب المقاومة.


$$0.3 \times 30 \times 30 = 270 \text{ W}$$

\* generator or motor? generator

لما لانتي أنتجت طاقة مقدارها 3870W راجع عن

3600 البطارية و 270 عن تسخين حار.

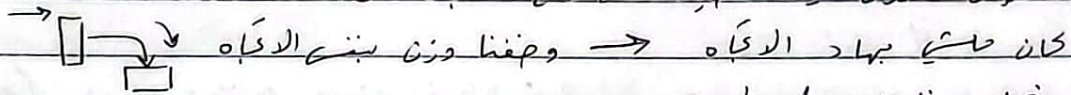لما بالموال، الوزن الك حطيتاه اطلاق اجاب حركة ال bar.



كان طبعي جهاد ال كباة → وبقنا وزن بنسبة ال كباة  
 وضار عنا produced power.

\* لو كان طبعي → وبقنا وزن جهاد ال كباة ← زي فرج (C) بغير عنا effect motor.

← حسب قانون Lenz، ال  $V_{ind}$  لازم تعاكس ال حسي اللي بطنه، ف  $E_{ind}$  ليلها

راج تكون جهاد ال كباة → والسار.

$$\rightarrow C: 30 = i (L \times B)$$

$$30 = i (10 \times 0.1) \Rightarrow i = 30 \text{ A}$$


$$e_{ind} (V_{ind}) = 120 - 9 = 111 \text{ V}$$

$$V_{ss} = \frac{111}{10 \times 0.1} = 111 \text{ m/s}$$

(Motor)

بغير في losses من البطارية.

Transformer

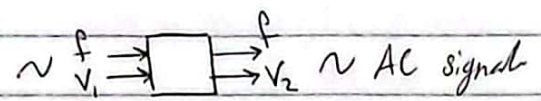


The magnetic flux is the only thing that connects the primary with the secondary coil.

Load عنده طرفين، واحد عن ال source وواحد ال load.

Power generator، losses، DC، impedance، customers، losses تكون حبة عالية.

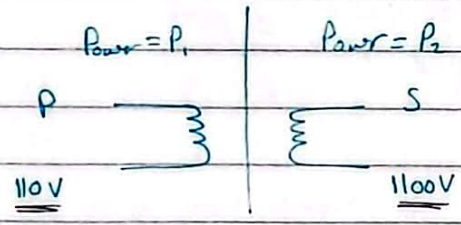AC، generator، up transformer، customer، down transformer.



Power، current، voltage، current.

$$P = VI$$

$$\text{Losses} = I^2R$$

Transformer types: core types, shell type.

جارية التردد، up، down، functionality.

Laminated to reduce eddy current.

$$a = \frac{N_p}{N_s} \Rightarrow \text{emf} = N \frac{\Delta\phi}{\Delta t}, \quad \frac{\Delta\phi}{\Delta t} = \frac{\text{emf}}{N}$$

$$\frac{\phi}{\Delta t} = \frac{V_p}{N_p} = \frac{V_s}{N_s}$$

\* a < 1 ⇒ step up

\* a > 1 ⇒ step down









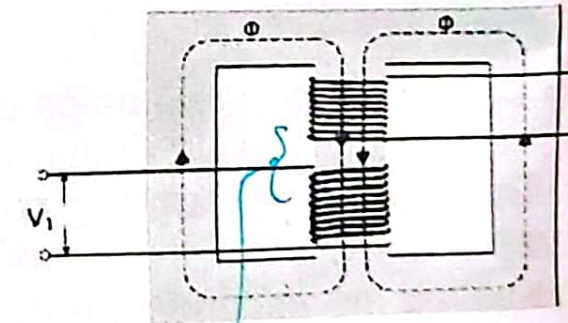
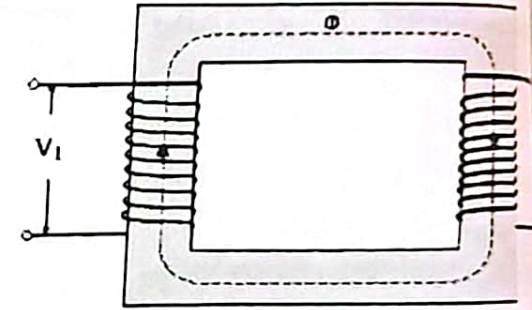
# Power Transformer Types

Power transformers are constructed on one of two types of cores:

- **Core types transformer:** Simple rectangular laminated piece of steel with the transformer windings wrapped around two sides of the rectangle.
- **Shell type transformer:** three legged laminated core with the windings wrapped around the centre leg.



more common

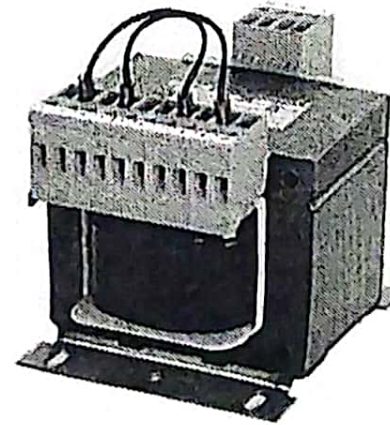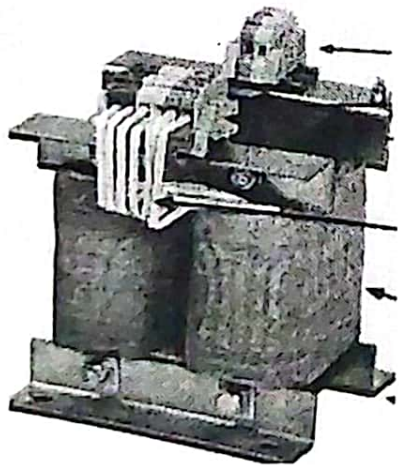

لا عشان يكونوا اتوبها  
عشان لان طاقته غير عادي  
مشكلة انه طاقته غير في  
Flux

- Dot convention: اشارة الزاوية
- ⇒ Primary current flows into the dot.
- ⇒ Secondary current flows out of the dot.

Peak value vs. RMS value:

$$V_{RMS} = \frac{1}{\sqrt{2}} * V_{PK}$$



$$v_t = 14 \sin \omega t$$

↓  
Peak value

- ⇒ Capacitive load: the voltage is leading power factor.
- ⇒ Inductive load: the voltage is lagging power factor.

⇒ Complex power: Apparent power  
Reactive power  
True power

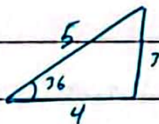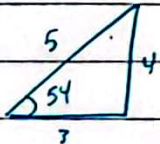لأنه ال imaginary part يجب وجود ال Capacitors وال Inductors بإختلاف ال circuit.



← الزاوية صحت مع ال Power factor  
الذو ال real part مع

\* بمعنى إختلاف ال real part  
أكبر ما عتد ال real part

ال imaginary part هو ال بطول ال

← ال Power factor =  $\frac{P}{S}$  ، كنه ما كان أقرب للواحد كنه ما كان أحسن.  
أقل ما  $\approx 0.9$  ✓



# Example 1


$$a = \frac{V_p}{V_s} = \frac{2400}{240} = 10$$

Step-down  
P S

Consider an ideal, single-phase 2400V-240V transformer. The primary is connected to a 2200V source and the secondary is connected to an impedance of  $2 \angle -36.9^\circ$ , find,

- The secondary output current and voltage.  $V_s = \frac{2200 \angle 0^\circ}{10} = 220 \angle 0^\circ$  V ;  $I_s = \frac{V_s}{Z_s} = \frac{220 \angle 0^\circ}{2 \angle -36.9^\circ} = 110 \angle -36.9^\circ$  A
- The primary input current.  $I_p = I_s/a = \frac{110 \angle -36.9^\circ}{10} = 11 \angle -36.9^\circ$  A
- The load impedance as seen from the primary side.
- The input and output apparent power.

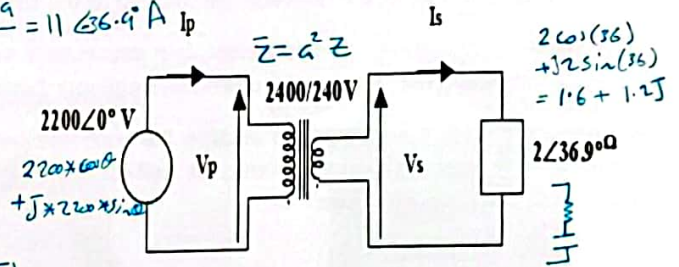c)  $Z = \frac{V_p}{I_p} = \frac{2200 \angle 0^\circ}{11 \angle -36.9^\circ} = 200 \angle 36.9^\circ$



d)  $2200 \angle 0^\circ * 11 \angle -36.9^\circ = 24.2 \text{ kVA} \angle -36.9^\circ$  input  
 output:  $2200 \angle 0^\circ * 110 \angle -36.9^\circ = 24.2 \text{ kVA} \angle -36.9^\circ$   
 input power = output power

As if we have a simple circuit:


## Impedance Transformation through a Transformer

Impedance of the load:

$$Z_L = V_s / I_s$$

The impedance of the primary circuit:
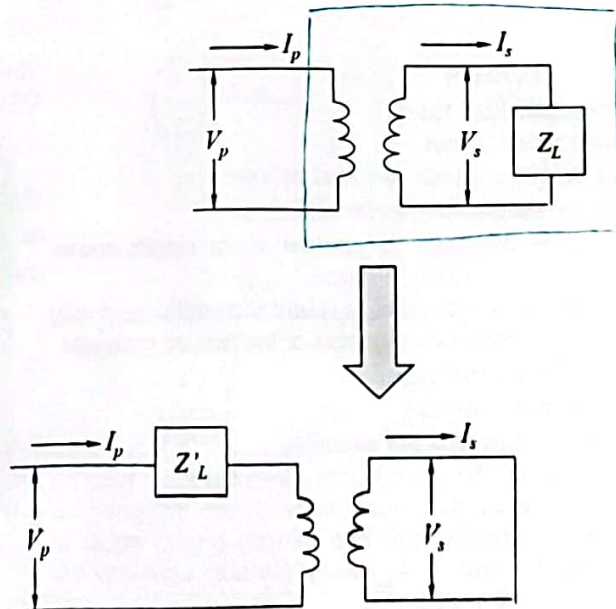
$$\begin{aligned} Z'_L &= V_p / I_p \\ &= (aV_s) / (I_s/a) \\ &= a^2 (V_s / I_s) \\ &= a^2 Z_L \end{aligned}$$



في فرع ٤ بالأسئلة السابقة يمكنني  
 $Z' = a^2 Z = 10^2 * 2 \angle -36.9^\circ$

# The Equivalent Circuit of a Real Transformer

The losses that occur in transformers have to be accounted for in any accurate model of transformer behaviour.


1. Copper ( $I^2R$ ) losses. Copper losses are the resistive heating losses in the primary and secondary windings of the transformer. They are proportional to the square of the current in the windings.
2. Eddy current losses. Eddy current losses are resistive heating losses in the core of the transformer. They are proportional to the square of the voltage applied to the transformer.
3. Hysteresis losses. Hysteresis losses are associated with the rearrangement of the magnetic domains in the core during each half-cycle. They are a complex, nonlinear function of the voltage applied to the transformer.
4. Leakage flux. The fluxes which escape the core and pass through only one of the transformer windings are leakage fluxes. These escaped fluxes produce a self-inductance in the primary and secondary coils, and the effects of this inductance must be accounted for.

$$V_1 = I_1 \left[ Z_1 + \frac{Z_m (Z'_m + Z'_L)}{Z_m + (Z'_2 + Z'_L)} \right]$$

\* Copper losses can be implemented as resistors.

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

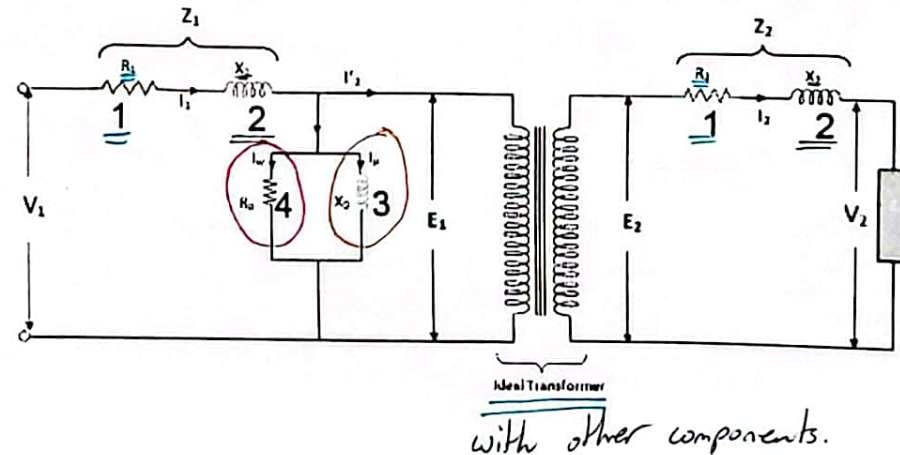↳ open circuit and short circuit tests are used to get the values of the elements in the circuit.




Quiz: Find the current in a primary cable for a current transformer that has 200 turns in the secondary part, Assuming  $I_s = 5A$ .

$$a = \frac{N_p}{N_s} = \frac{1}{200} \Rightarrow \frac{1}{a} = 200$$


$$\frac{I_p}{I_s} = \frac{1}{a} \Rightarrow \frac{I_p}{5} = 200 \Rightarrow I_p = 200 \times 5 = 1000A.$$

من بستنم بالاجزاء الطويل.


# Other Transformers

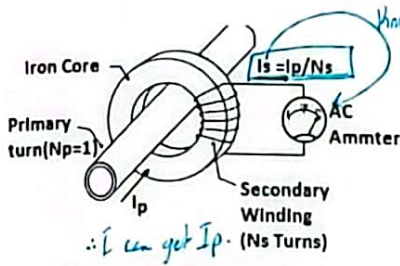

CURRENT TRANSFORMER

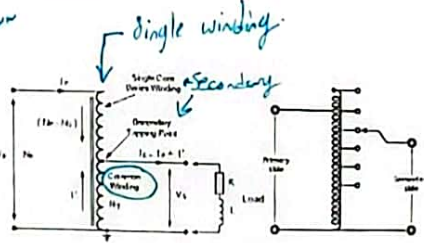

AUTOTRANSFORMER

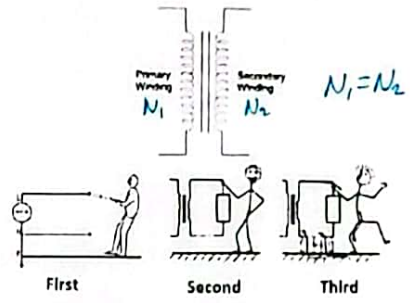

ISOLATION TRANSFORMER



used to measure the current instead of adding an ammeter to the circuit.

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)



له الفكرة انه حزن بستن ال winding منه حزين.





14  
له غايه يكون ال  $N$  ال primary  
باده ال  $N$  ال secondary  
Step up or down  
isolation dai  
For safety purposes.

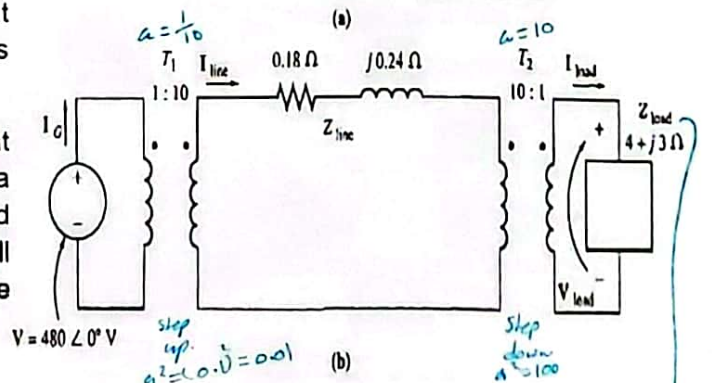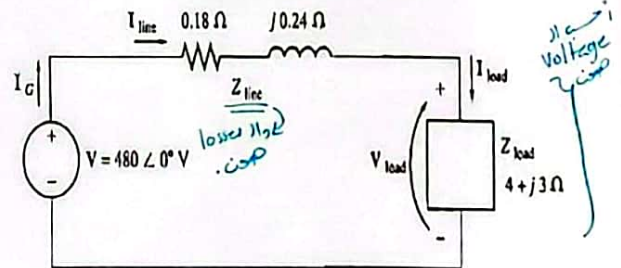
## Example 2

A single-phase power system consists of a 480-V 60-Hz generator supplying a load  $Z_{load} = 4 + j3 \Omega$  through a transmission line of impedance  $Z_{line} = 0.18 + j0.24 \Omega$ . Answer the following questions about this system.

- If the power system is exactly as described above (and shown in Figure a), what will the voltage at the load be? What will the transmission line losses be?
- Suppose a 1:10 step-up transformer is placed at the generator end of the transmission line and a 10:1 step-down transformer is placed at the load end of the line (as shown in Figure b). What will the load voltage be now? What will the transmission line losses be now?



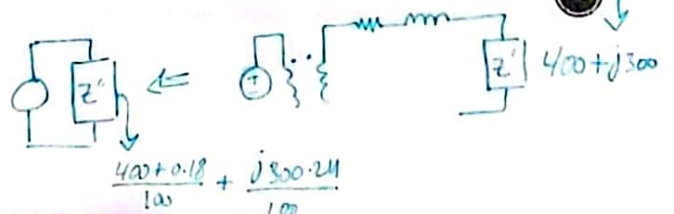Prepared by Dr. Musa Alyaman Electrical Machines (0908321)



← ال losses بتكون موجوده على Primary وعلى Secondary مع بعض.

⇒ Example 2 slide 15:

لما عندها نسبة ال voltage وال losses بيننا نطلع قيمة ال current ، ال V موجوده عندها  
 نغير بيننا نطلع ال total impedance :

$$\begin{aligned} a) Z_{eqn} &= 0.18 + j0.24 + 4 + j3 \\ &= 4.18 + j3.24 \\ &= \sqrt{4.18^2 + 3.24^2} , \tan^{-1}(3.24/4.18) \\ &= 5.29 \angle 37.8^\circ \end{aligned}$$

$$\begin{aligned} Z_{load} &= \sqrt{9+16} = 5 \\ \tan^{-1}(3/4) &= 36.9^\circ \end{aligned}$$

$$I_{line} = \frac{V}{Z_{eqn}} = \frac{480 \angle 0^\circ}{5.29 \angle 37.8^\circ} = 90.8 \angle -37.8^\circ$$


$$V_{load} = I_{line} * Z_{load} = 90.8 \angle -37.8^\circ * 5 \angle 36.9^\circ$$

لما يكون بيننا نطلع ال losses !

$$V_{load} = 454 \angle -0.9^\circ \text{ V}$$

\* ال losses ال real part ال power :
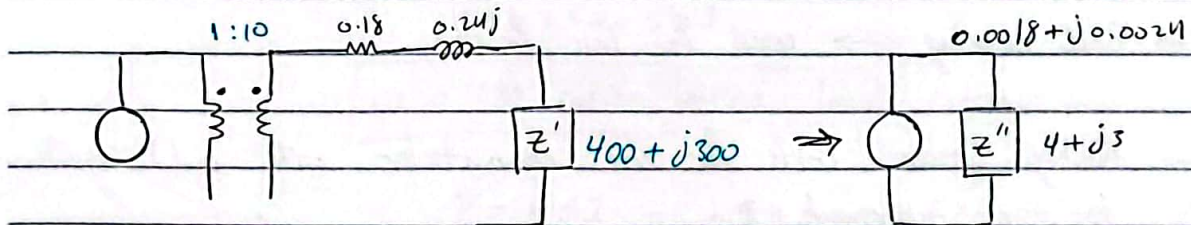
$$\begin{aligned} P_c(P) &= I^2 R \\ &= 90.8^2 * 0.18 = 1484 \text{ W} \end{aligned}$$



$$I_G = \frac{480 \angle 0^\circ}{4.0018 + j3.0024} = \frac{480 \angle 0^\circ}{5.003 \angle 36.88^\circ} = 95.94 \angle -36.88^\circ \text{ A}$$

$$I_{line} = (95.94 \angle -36.88^\circ) / 10 = 9.594 \angle -36.88^\circ \text{ A}$$

$$I_{load} = 10 * 9.594 \angle -36.88^\circ = 95.94 \angle -36.88^\circ \text{ A} \rightarrow$$



$$\rightarrow V_{load} = \left\{ \begin{array}{l} 4 + j3 \\ 5 \angle 36.9^\circ \end{array} \right\} \rightarrow Z$$

$$\Rightarrow V_{load} = I_{load} * Z = 95.94 \angle -36.88^\circ * 5 \angle 36.9^\circ = 479.7 \angle -0.01^\circ V$$

Losses: لقد ال losses هون ابل ببيع فبقولة.

$$\rightarrow R(P) = I^2 R = (9.594)^2 * 0.18 = \boxed{16.7W}$$

## Lecture 8

## Chapter 3

→ The commutator changes the current direction automatically, it uses soft brushes to do so instead of manually changing the wires.

↳ it changes the current direction every half cycle.

↳ The commutators are also used to prevent the wires from being twisted.

↳ Splitting it & adding more loops will increase the force.

\* DC motors can have many movements due to: adding gears.

→ Ball bearing → used for less friction.

→ Adding more coils for the commutator will add smoothness to the movement.

→ The momentum helps the coils to keep moving.

# DC MACHINERY FUNDAMENTALS

Chapter 3



Prepared by Dr. Musa Alyaman Electrical Machines (0908321)




# Introduction

DC Motors are widely used in robotics because of their small size and high energy output.

Key characteristics of DC motors include:

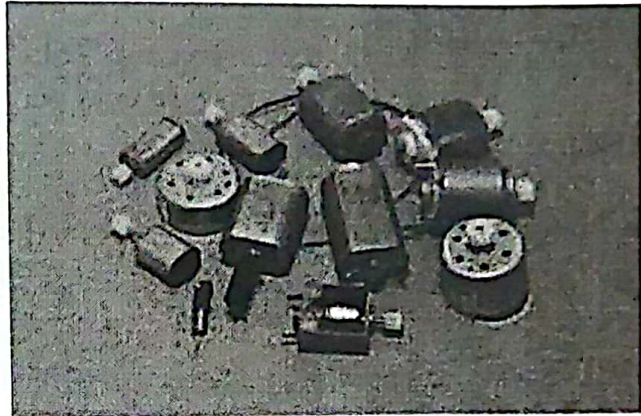1. High Speed
2. Low Torque
3. Reversibility → it works forward & reverse.  
 في اتجاهين  
 - كما في





Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

3

\* Chargeable devices are DC motors.
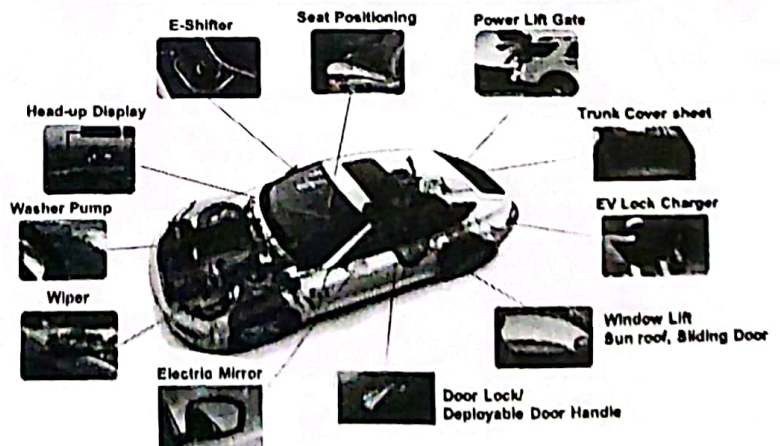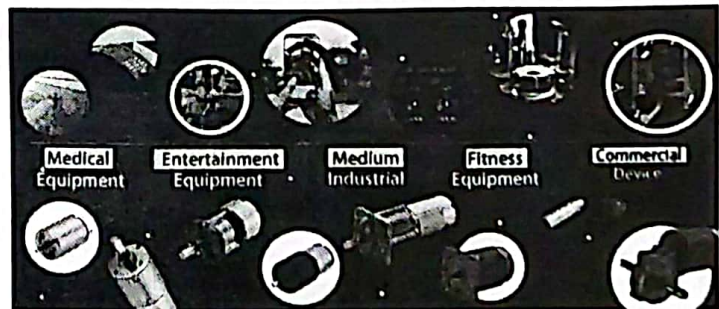
## DC Motor Applications

- Cordless hand drill
- Electric lawnmower
- Fans
- Toys
- Electric toothbrush
- Servo Motor
- Automobiles
  - Windshield Wipers
  - Door locks
  - Window lifts
  - Antenna retractor
  - Seat adjust
  - Mirror adjust
  - Anti-lock Braking System






Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

4

\* المغناطيسية لا motor لا لازم يكون في magnetic flux  
 ثابت نوع اما في permanent magnet او في ferro-magnetic material  
 في rotor هو عبارة عن مجموعة من ال coils كل coil بعد cutting  
 لا flux ينتج عنها force صافي force في rotation rotor
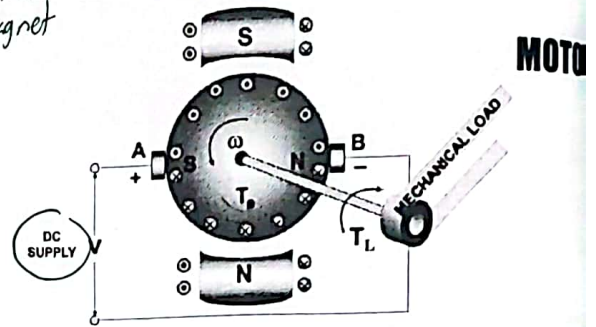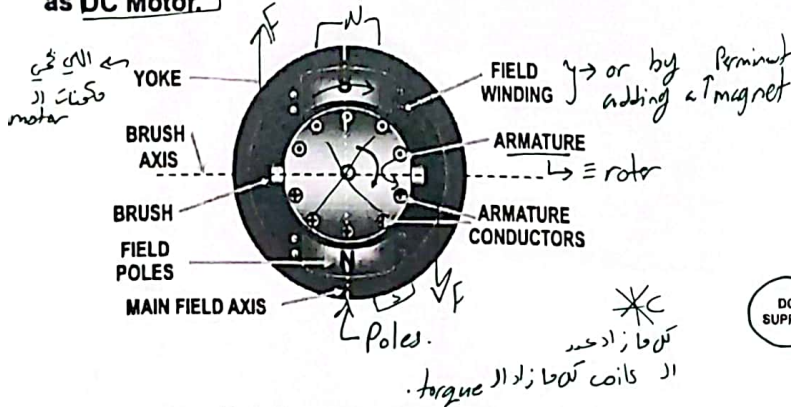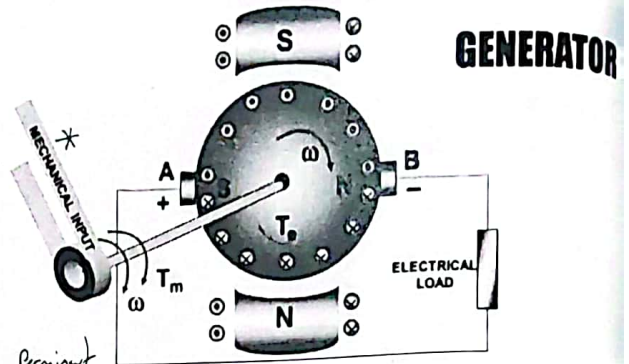
# DC MACHINES




A DC machine is an electro-mechanical energy conversion device. It can convert Mechanical power into Electrical Power. When output electrical power is DC, it is called DC Generator. When it converts DC electrical power into mechanical power, it is known as DC Motor.



Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

↳ There are 2 main parts: ① Stator → ثابت  
 ② Rotor → ملف

## Construction of DC Machine

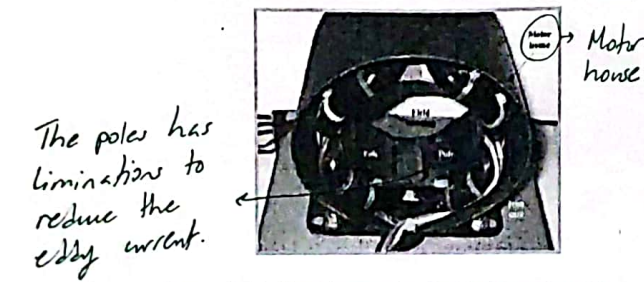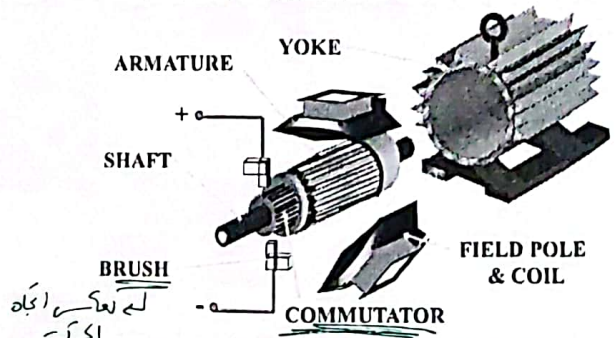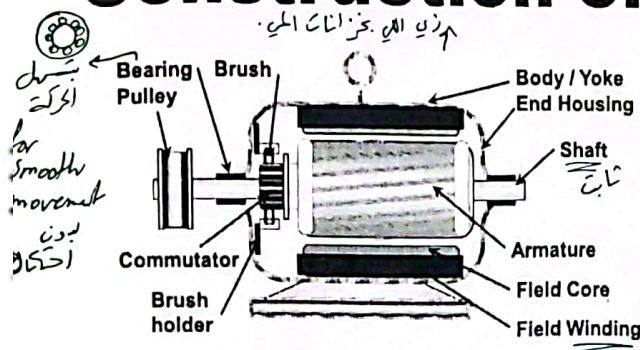

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)


\* minimum: we need 2 poles (N-S).

\* عكس اتجاه ال Force لا تغير القطبية .  
 لازم التيار ينعكس  
 له يكون ييجي دور ال commutator .



# DC Motor - How it Works

A DC Motor has 4 major components:

- A permanent magnet that doesn't move, called the stator. (OR winding)
- An electromagnet (usually wound bare wire) 
- A frame on which the electromagnet is wound, called the armature
- A set of brushes for transferring voltage to the armature



If a loop of wire were placed within a magnetic field, and current were applied to it, a magnetic field would be induced in the loop and it would try to rotate until both magnetic fields lined up.

As the loop of wire rotates, its connection with the brushes is broken, but because of momentum, the loop will continue to rotate until, after 180°, the other sides of the loop are in contact with the brushes.

As long as current is applied to the brushes, the loop of wire will continue to rotate again and again and the rotor will continue rotation.

Direction of rotation depends upon the polarity of the applied voltage.

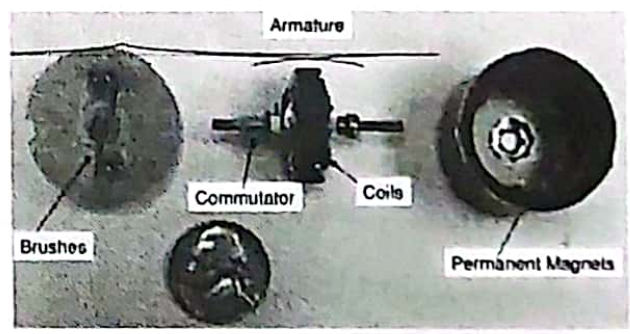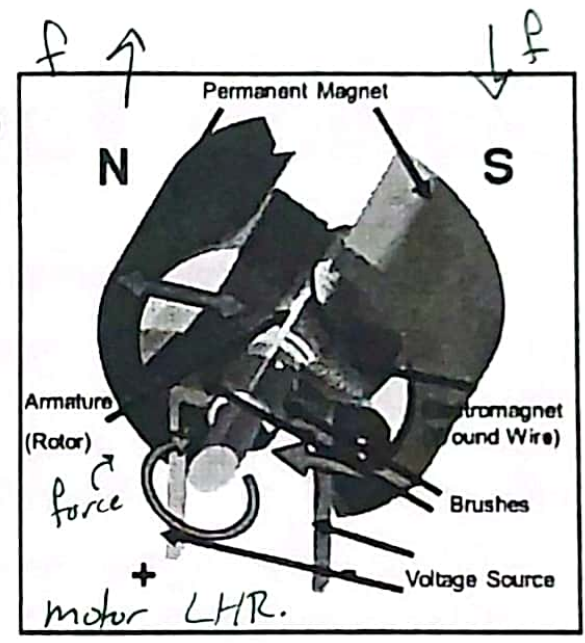
To change the direction of a DC Motor, simply change the polarity of the applied voltage.



$\rightarrow P = \omega T$
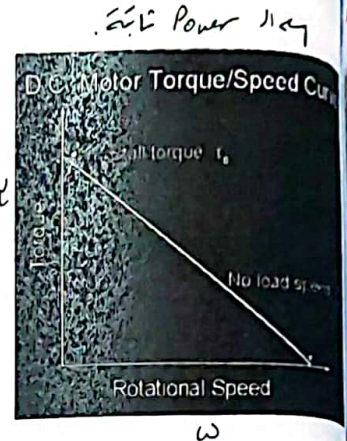
# Power, Torque and Speed

- The power of a DC Motor is proportional to the product of its torque and its speed.
- As the speed of the motor decreases, the torque increases proportionally until maximum torque is achieved. At this point, the motor is stalled, meaning that the motor is not turning even though power is being supplied to it. This is known, appropriately, as the "Stall Torque."
- The DC Motor has two "End States"- the Unloaded Speed (maximum speed, no torque) and Stalled Speed (zero speed, maximum torque).
- Current ratings of DC Motors are given at the stall torque, since this is the point of maximum current.
- Maximum power is achieved at a point between Stall and Unloaded Speed, where the speed and torque curves intersect.
- The speed of the DC Motor is directly proportional to the applied voltage. Increase the voltage for higher speeds and decrease the voltage for lower speeds



Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

\*E depends on the speed  $\omega$   
& the flux  $\phi$

## Important DC Machine Equations

### EMF Equation

$$E = k_A \phi \omega = k'_A \phi n$$

$$n = \frac{60\omega}{2\pi}$$

generated from the motor action

$E$  = EMF induced in armature (V)  
 $k_A$  = geometry constant  $\rightarrow$  depends on the motor itself.  
 $\phi$  = flux/pole (Wb)  
 $\omega$  = speed of rotation (rad/s)  
 $n$  = speed of rotation of armature (rpm)

### Torque Equation

$$T = k_A \phi I_A$$

$T$  = torque of armature (N-m)  
 $k_A$  = geometry constant  
 $\phi$  = flux/pole (Wb)  
 $I_A$  = armature current (A)

### Power Equation (no losses)

$$P = EI_A = T\omega$$

$P$  = power (W) - not counting losses  
 $E$  = EMF induced in armature (back EMF)  
 $I_A$  = armature current (A)  
 $T$  = torque of armature (N-m)  
 $\omega$  = speed of rotation (rad/s)  
 Note that  $P_m = V I_A$  which will be higher than  $P$  because of loss in the field and armature windings as well as rotational (friction) losses.



### Geometry Constant

$$k_A = \frac{pN}{2\pi M} \text{ (rad/s)}, k'_A = \frac{pN}{60M} \text{ (rpm)}$$

$p$  = number of field poles  
 $N$  = number of active conductors on armature  
 $M$  = number of parallel paths in armature winding ( $m$  for lap winding,  $=2$  for wave winding)

$$K = \frac{ZP}{2\pi a}$$

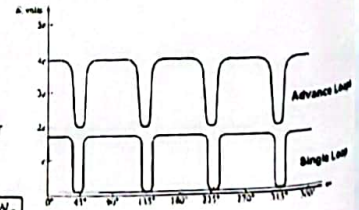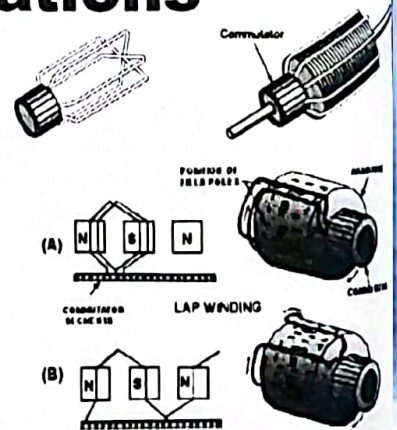$Z$  = number of conductors on rotor  
 $C$  = number of coils on rotor  
 $N_c$  = number of turns per coil



Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

$T = \frac{Z}{2} \phi I$  for a single loop.



Chapter 3 - Example slide 11:

→ a: A current will pass, which will induce a force that moves, the movement according to Len's law will create a generator effect that creates a magnetic flux that is opposite to the original flux. transient state

This will result of having induced voltage which will equal to 120 V at the steady-state, the current will then be 0.   
 ⇒ It'll keep turning with no load speed.

→ b:

$$i = \frac{V_B - V_{ind}}{R} = \frac{120}{0.3} = 400 \text{ A}$$

(e<sub>ind</sub>) V<sub>ind</sub> = 0

$$e_{ind} = 120 = k \omega \phi, \quad k = \frac{ZP}{2\pi a} = \frac{[2 \times 1 \times 1] \times 2}{2 \times \pi \times 1} \Rightarrow k = \frac{2}{\pi}$$


$$120 = \frac{2}{\pi} \omega B r L \pi$$

$$\phi = BA \quad A = \frac{2\pi r \times L}{2}$$

$$\phi = B r L \pi$$

$$120 = \omega B r L \Rightarrow \omega = \frac{120}{2 \times 0.25 \times 0.5 \times 1}$$
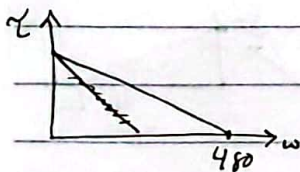
$$\omega = 480 \text{ rad/sec} \leftarrow \text{no load rotational speed.}$$



$$\tau = k \phi i = 0.5 \times 1 \times 2 \times \pi \times \frac{2}{\pi} \times 400 = 100 \text{ N.m.}$$

→ c:  $\tau = 10 \text{ N.m}$

$$\tau = k \phi i \leftarrow \text{المحرك}$$

$$10 = \frac{2}{\pi} \times 1 \times 0.5 \times 0.25 \times \pi \times i \Rightarrow i = 40 \text{ A}$$

$$V_{induced} = 120 - (40 \times 0.3) = 108 \text{ V}$$

$$\rightarrow \omega = \frac{e_{in} \cdot V_{in}}{\phi k} = \frac{108}{\frac{2}{\pi} \times 1 \times 0.5 \times 0.25 \times \pi} = 432 \text{ rad/s.}$$

$$P_{elec} = IV = 40 \times 120 = 4800 \text{ W}$$

$$P_{mech} = \omega \tau = 432 \times 10 = 4320 \text{ W}$$

$\gamma \rightarrow$  difference between them (loss)

$$P_B = I^2 R = 40 \times 40 \times 0.3 = 480 \text{ W}$$

$$\rightarrow d: \tau = 7.5 \text{ N.m}$$

$$7.5 = \frac{2}{\pi} \times 1 \times 0.5 \times 0.25 \times \pi \times i \Rightarrow i = \frac{7.5}{0.25} = 30 \text{ A.}$$

$$e_{ind} = 30 \times 0.3 + 120 = 129 \text{ V}$$

$$\omega = 129 / \left( \frac{2}{\pi} \times 1 \times 0.5 \times 0.25 \times \pi \right) = 516 \text{ rad/sec.}$$

$$\tau = k \phi i$$

generator

$\omega \rightarrow$  ~~cap~~  $i$   $\phi$   $\tau$ ,  $\omega$

$\rightarrow e:$


$$\omega = \frac{120}{\phi k} = \frac{120}{\frac{2}{\pi} \times 1 \times 0.5 \times 0.2 \times \pi} = 600 \text{ rad/s.}$$

$$i = \frac{120}{0.3} = 400 \text{ A}$$

$$\phi = \frac{0.2 \times 2\pi \times 0.5 \times 1}{2} = \frac{\pi}{10}$$

$$E = k \phi \omega \Rightarrow \omega = 600 \text{ rad/s}$$
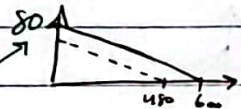
$$\tau = \frac{2}{\pi} \times \frac{\pi}{10} \times 400 = \underline{80}$$







\* فكرة التسيئة انه بيتا دق transition ل power ، بشدة عام بال machines بخون بين electrical و mechanical ، اذا كان ال system عننا ideal ما بضيع شيء من ال power ، لكن بالعام بسير في losses ، ال losses بكونا لا شيء عن ال efficiency .


# Power flow and losses in DC machines

The efficiency of a DC machine is:

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$


$$\eta = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$$

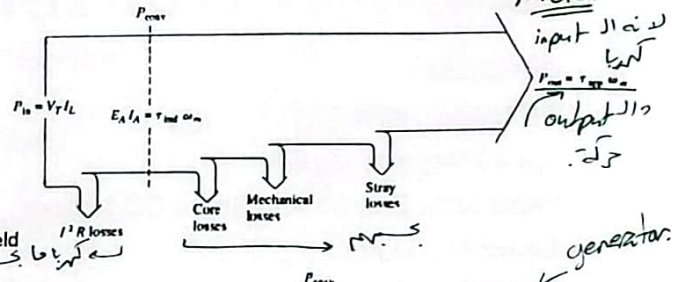$P_{in}$  بيتا انك  $P_{out}$  لانه ال دقا بسير بالطريق .



There are five categories of losses occurring in DC machines.

- Electrical or copper losses** – the resistive losses in the armature and field windings of the machine.  $I^2 R$
- Brush (drop) losses** – the power lost across the contact potential at the brushes of the machine. → because of the direct contact.
- Core losses** – hysteresis losses and eddy current losses.
- Mechanical losses** – losses associated with mechanical effects: friction (friction of the bearings) and windage (friction between the moving parts of the machine and the air inside the casing).
- Stray (Miscellaneous) losses** – losses that cannot be classified in any of the previous categories.

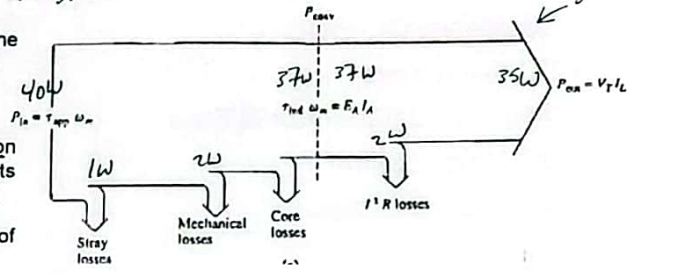

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

\* بعد الخط هم ال نغلا بكونوا ضاعوا لكن لازم احسب ال final مع ادل input بغلا النظر .


③ ④ ⑤  
 ليه موجودين بتلك motor .  
 ② هو موجود بال Brushless DC motors

# DC Motors and Generators

Chapter 4



## DC Motors

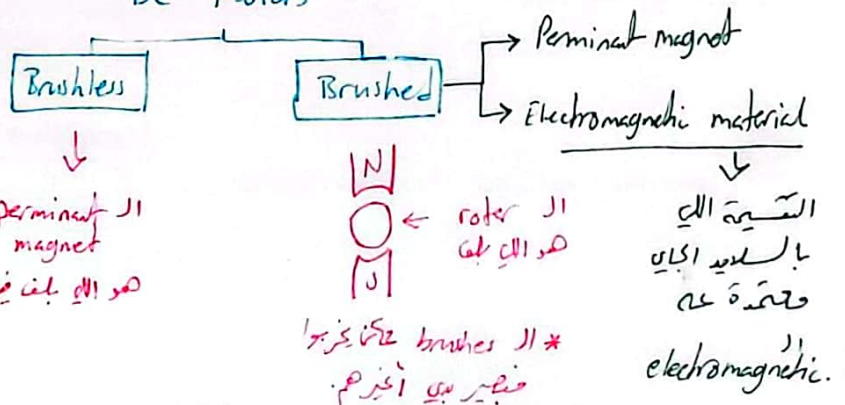

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

# Table of Content

- Introduction
- DC Motor Types
- Speed Regulation (SR)
- Separately Excited and Shunt DC Motors
- Series DC Motor
- Compound DC Motor
- DC Generators
- Motors and Generator in Cars
- DC Motor Control
- Brushless DC Motor


بني  
 \* shunt في نفس المجال  
 لا Series منجدة.

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

→ For large motors.

Winding of the field not the armature.  
 ↓

## Introduction

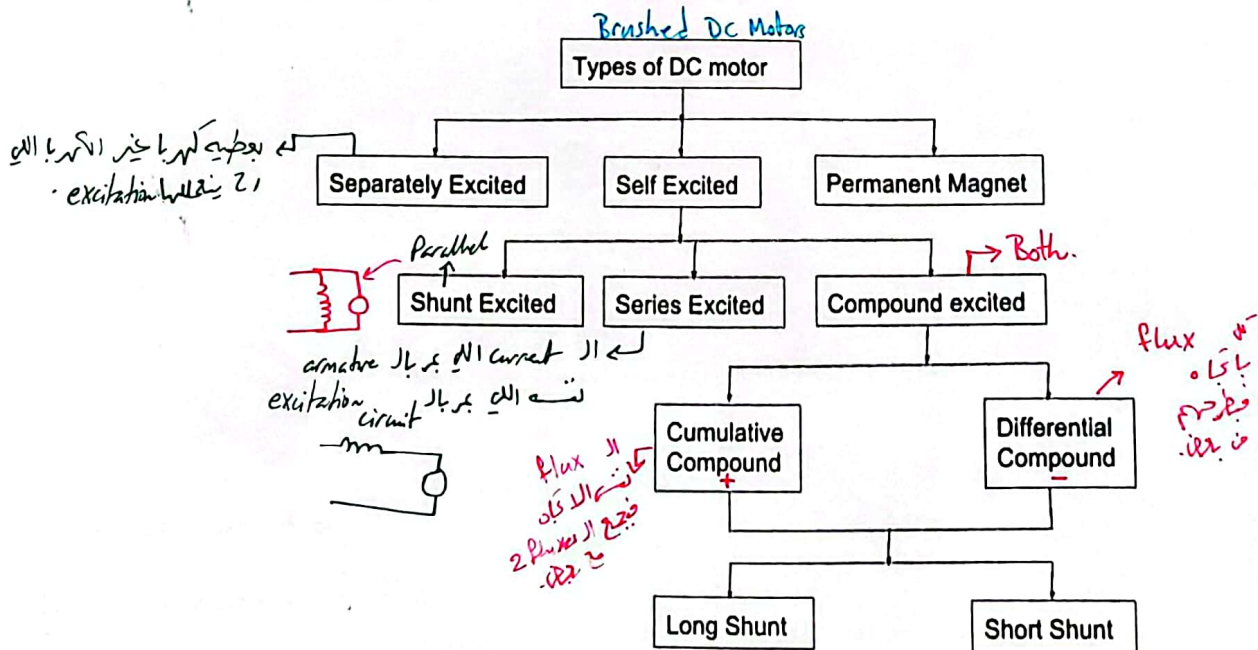


Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

# DC Motor Types


In a dc motor, the stator poles are supplied by dc excitation current, which produces a dc magnetic field.

There are four major types of dc motor in general used;

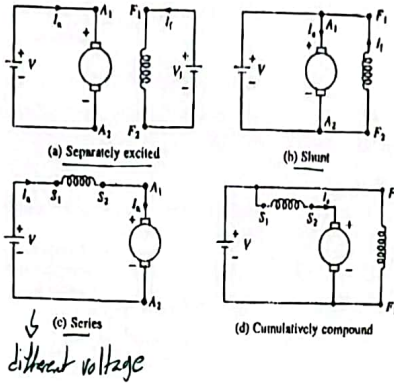- (1) Separately Excited DC Motor.
- (2) Shunt DC Motor.
- (3) Series DC Motor.
- (4) Compounded DC Motor.



different voltage

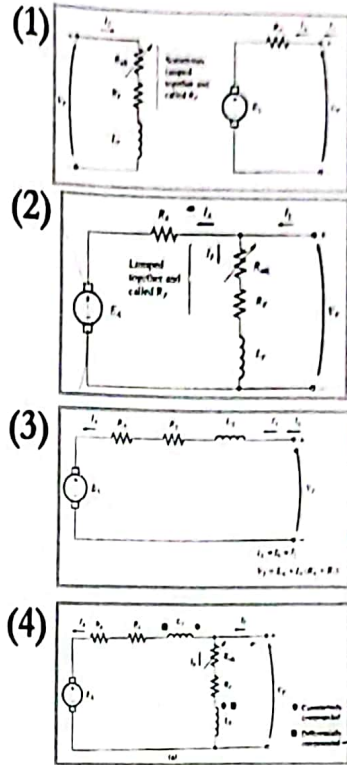

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

$$\begin{aligned} \omega_{n1} &\equiv \omega_{no\ load} \\ \omega_{f1} &= \omega_{full\ load} \end{aligned}$$

## Speed Regulation (SR)


كل ما كان اقل  
كل ما كان ار  
سرته  
و كانت لانه ما بينا  
يكون الفرق  
بين الـ و الـ كبير  
كنت ما تفرق كبر بالـ

DC motors are often compared by their speed regulation (SR) which is defined as;

$$SR = \frac{\omega_{n1} - \omega_{f1}}{\omega_{f1}} \times 100\%$$

SR is the measure of the shape of the motor's torque-speed characteristic.

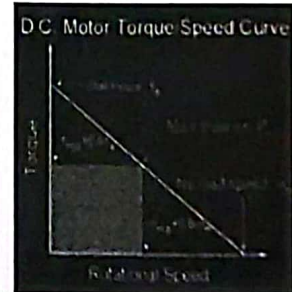
- (a) Positive SR means that the motor's speed drops with increasing load.
- (b) Negative SR means that the motor's speed increasing with increasing load.
- (c) The magnitude of the SR tells approximately how steep the slope of the torque-speed curve is



On application of load the speed of a DC motor decreases gradually. This is not at all desirable. So the difference between no load and full load speed should be very less.

The motor capable of maintaining a nearly constant speed for varying load is said to have good speed regulation i.e the difference between no load and full load speed is quite less.

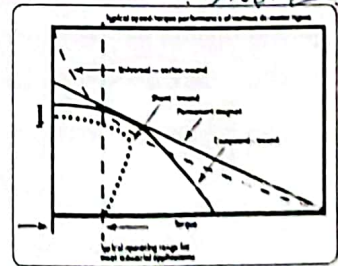The speed regulation of a permanent magnet DC motor is good ranging from 10 – 15% whereas for DC shunt motor it is somewhat less than 10%. DC series motor has poor value of regulation. In case of compound DC motor for DC cumulative compound the speed regulation is around 25% while differential compound has its excellent value of 5%.





Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

\* كمن circuit الهيا:  $R_F$  ← resistor لا field ودا غنا موجودي.  
 $R_A$  ← adjustable R بغير فيها عشان انكم شبه المحاكه بتحكم فيها حركات انكم بد Speed.  
 Inductance ←  $L_F$

بجانب عليه نسخة الكتر حمر
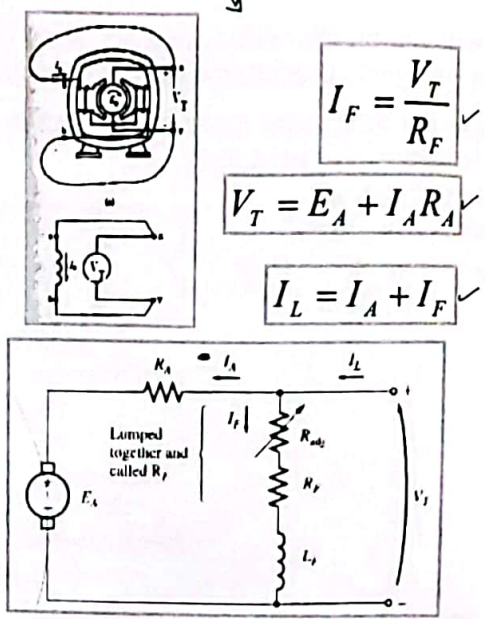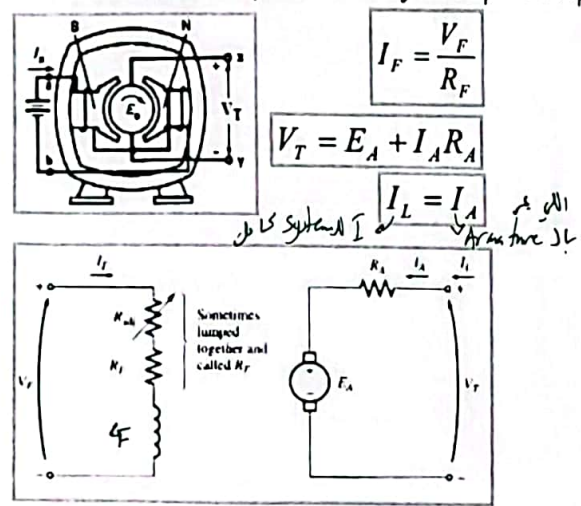
# Separately Excited and Shunt DC Motors

- The armature circuit is represented by the  $E_A$  and  $R_A$ .
- The field coil is represented by the  $L_F$  and  $R_F$ .



Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

الـ excited فيصل

صمد كرفه التحكم بال Shunt  
 ← زادت  $R_A$  بتاثر جوده خيز مشرحة ال flux كانه حا، زادت بحد  $I_F$  فيقل ال flux.  
 ← زادت بتاثر  $V_T$  ، تاثيرها بكون مباشر.

# Speed Torque Characteristics

- The internal generated voltage,  $E_A$ .

$$V_T = E_A + I_A R_A \quad E_A = K\phi\omega$$

- Solving for the above equation yields;  $\omega$ ,

\* كمن ما زاد  $\phi$  حله ك

$$\omega = \frac{V_T - I_A R_A}{K\phi}$$

\* The loss of field excitation results in over speeding for a shunt motor. Thus, care should be taken to prevent the field circuit from getting open.

- The armature current may be expressed as follows:

$$I_A = \frac{\tau_{ind}}{K\phi}$$

\* The speed-torque equation of a DC shunt motor.

$$\omega_m = \frac{V_T}{K\phi} - \frac{R_A}{(K\phi)^2} \tau_{ind}$$


$R_A$  of Armature حاب بغير الخ حاب الـ linear motor.

[بدر انفرجه] (Rad)

\* The actual machine, as the load increases flux is reduced because of armature reaction the denominator terms decrease.

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

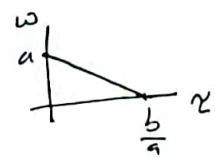
له العلاقة بين  $\omega$  و  $\tau$  Linear  
 له بغير  $\phi$  كانه تغيريا وكما اصله كانه.  
 له لكن بال actual ال  $\phi$  ما بكون نظره لانه  $\phi$  بغير حوي.



زيادة قوة التورق مع زيادة التيار  
على حدٍ قريب (حالة كـر بـيـنـة).
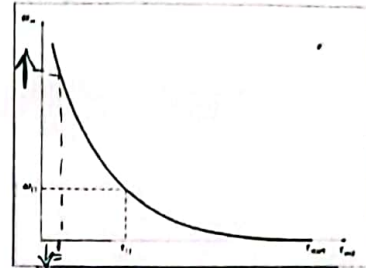
# Series DC Motor

- The induced or developed torque is given by:  $\tau_{ind} = K\Phi I_A$
- The flux in this motor is directly proportional to its armature current. Therefore, the flux in the motor can be given by  $\Phi = cI_A$
- where c is a constant of proportionality. The induced torque in this machine is thus given by  $\tau_{ind} = K\Phi I_A = KcI_A^2$
- This equation shows that a series motor give more torque per ampere than any other dc motor, therefore it is used in applications requiring very high torque, example starter motors in cars, elevator motors.  $\rightarrow$  with low speed
- One disadvantage of series motor can be seen immediately from this equation. When the torque on this motor goes to zero, its speed goes to infinity. If no other load is connected to the motor, it can turn fast enough to seriously damage itself.
- However, if no other load is connected to the motor, it can turn fast enough to seriously damage itself.



$$V_T = E_A + I_A(R_A + R_S)$$


$$I_A = \sqrt{\frac{\tau_{ind}}{Kc}} \quad \tau_{ind} = \frac{K}{c} \Phi^2 \quad \Phi = \sqrt{\frac{c}{K}} \sqrt{\tau_{ind}}$$

$$V_T = K\Phi\omega + \sqrt{\frac{\tau_{ind}}{Kc}}(R_A + R_S)$$

$$V_T = K\sqrt{\frac{c}{K}}\sqrt{\tau_{ind}}\omega + \sqrt{\frac{\tau_{ind}}{Kc}}(R_A + R_S)$$

$$\omega = \frac{V_T}{\sqrt{Kc}} \frac{1}{\sqrt{\tau_{ind}}} - \frac{R_A + R_S}{Kc}$$

$\rightarrow$  non-linear.

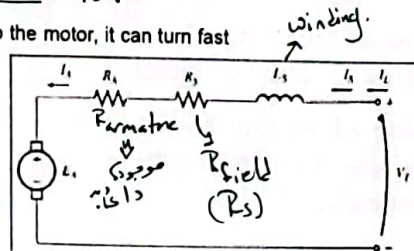

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

8

يتميز هذا النوع من المحركات بـ Series و Shunt  
هذا النوع لا يمكن ان يكون التورق عالي جداً  
لأنه كلما زاد speed كان التورق ينخفض  
 $\Rightarrow$  ما كان يملك torque عالي  
هذه النوع يستعمل في سيارات  
لأنه عند الـ low speed يكون  
عنا torque عالي.

# Compound DC Motor

- The shunt field is always stronger than the series field in a cumulative compound motor the mmf of the two fields add in a differential compound motor the series field is connected so the mmf opposes the mmf of the shunt field



Find magnetomotive force

$$F_{net} = F_F \pm F_{SE} - F_{AR}$$

- Where,
  - $F_F$  = magnetomotive force (shunt field)
  - $F_{SE}$  = magnetomotive force (series field)
  - $F_{AR}$  = magnetomotive force (armature reaction)
- The positive (+) sign is for cumulatively compound motor
- The negative (-) sign is for differentially compound motor

$$V_T = E_A + I_A(R_A + R_S)$$
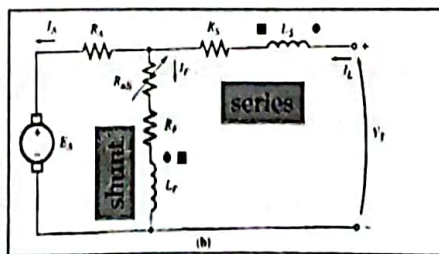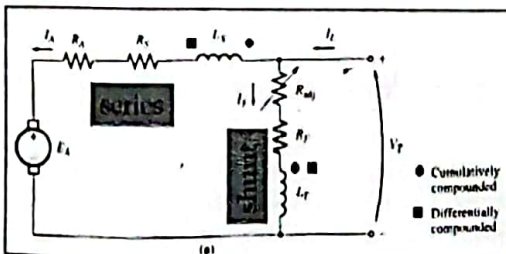
$$I_A = I_L - I_F \quad I_F = \frac{V_T}{R_F}$$



Prepared by Dr. Musa Alyaman Electrical Machines (0908321)


9

$\omega$ : rad/sec  
 من  $n$  ل  $\omega$ :  $\frac{2\pi n}{60}$   
 و  $n$  من  $\omega$ :  $\frac{60}{2\pi}$

لأنه عنده Flux أكثر طاقا. جمع بينا (Flux) Shunt أو تبعه ثابت.
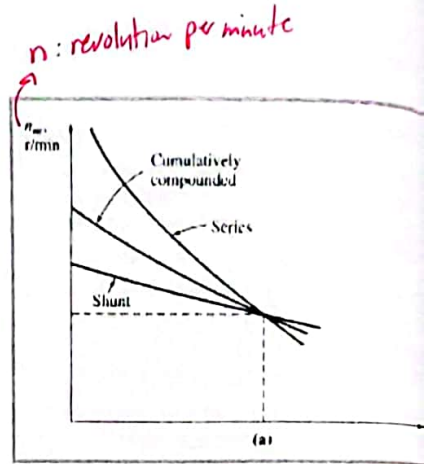
# Torque Speed Characteristic

- The cumulatively compounded motor has a higher starting torque than a shunt motor (whose flux is constant) but a lower starting torque than a series motor (whose entire flux is proportional to armature current).
- It combines the best features of both the shunt and the series motors.
- \* Like a series motor, it has extra torque for starting; like a shunt motor, it does not over speed at no load.
- At light loads, the series field has a very small effect, so the motor behaves approximately as a shunt dc motor.
- As the load gets very large, the series flux becomes quite important and the torque speed curve begins to look like a series motor's characteristic.



Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

## Example 1


hp  $\rightarrow$  Watt  
 1hp = 750W

$\frac{1200 \times 2\pi}{60} \Rightarrow$  rad/sec

Armature reaction  $\Rightarrow$  Armature reaction

A 50-hp, 250-V, 1200 r/min dc shunt motor with compensating windings has an armature resistance (including the brushes, compensating windings, and interpoles) of  $0.06 \Omega$ . Its field circuit has a total resistance  $R_{adj} + R_F$  of  $50 \Omega$ , which produces a no-load speed of 1200 r/min. There are 1200 turns per pole on the shunt field winding

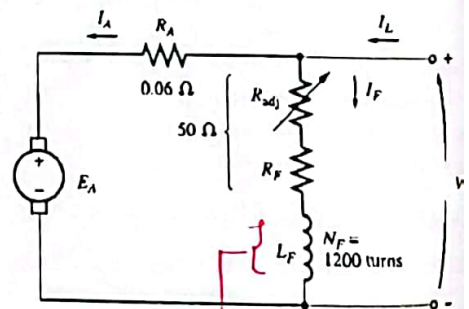- Find the speed of this motor when its input current is 100 A.
- Find the speed of this motor when its input current is 200 A.
- Find the speed of this motor when its input current is 300 A.
- Plot the torque-speed characteristic of this motor.



المقاومة  
 لكن عم مستقل  
 Steady State  
 هو بال transient  
 لما بتغير انه المقاومة  
 (مقاومته = هن)

Input power = Output power


$I_A V_A = \omega \tau \Rightarrow$  ربط

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

بجوز برسم العلاقة

→ Natural plane: shifts with time which causes sparks.

→ Power flow & losses:

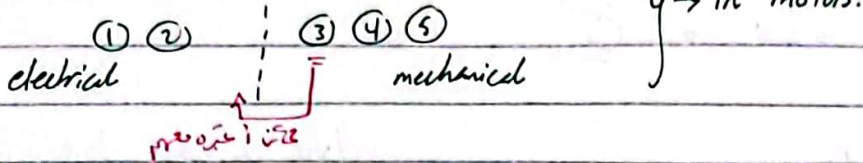

→ From AC to DC:

⇒ → It's not giving a fixed DC.

⇒ when adding coils: ← fixed ✓.

⇒ Example 1 slide 11:

$$I_F = \frac{250}{50} = 5A$$

induced current  $I_a$   $\Rightarrow$  induced voltage on EA

$$E = k\phi\omega$$

induced voltage on EA

$$\left. \begin{aligned} E_1 &= k\phi\omega_1 \\ E_2 &= k\phi\omega_2 \end{aligned} \right\} \Rightarrow \frac{E_1}{E_2} = \frac{\omega_1}{\omega_2}$$

→ a:

1200 rpm ⇒ no load rotational speed.

$$\frac{250}{244.3} = \frac{1200}{n_2} \Rightarrow n_2 = \boxed{1173 \text{ r/m}}$$

بغير حمل  $\Rightarrow$   $\omega$   $\Rightarrow$   $\omega$   $\Rightarrow$   $\omega$

250 - 0.06 \* 95 = 244.3

→ b:  $250 - 0.06 * 195 = 238.3V$

$$n_2 = \frac{1200 * 238.3}{250} = \boxed{1144 \text{ r/m}} \rightarrow \text{قلع}$$

$P_2 = 46.5 \text{ kW}$

$$\tau_2 = \frac{195 * 238.3}{1144 * 2\pi} = 388 \text{ N.m}$$

→ c:  $250 - 0.06 * 295 = 232.3V$

$$n_2 = \frac{1200 * 232.3}{250} = \boxed{1115 \text{ r/m}}$$


$P_3 = 68.5 \text{ kW}$

$$\tau_3 = \frac{295 * 232.3}{1115 * 2\pi} = 587 \text{ N.m}$$

→ d:  $\gamma = \frac{I_a V_a}{\omega}$


$$\tau_1 = \frac{I_a V_a}{\omega} = \frac{95 * 244.3}{\frac{1173}{60} * 2\pi} = 190 \text{ N.m}$$

$P_1 = 23 \text{ kW}$

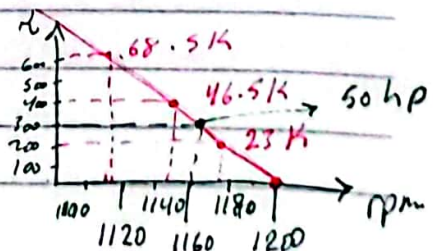
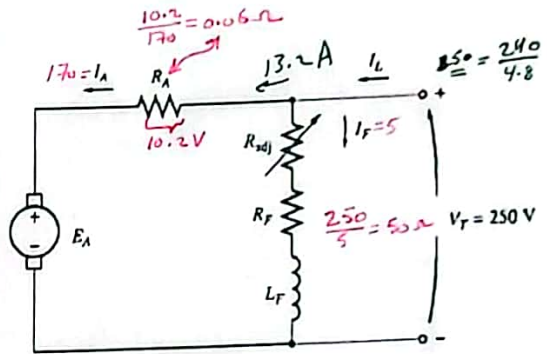
# Example 2

A 50-hp, 250-V, 1200 r/min shunt dc motor has a rated armature current of 170 A and a rated field current of 5 A. When its rotor is blocked, an armature voltage of 10.2V (exclusive of brushes) produces 170 A of current flow, and a field voltage of 250 V produces a field current flow of 5 A. The brush voltage drop is assumed to be 2 V. At no load with the terminal voltage equal to 240 V, the armature current is equal to 13.2 A, the field current is 4.8 A, and the motor's speed is 150 r/min. (Assume stray losses are 1 percent of input power)



- How much power is output from this motor at rated conditions?
- What is the motor's efficiency?

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

× انجاہ الیکٹرک کان لیفٹ علی ارمیچر کورنٹ  
 × صلیب اور ارمیچر کو الیکٹرک کوریجٹ

12

→ Mechanical input → Electrical output


× الیکٹرک کوریجٹ علی پرائم شافت

× نولہ حرکت ف  
 × برقع کوریجٹ

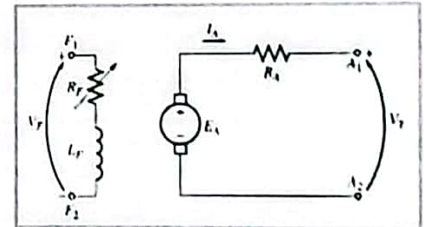
# DC Generators

DC generators are dc machines used as generator.

There are five major types of dc generators, classified according to the manner in which their field flux is produced:



- Separately Excited Generator:** In separately excited generator, the field flux is derived from a separately power source independent of the generator itself.
- Shunt Generator:** In a shunt generator, the field flux is derived by connecting the field circuit directly across the terminals of the generators.
- Series Generator:** in a series generator, the field flux is produced by connecting the field circuit in series with the armature of the generator.
- Cumulatively Compounded Generator:** In a cumulatively compounded generator, both a shunt and series field is present, and their effects are additive.
- Differentially Compounded Generator:** In differentially compounded generator, both a shunt and a series field are present, but their effects are subtractive.

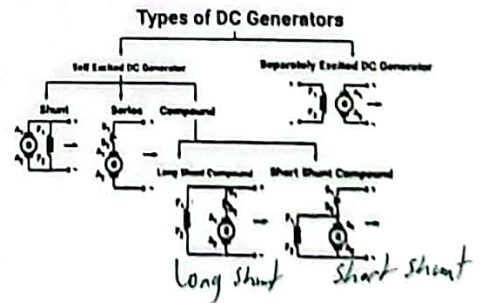

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

(2) الیکٹرک کوریجٹ علی ارمیچر (I) generator کو لیتا ہے الیکٹرک کوریجٹ علی ارمیچر


13



→ Example 2 slide 12

↳ 50 hp : mechanical power that gives the rated value.

↳ 1200 → rated N

↳ Brush → 2V → 

→ a:

$$P_{out} = P_{in} - P_{losses}$$

$$I_L \text{ total current} = 170 + 5 = 175A$$

$$175 \times 250 = 43750W \rightarrow \text{input power.}$$

$$\text{Losses } I^2R : (170)^2 \times 0.06 + 5^2(50) = 1734 + 1250 = 2984 W$$

$$\text{brushes: } VI$$

$$= 2 \times 170 = 340W$$

$$\text{stray: } 0.01 \times 43750 = 437.5W$$

$$P_{mch} + P_{core} \Rightarrow V_{nl} \times I_{nl} = 240 \times 13.2 = 3168W$$

$$\Rightarrow 43750 - (2984 + 340 + 3168 + 437.0)$$

$$P_{out} = 36820 W \leftarrow \text{horse power}$$

$$\rightarrow b: \frac{36820}{43750} \times 100\% = 84.2\%$$




↳ considered really good efficiency.

\* لو ايجب \* 100hp بدل 50hp ، كمد ال efficiency براه ال انا .  
 \* لو عندي system ال power capability ال بتراوح بين 50hp ← 100hp ، بدل ما ايجب  
 100hp بجيب 2 \* 50hp ، و قد حا بلزمني تشتغل على 50 بتك واحد واذا بي  
 تشتغل على 100 بتك ال 2 مع بعض .



Self  
made  
manual

# Motors and Generator in Cars

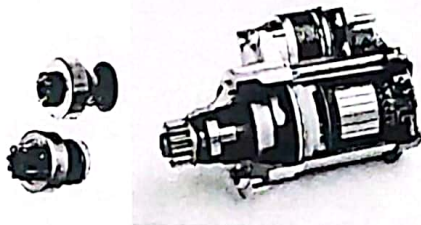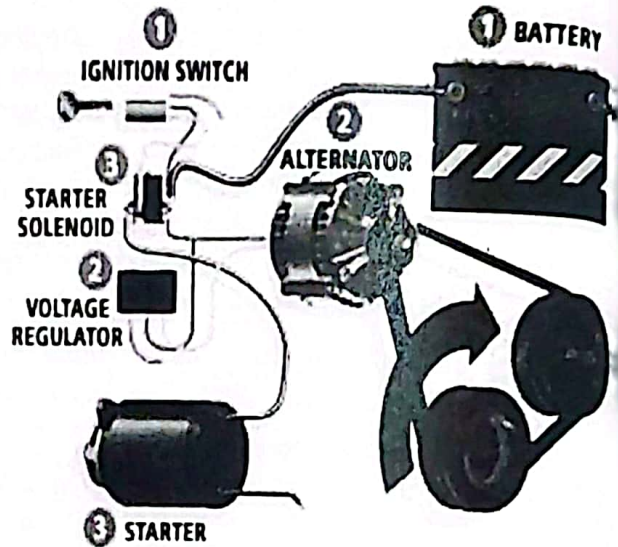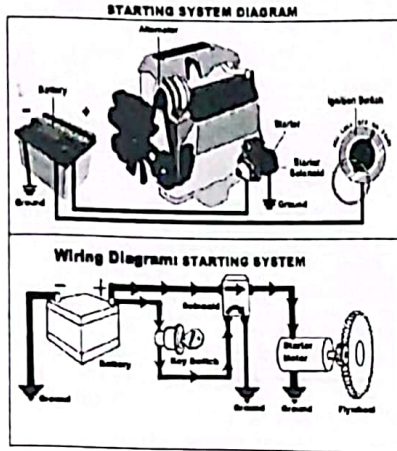


\* Alternator يطلع AC ويتحول لـ DC  
و يساعده شحن البطارية.

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

# Brushed DC Motor Type Comparison

Characteristic	Electromagnet			
	Permanent Magnet	Shunt	Series	Compound
COST	Low	Moderate	Moderate	High
Loss of Magnetism	Worst لأنه أجلا مغناطيس عن طريق التخزين أو الألف.	None	None	None
Torque vs. Speed	Good at low speed Less at high speed	Good, consistent at low speed.	Great at low speed	Best at low speed شغل بالبطارية زي شغل series جيتو شانت
Safety ( Motor Runaway ) ان زحف المحرك	No chance	High chance بالسرعات العالية تلف بسرعة.	High chance	Low chance
Speed Control	Excellent L	Excellent L	Poor صعاب فيه	Great L

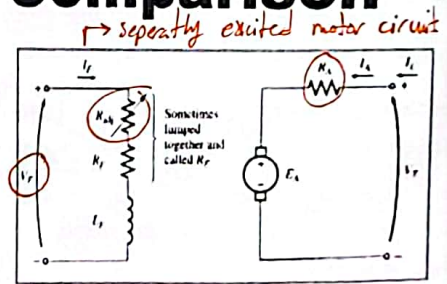

Speed control methods for dc motors are simpler and less expensive than those for ac motors. The speed of a dc motor can be changed by using the following methods:

- (a) Field control method
- (b) Armature resistance control method
- (c) Armature voltage control method

← بالبطارية بتقاس بـ  $V_f$  أو  $R_{fd}$ .

أبسيانه  
طيفي الكاراك  
أو يكون ما في  
load.

non-linear









Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

- \* A transistor has 3 modes of operation:
  - ① Cutoff (logic 0)
  - ② Active region.
  - ③ Saturation (logic 1)

\* A transistor can be used as a switch.

\* Transistors → MOSFET → BST  
 ← التيار يتم بقلعة او (control)  
 بقولم بار gate voltage

# Switching Circuitry

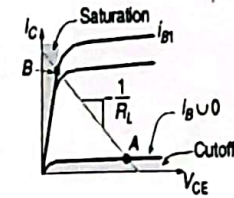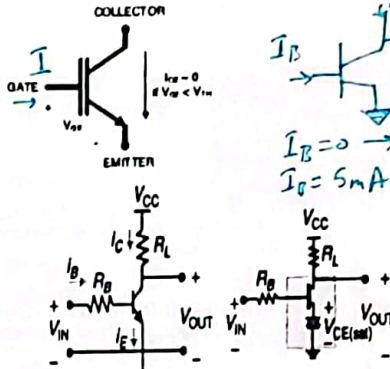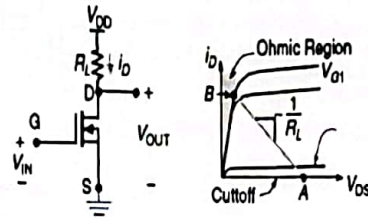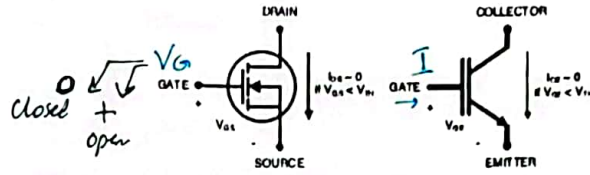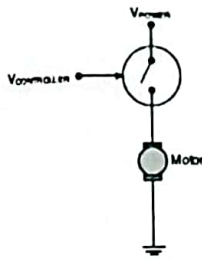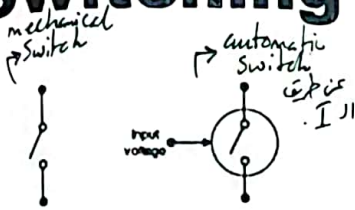

$V_{out} = 5V$   
 $I_B = 0 \rightarrow V_{out} = 5V$   
 $I_B = 5mA \rightarrow V_{out} = 0V$



Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

# Pulse Width Modulation (PWM)


With an electrical switch, the controller can turn a motor's current fully on or fully off. But what if you want the motor to rotate at 75% of its full speed? What if you want the motor's speed to ramp up gradually?

Instead, controllers govern the motor's behaviour by delivering pulses that open and close the switch for precise amounts of time. This pulse delivery is referred to as pulse width modulation, or PWM.

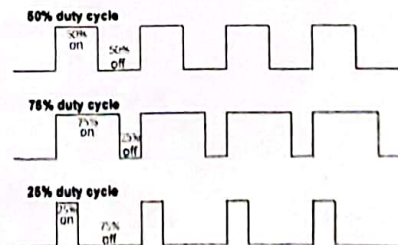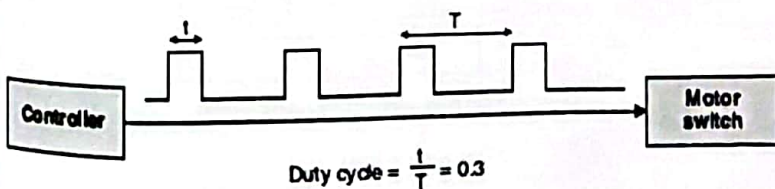Pulse Width Modulation is used when the amount of power delivered to the DC Motor is to be reduced without decreasing the input voltage.



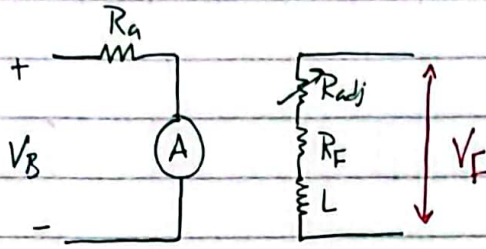Prepared by Dr. Musa Alyaman Electrical Machines (0908321)



$$V_B = I_a R_a + V_{ind}$$

$$V_B = I_a R_a + k\phi\omega$$


$$\tau = kI_a\phi \Rightarrow I_a = \frac{\tau}{k\phi}$$

$$\Rightarrow V_B = \frac{\tau}{k\phi} R_a + k\omega\phi \Rightarrow \frac{\tau}{k\phi} = \frac{V_B}{k\phi} - \omega$$

$$\tau = \frac{V_B k\phi}{R_a} - \frac{(k\phi)^2 \omega}{R_a}$$


↓ slope

$y = c - m\omega$  ← صيغة خط مستقيم

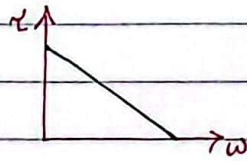

Case 3: تغير  $R_a$

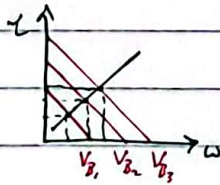⇒ Case 1: تغير  $V_B$  بتغيير كومات components:



$$V_{B3} > V_{B2} > V_{B1}$$

\*  $\omega$  و  $\tau$  يتغيران مع  $V_B$  بدون تغيير

في steady-state condition

التي  $\tau = \tau_{ind}$  و  $\omega = \omega_{ind}$

عند  $\omega = \omega_{ind}$  و  $\tau = \tau_{ind}$  rated

التي  $\tau = \tau_{max}$  (maximum power)


(بين  $\omega$  و  $\tau$  يتغير)

⇒ Case 2: تغير  $R_F$

و كومات components ثابتين.

← بتغيير  $V_B$  و بتغيير  $R_a$  بتغيير  $\phi$  عن طريق  $R_{adj}$ ، العلاقة بين  $\phi$  و  $\tau$  و  $\omega$

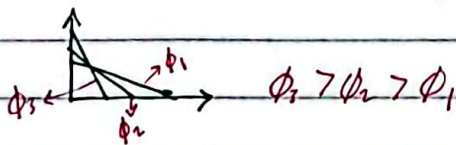(بتغير  $\omega$  slope و بتغير  $\tau$  slope  $y$ )



$$\phi_3 > \phi_2 > \phi_1$$



current through winding is increased by increasing the armature current of Motor. Flyback diode is used to protect the winding from the back EMF generated when the motor is switched off. Flyback diode provides a path for the current to flow when the switch is off.

# Control Circuitry

Controlling a brushed motor is straightforward because the motor's operation is so easy to understand.





- Single-direction control— If the motor only needs to turn in one direction, the circuit can be easily constructed with a transistor.

*forward & reverse*  
Dual-direction control— If the motor's direction needs to be changed, an H bridge should be added to the circuit.  
Ex: elevator

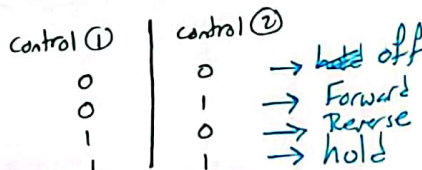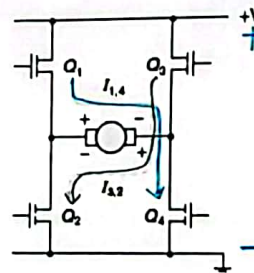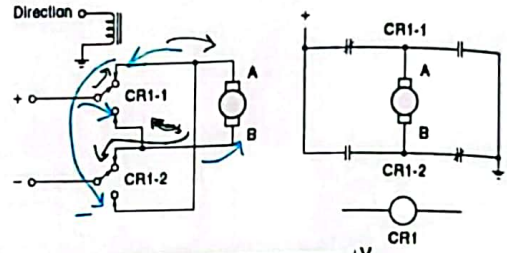
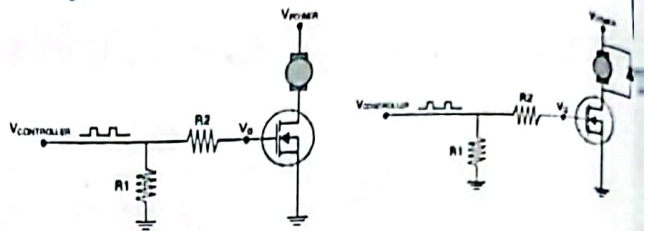
## Control of DC Motors

- Switch ON-OFF ← Transistor
- Speed ← PWM
- Direction ← H. Bridge

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)



# L293D H Bridge

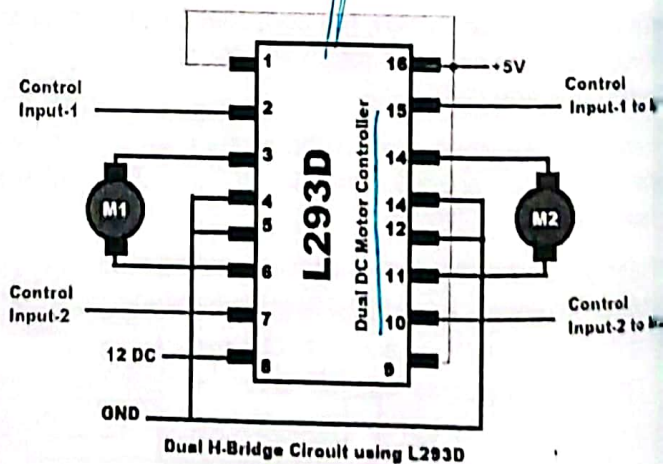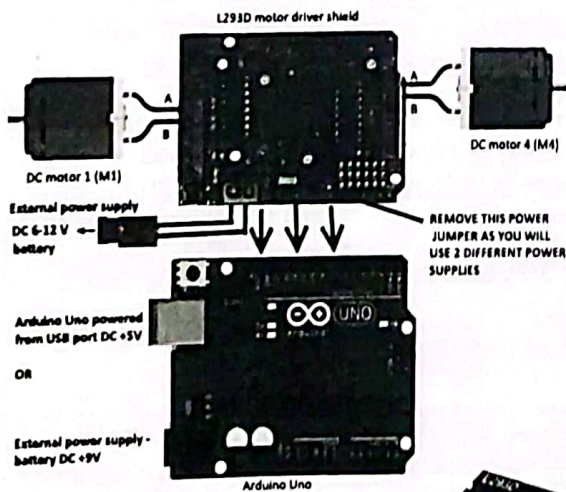

All Inputs Low Motor M1 & M2 = OFF.  
Input-1 is High and Input-2 is Low Motor M1 = Forward Direction.  
Input-1 is Low and Input-2 is High Motor M1 = Backward Direction.

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)

↓ Rotor is Permanent magnet and stator is coils : *ساي* Brushless DC ←  
 \*no need for brushes in this case.

# Brushless DC Motors

BLDCs are more complex and more expensive than brushed motors, but because there's no mechanical contact between the rotor and stator, they're more reliable and efficient.




The controller delivers positive and negative current to different windings in a sequence, and the rotor spins to follow the change in current.

The windings' names are important because windings with the same name are connected. That is, both windings named A receive current at the same time, as do both windings named B and both windings named C. In this manner, the controller only has to deliver three inputs to the motor. For this reason, this BLDC is called a three-phase motor. More phases are possible, but most BLDCs are three-phase motors.

BLDCs can be divided into two categories depending on the relative positions of the rotor and stator.

- If the rotor turns inside the stator, the motor is an inrunner.
- If the rotor turns outside the stator, it's an outrunner.

↳ used in PC

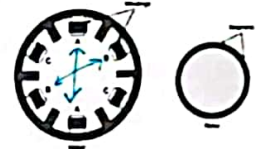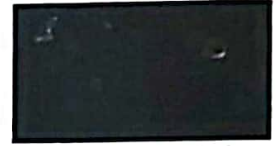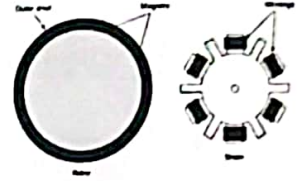

# Brushless DC Motors

## Applications


- CPU cooling fans
- CD/DVD Players
- Electric automobiles (*cars*)

## Pros


- Higher efficiency
- Longer lifespan, low maintenance
- Clean, fast, no sparking/issues
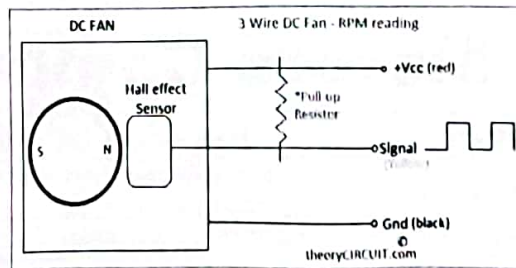
## Cons

- Higher cost
  - More complex circuitry and requires a controller
- ↳ harder to control.



fan parts >>

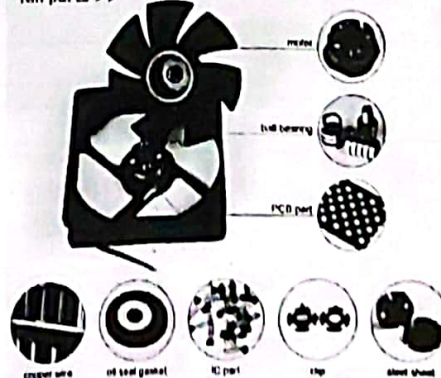

↳ outrunner



A + -  
 B - +  
 C f f  
 Floating

6 احتمالات  
 \* وكل 6 احتمالات  
 عبارة عن لفحة واحدة

( الزاوية بينهم 60° )

# Controlling BLDC





A three-phase BLDC has three inputs that deliver current to the windings. At any time, one input will be set high (V+), one will be set low (V-), and one will be left floating.

For a three-phase BLDC, there are only six unique phase states before they repeat. As the controller energizes the windings through these states, the rotor makes a complete rotation (360°). Therefore, each phase state corresponds to one-sixth of the complete turn, or 60°.

If the controller delivers more current, the motor will exert more torque as it rotates. If the pulses' order and timing is reversed, the motor will turn in the reverse direction. For this reason, BLDC control circuits don't require the H bridges needed to reverse brushed motors.

BLDCs receive power through special switching circuits called voltage source inverters, usually shortened to *inverters*

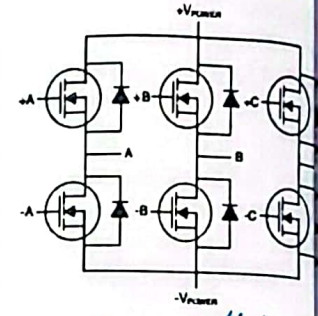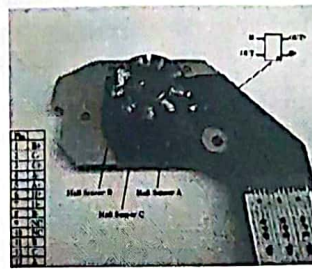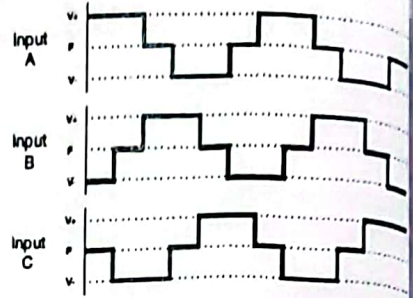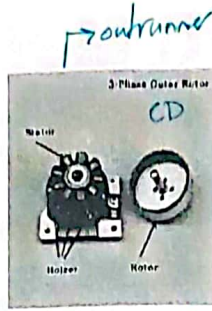Sensored motor control is easier to implement and more reliable than sensorless control, but sensed BLDCs require additional circuitry, which means larger motors and higher cost.



↳ no need for H-Bridge to change the direction !!

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)


→ sensor [Hall effect sensor]  
 → sensorless  
 Floating

(with sensor) ولكنة انه لا يمكن في اوجه (دس ا) (with sensor)

Brushed control له ايجابيات في ال direction  
 تيار ال current  
 و في ال true  
 و في ال -ve

# \* DC Motors Comparison

Feature	Brushless DC Motor	Brushed DC Motor
Commutation	Electronic commutation based on Hall position sensors	Brushed commutation
Maintenance	Less or no maintenance	Periodic maintenance
Life	Longer	Shorter
Speed / Torque	Enable operations on all speeds with rated load	At higher speeds, brush friction increases and reduce torque
Efficiency	High	Moderate
Speed Range	Higher - No mechanical limitation due to contact	Lower - Mechanical limitations due to brushes
Electric Noise Generation	Low - because it has permanent magnets on the rotor, improves dynamic response	Arcs in the brushes will generate electric noise

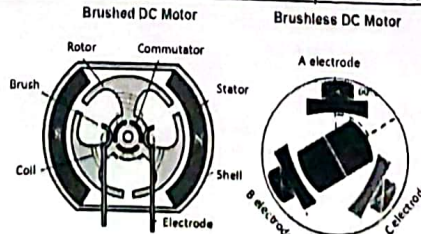

Prepared by Dr. Musa Alyaman Electrical Machines (0908321)